

# EEE104

# Circuit Analysis I

Ankara University

Faculty of Engineering

Electrical and Electronics Engineering Department

# Circuit Variables

EEE104 Circuit Analysis I

Lecture 1

# Agenda

- Circuit Variables
- Circuit Theory
- Voltage and Current
- Passive Sign Convention
- Power and Energy

- Electric circuit: Mathematical model of actual electrical system.
- Circuit Theory:
  - Lumped-parameter system
  - Zero net charge
  - No magnetic coupling

## Voltage and Current

$$\text{Voltage: } v = \frac{dw}{dq}$$

$v$ : Voltage (Volt)

$w$ : Energy (Joule)

$q$ : Charge (Coulomb)


Current:

$$i = \frac{dq}{dt}$$

*i*: Current (Ampere)

*t*: Time (second)

# Ideal Basic Circuit Element

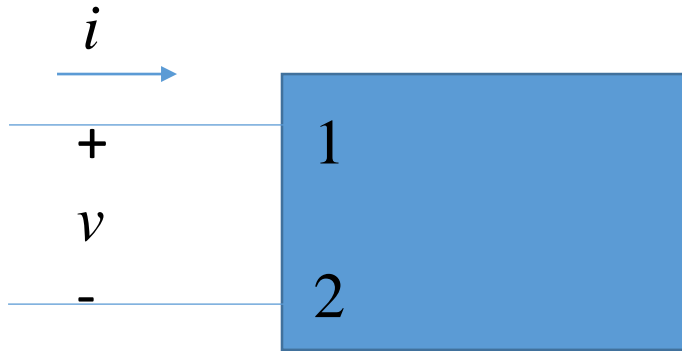

- Passive Sign Convention:



Positive sign for any equation that relates current and voltage if current enters to the terminal with positive sign of voltage,



Negative sign, otherwise

## Power and Energy


$$p = \frac{dw}{dt}$$

$p$ : Power (Watt)


$w$ : Energy (Joule)

$$p = vi$$




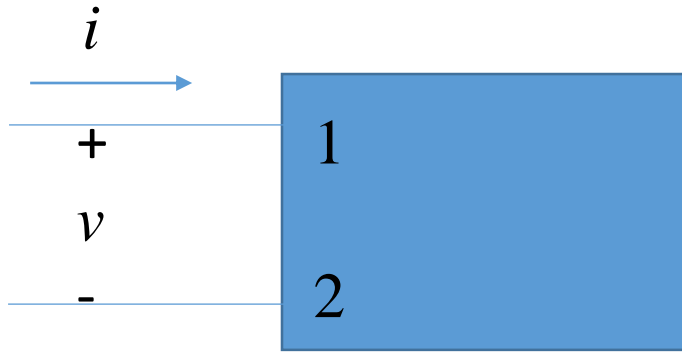


$$p=vi$$

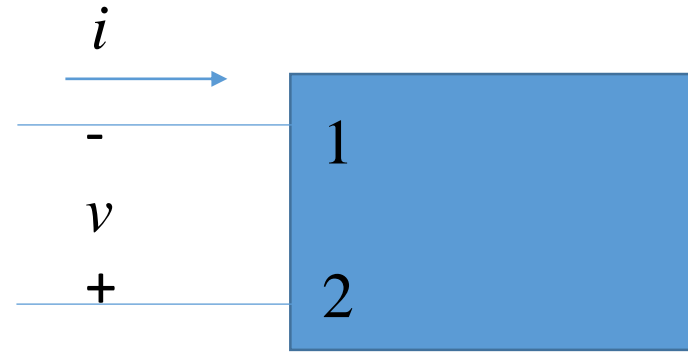

$$p=-vi$$

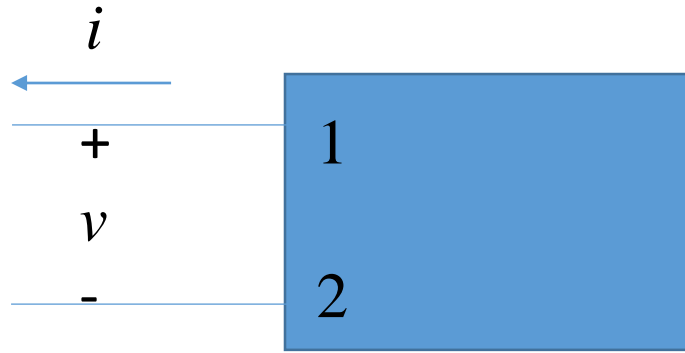

$$p = -vi$$

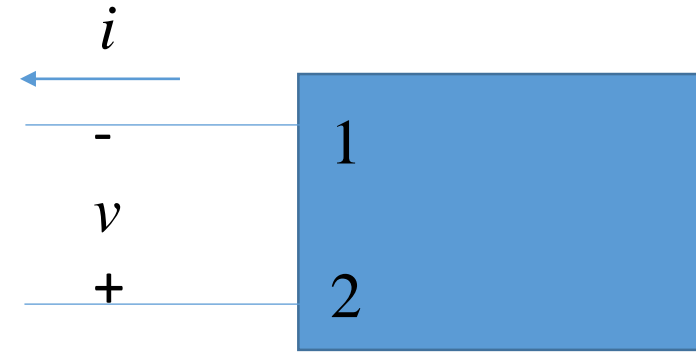

$$p = vi$$

# Reference

- Electric Circuits, Tenth Edition, James W. Nilsson, Susan A. Riedel  
Pearson, 2015