

# EEE104

# Circuit Analysis I

Ankara University

Faculty of Engineering

Electrical and Electronics Engineering Department

# Circuit Elements


EEE104 Circuit Analysis I

Lecture 2

# Agenda


- Voltage Sources
- Current Sources
- Electrical Resistance

## Voltage Source

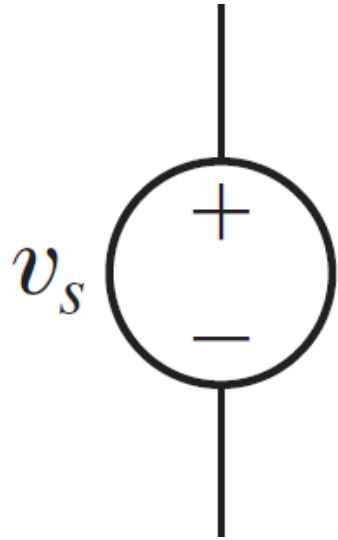


Ideal independent voltage source

## Current Source

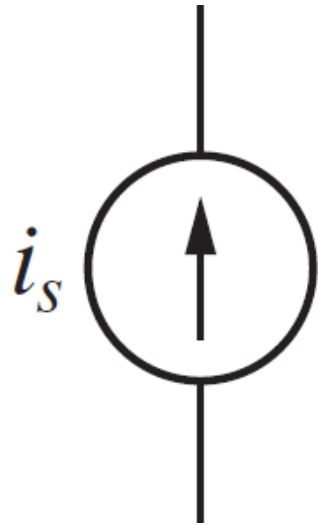


Ideal independent current source

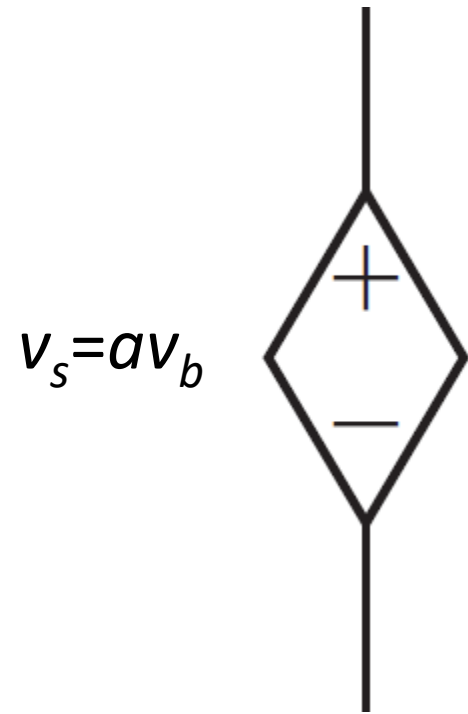
## Ideal dependent voltage-controlled voltage source


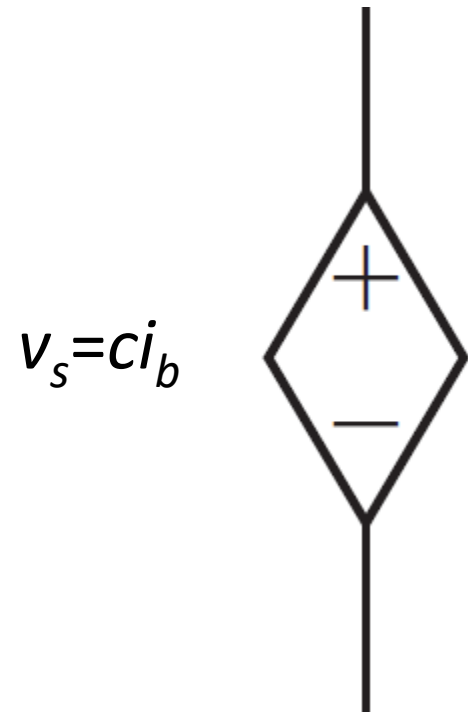
## Ideal dependent current-controlled voltage source



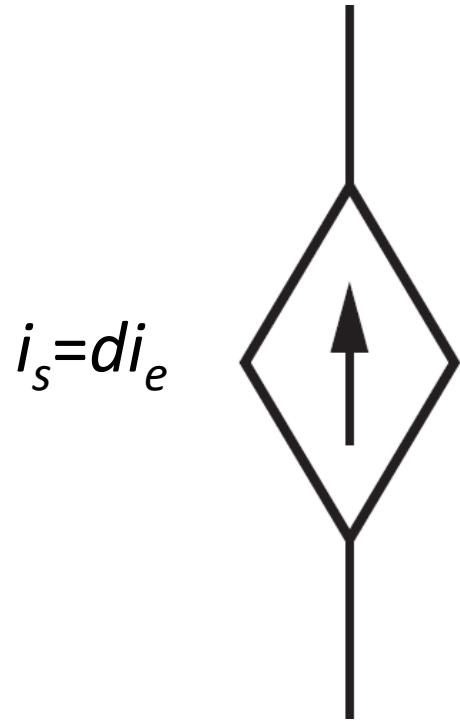
## Ideal dependent current-controlled current source






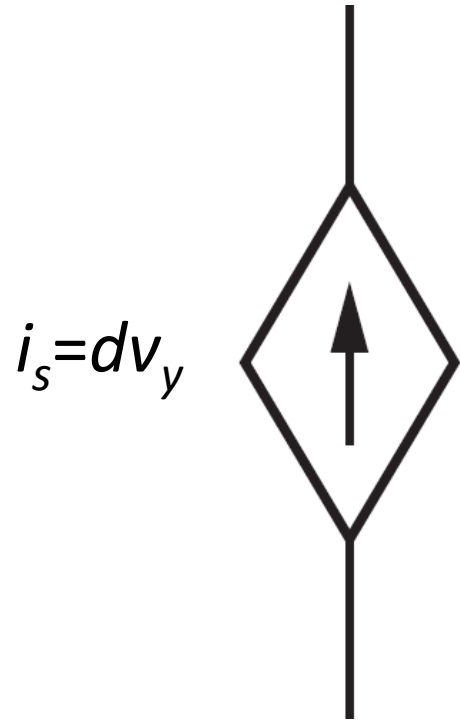
## Ideal dependent voltage-controlled current source



# Electrical Resistance

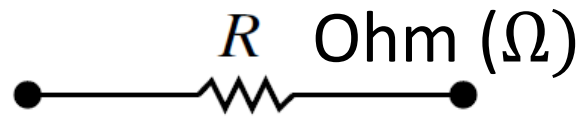

Ohm's Law

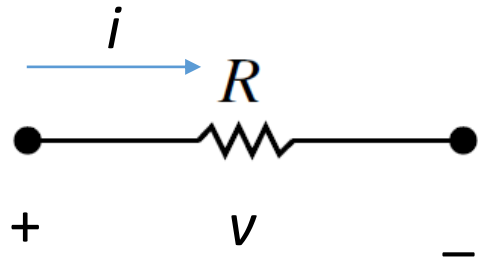

$$v=iR$$



Resistor


- Conductance:

$$G = \frac{1}{R} \text{ Siemens (S) or Mho (}\mathcal{U}\text{)}$$

$$i = \frac{v}{R}$$

$$i = vG$$

Power dissipated in resistor:

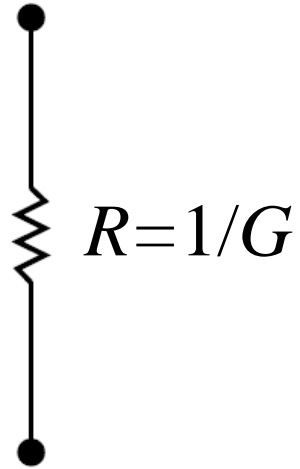

$$p = vi \quad v = iR$$

$$p = i^2 R = \frac{i^2}{G}$$

$$p = v^2 G = \frac{v^2}{R}$$

# Reference

- Electric Circuits, Tenth Edition, James W. Nilsson, Susan A. Riedel  
Pearson, 2015