

# EEE201

# Circuit Analysis II

Ankara University

Faculty of Engineering

Electrical and Electronics Engineering Department

# Sinusoidal Steady-State Analysis

EEE201 Circuit Analysis II

Lecture 3


# Agenda

- Series, Parallel, and  $\Delta$ -to-Y Simplifications
- Source Transformations
- Thevenin-Norton Equivalent Circuits

# Series, Parallel, and $\Delta$ -to-Y Simplifications

Combining impedances in series:


$$Z_{ab} = Z_1 + Z_2 + \dots + Z_n$$

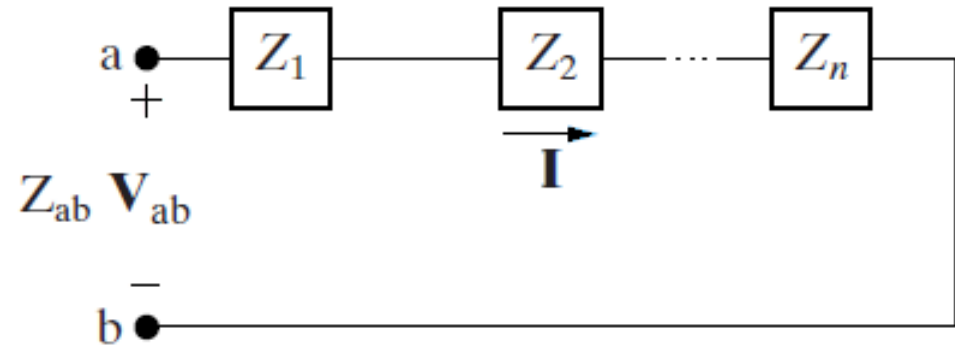
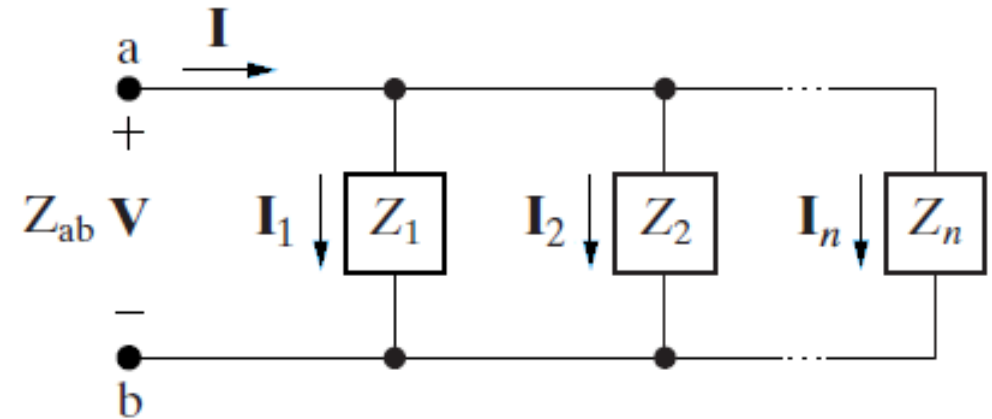
# Series, Parallel, and $\Delta$ -to-Y Simplifications

Combining impedances in parallel:

$$\frac{1}{Z_{ab}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$$




# Series, Parallel, and $\Delta$ -to-Y Simplifications

$\Delta$ -to-Y transformation:

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$
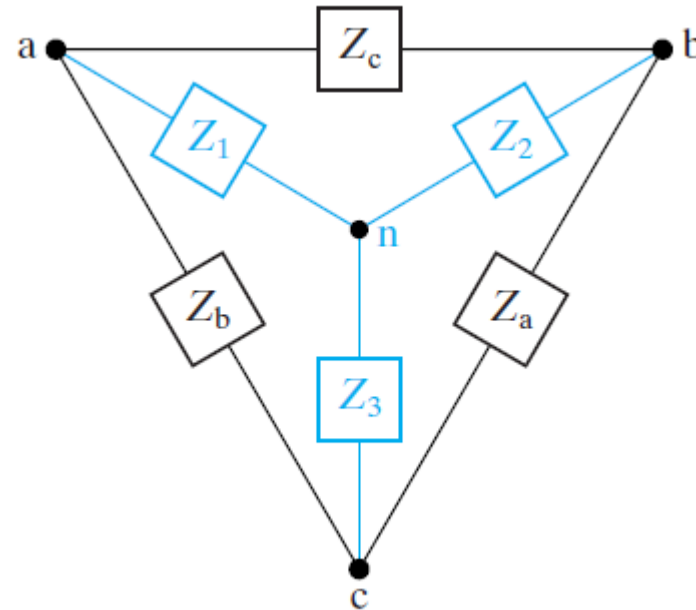
$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$




# Series, Parallel, and $\Delta$ -to-Y Simplifications

Y-to- $\Delta$  transformation:


$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$
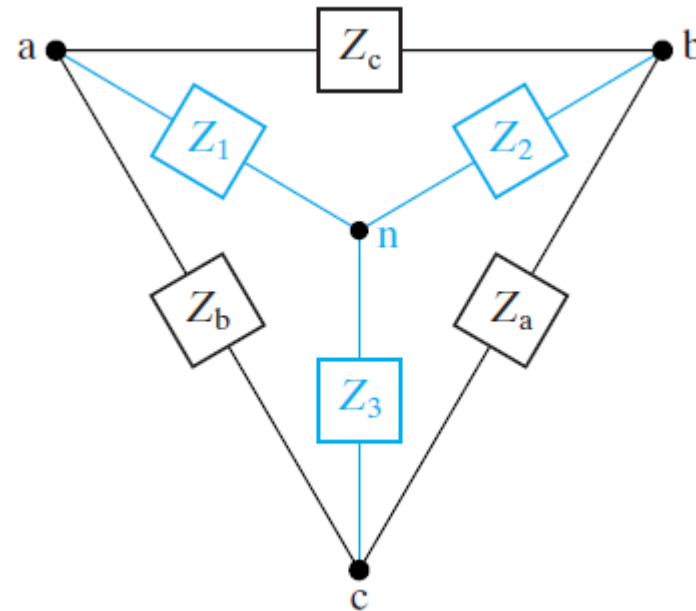
$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$




# Source Transformations

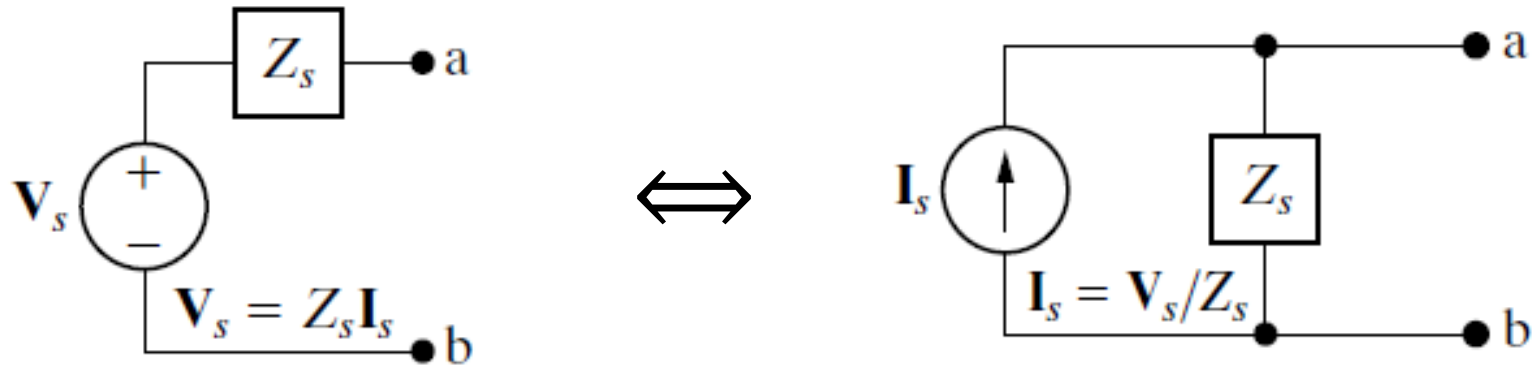




# Thevenin-Norton Equivalent Circuits

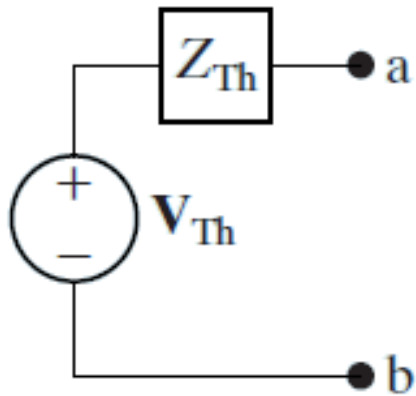

Thevenin equivalent circuit

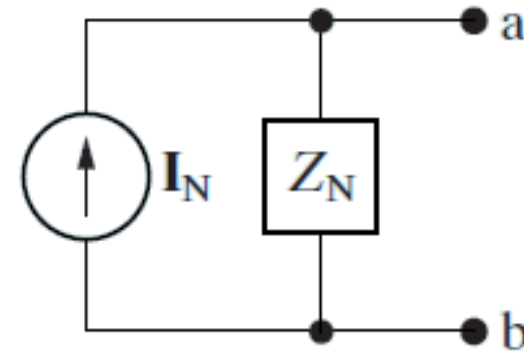

Norton equivalent circuit

# Reference

- Electric Circuits, Tenth Edition, James W. Nilsson, Susan A. Riedel  
Pearson, 2015