

# EEE201

# Circuit Analysis II

Ankara University

Faculty of Engineering

Electrical and Electronics Engineering Department

# Introduction to Frequency Selective Circuits

EEE201 Circuit Analysis II

Lecture 13

# Agenda


- Concept of Frequency-Selective Circuits
- Low-Pass Filters (LPFs)
- High-Pass Filters (HPFs)

# Concept of Frequency-Selective Circuits


Frequency-selective circuits are also called **filters**. Their ability is to filter out certain input signals on the basis of frequency:

- Passband
- Stopband
- Frequency response plot: Magnitude plot and phase angle plot
- Cut-off frequency
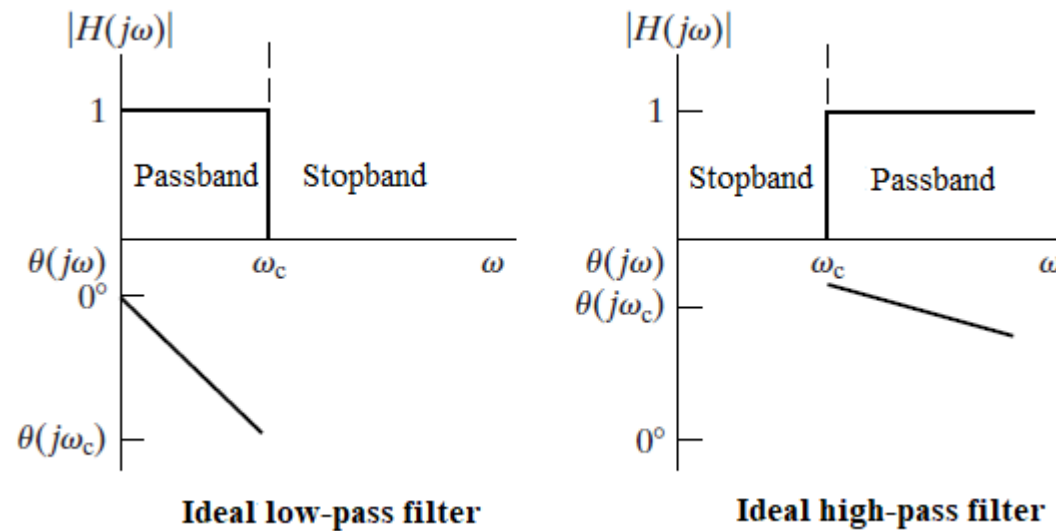
# Concept of Frequency-Selective Circuits



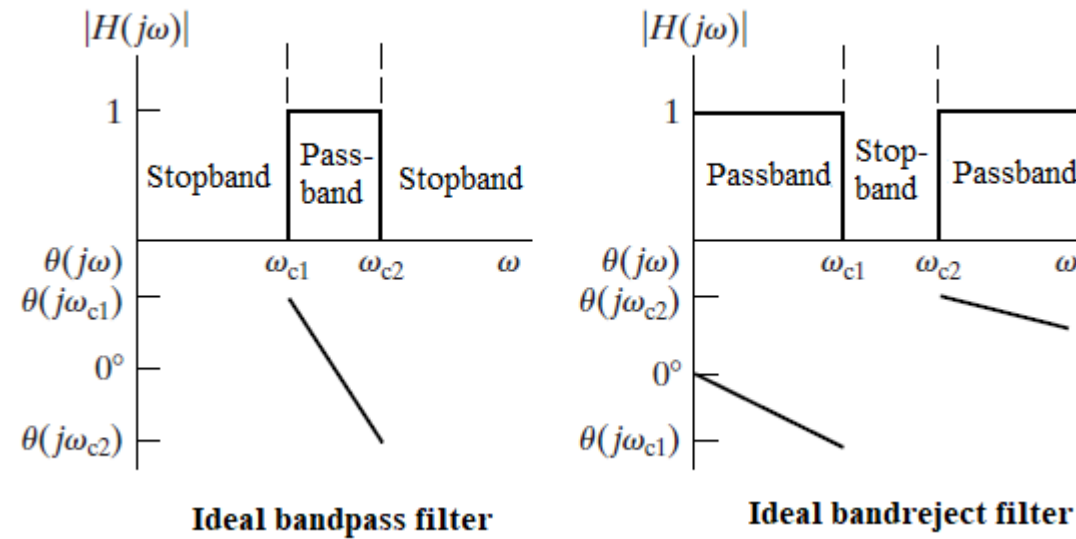
# Concept of Frequency-Selective Circuits



# Low-Pass Filters: The Series RL Circuit

Voltage transfer function:

$$H(s) = \frac{R/L}{s + R/L}$$

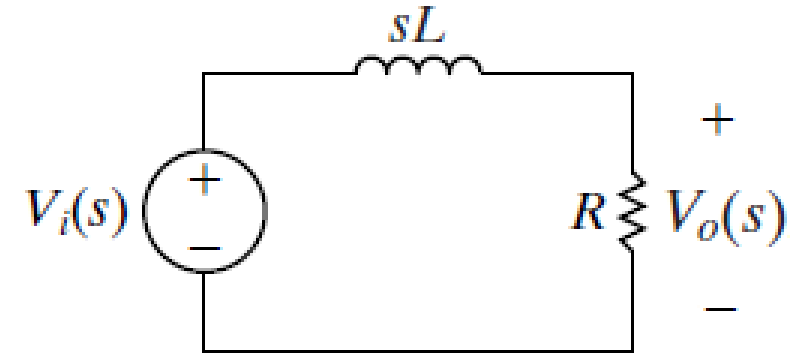

Let's make the substitution  $s = j\omega$ ,

$$H(j\omega) = \frac{R/L}{j\omega + R/L}$$


# Low-Pass Filters: The Series RL Circuit

Transfer function magnitude:

$$|H(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + (R/L)^2}}$$

Transfer function phase angle:
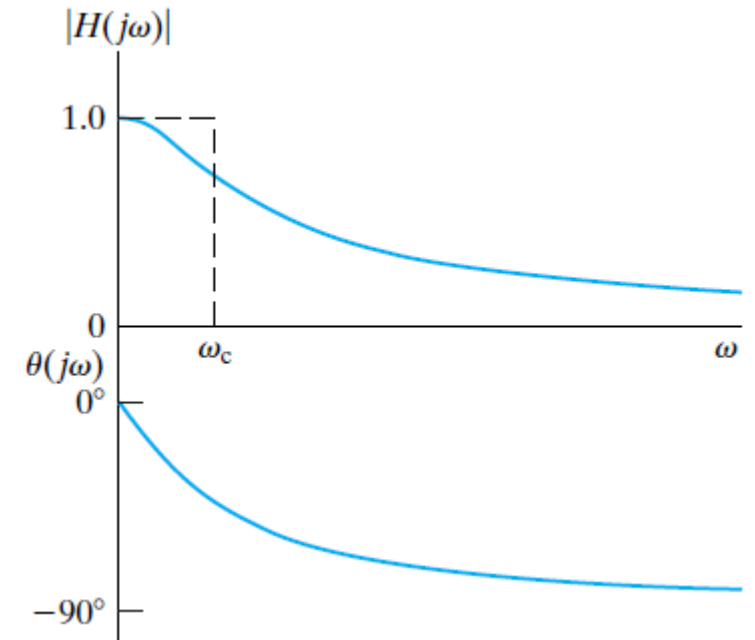
$$\theta(j\omega) = -\tan^{-1}\left(\frac{\omega L}{R}\right)$$





# Low-Pass Filters: The Series RL Circuit

Let's define the cut-off frequency,

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} H_{max}$$

$\omega_c$  is also called the half-power frequency,

$$P(j\omega_c) = \frac{P_{max}}{2}$$


For RL filters,

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} |1| = \frac{R/L}{\sqrt{\omega_c^2 + (R/L)^2}} \rightarrow \omega_c = \frac{R}{L}$$
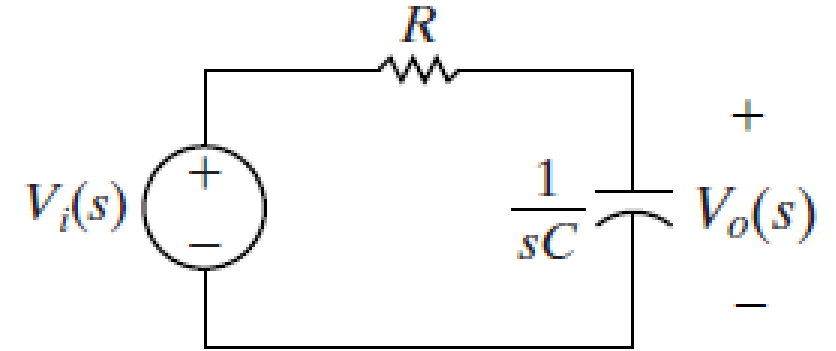
# Low-Pass Filters: The Series RC Circuit

Voltage transfer function:

$$H(s) = \frac{\frac{1}{RC}}{s + \frac{1}{RC}}$$



Let's make the substitution  $s = j\omega$ ,

$$H(j\omega) = \frac{\frac{1}{RC}}{j\omega + \frac{1}{RC}}$$

# Low-Pass Filters: The Series RC Circuit

Transfer function magnitude:

$$|H(j\omega)| = \frac{\frac{1}{RC}}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}}$$


Cut-off frequency:

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} |1| = \frac{\frac{1}{RC}}{\sqrt{\omega_c^2 + \left(\frac{1}{RC}\right)^2}} \rightarrow \omega_c = \frac{1}{RC}$$

# High-Pass Filters: The Series RC Circuit

Voltage transfer function:

$$H(s) = \frac{s}{s + \frac{1}{RC}}$$

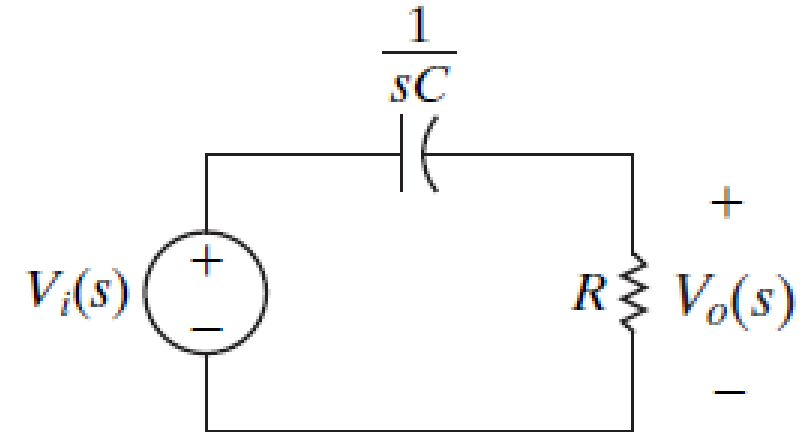

Let's make the substitution  $s = j\omega$ ,

$$H(j\omega) = \frac{j\omega}{j\omega + \frac{1}{RC}}$$

# High-Pass Filters: The Series RC Circuit

Transfer function magnitude:


$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}}$$

Transfer function phase angle:

$$\theta(j\omega) = 90^\circ - \tan^{-1}(\omega RC)$$

Cut-off frequency:


$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} |1| = \frac{\omega_c}{\sqrt{\omega_c^2 + \left(\frac{1}{RC}\right)^2}} \rightarrow \omega_c = \frac{1}{RC}$$

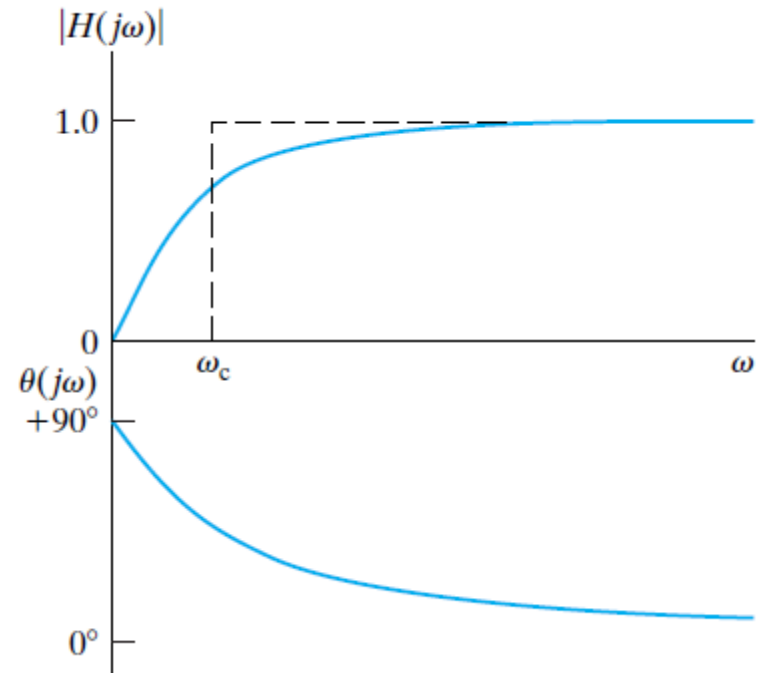

# High-Pass Filters: The Series RL Circuit

Voltage transfer function:

$$H(s) = \frac{s}{s + R/L}$$

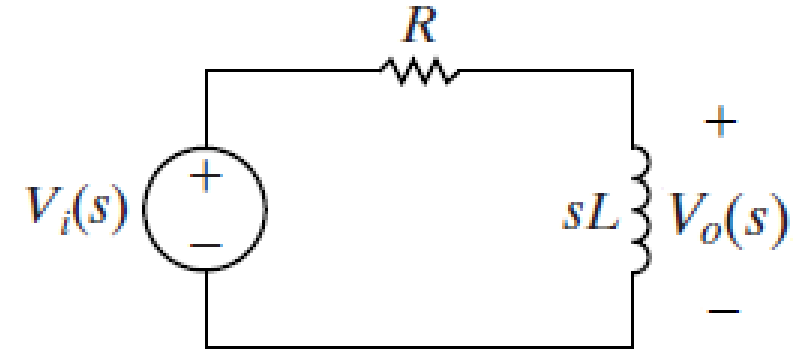

Let's make the substitution  $s = j\omega$ ,

$$H(j\omega) = \frac{j\omega}{j\omega + R/L}$$

# High-Pass Filters: The Series RL Circuit

Transfer function magnitude:

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + (R/L)^2}}$$

Cut-off frequency:

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} |1| = \frac{\omega_c}{\sqrt{\omega_c^2 + (R/L)^2}} \rightarrow \omega_c = \frac{R}{L}$$

# Reference

- Electric Circuits, Tenth Edition, James W. Nilsson, Susan A. Riedel  
Pearson, 2015