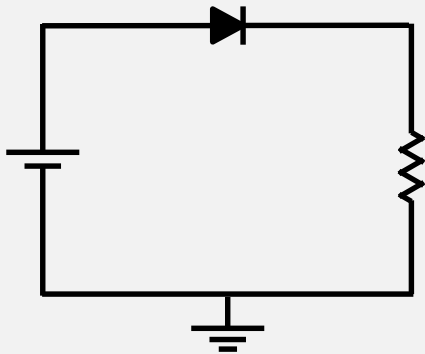





BME 202 Electronics

Lecture 3: Diode Applications

Load-Line Analysis



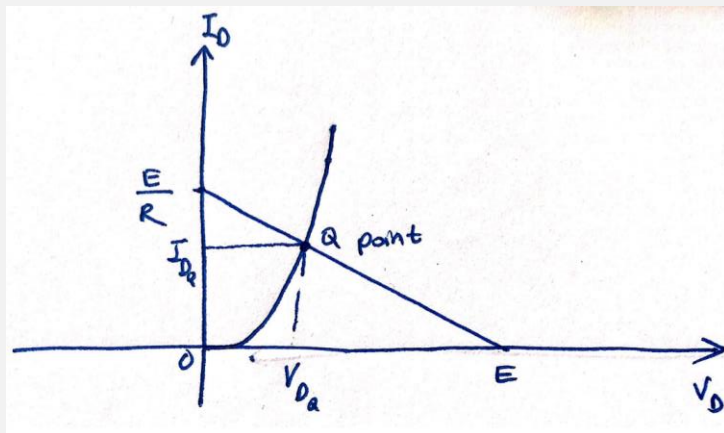The load line plots all possible combinations of diode current (I_D) and voltage (V_D) for a given circuit. The maximum I_D equals E/R , and the maximum V_D equals E .




The point where the load line and the characteristic curve intersect is the **Q-point**, which identifies I_D and V_D for a particular diode in a given circuit.

Series Diode Configurations

Analysis (for silicon)

Forward Bias

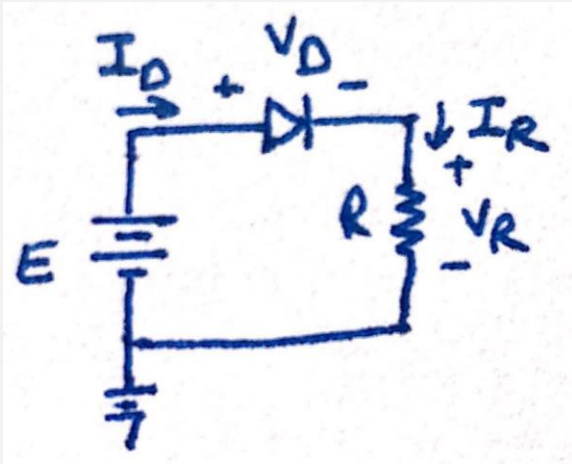

$$V_D = 0.7 \text{ V (or } V_D = E \text{ if } E < 0.7 \text{ V)}$$

$$V_R = E - V_D$$

$$I_D = I_R = I_T = V_R / R$$

Reverse Bias

$$V_D = E$$

$$V_R = 0 \text{ V}$$


$$I_D = 0 \text{ A}$$

Constants

Silicon Diode: $V_D = 0.7 \text{ V}$

Germanium Diode: $V_D = 0.3 \text{ V}$

Paralel Diode Configurations

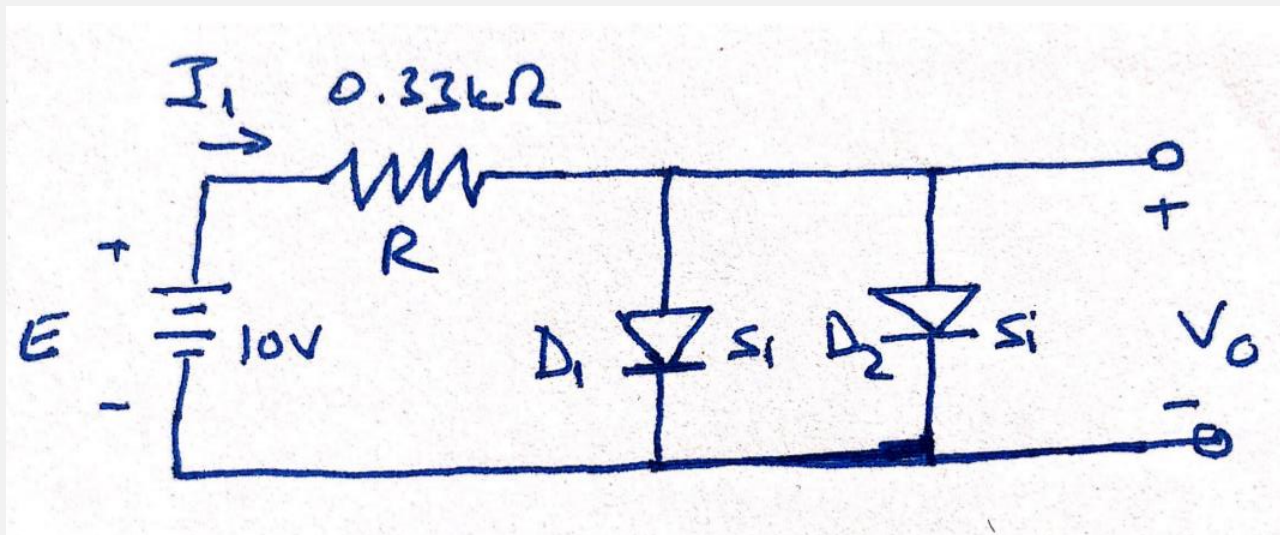

Half Wave Rectifier

The diode conducts only when it is forward biased, therefore **only half of the AC cycle** passes through the diode to the output.

The DC output voltage is $0.318V_m$, where V_m = the peak AC voltage.

PIV (PRV)

The diode is only **forward biased for one-half** of the AC cycle and is **reverse biased for the other half** cycle.

It is important that the reverse breakdown voltage rating of the diode be high enough to withstand the peak, reverse-biasing AC voltage.


$$\mathbf{PIV \text{ (or PRV)} > V_m}$$

where, **PIV** : Peak inverse voltage

PRV : Peak reverse voltage

V_m : Peak AC voltage

Full Wave Rectifier

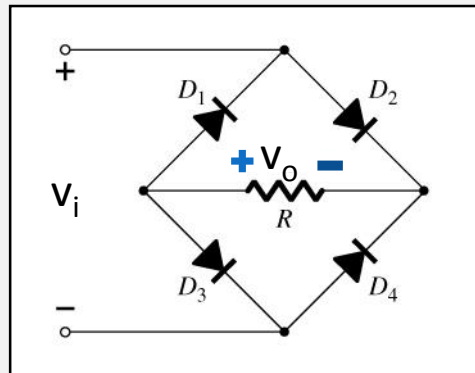


Bridge Rectifier

A full-wave rectifier with four diodes that are connected in a bridge configuration

$$V_{DC} = 0.636 V_m$$

Full Wave Rectifier

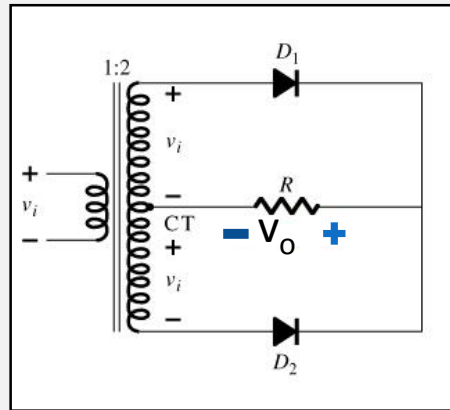

Center-Tapped Transformer Rectifier

Requires two diodes and a center-tapped transformer

$$V_{DC} = 0.636V_m$$

Summary of Rectifier Circuits

Rectifier	Ideal V_{DC}	Realistic V_{DC}
Half Wave Rectifier	$V_{DC} = 0.318V_m$	$V_{DC} = 0.318V_m - 0.7$
Bridge Rectifier	$V_{DC} = 0.636V_m$	$V_{DC} = 0.636V_m - 2(0.7 \text{ V})$
Center-Tapped Transformer Rectifier	$V_{DC} = 0.636V_m$	$V_{DC} = 0.636V_m - 0.7 \text{ V}$

Clippers are networks that employ diodes to “clip” away a portion of an input signal without distorting the remaining part of the applied waveform.


e.g. Half wave rectifier

Categories of Clippers

- *Series*
- *Parallel*


Clippers

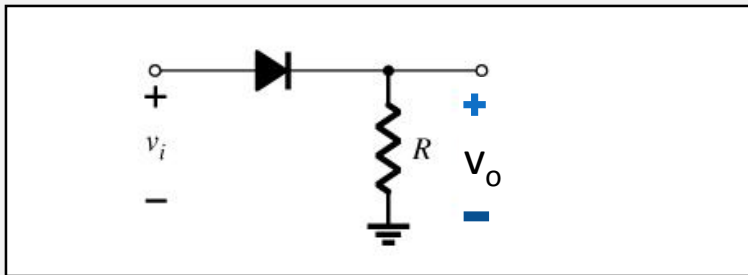The diode in a series clipper “clips” any voltage that does not forward bias it:




- A reverse-biasing polarity
- A forward-biasing polarity less than 0.7 V (for a silicon diode)

Biased Clippers

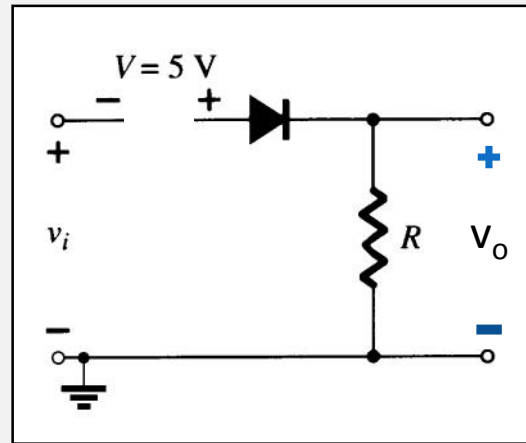

Adding a DC source in series with the clipping diode changes the effective forward bias of the diode.


Parallel Clippers

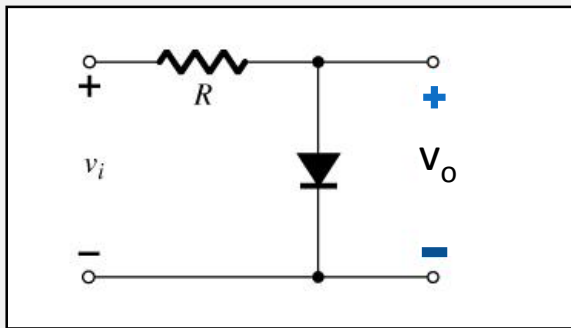

The diode in a parallel clipper circuit “clips” any voltage that forward biases it.

DC biasing can be added in series with the diode to change the clipping level.




Clampers

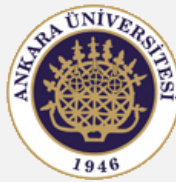

A clamper is a network constructed of a diode, a resistor, and a capacitor that **shifts** a waveform to a different DC level without changing the appearance of the applied signal.

Clamping networks have a **capacitor** connected **directly from input to output** with a **resistive element** in parallel with the **output** signal. The **diode** is also **in parallel with the output** signal but may or may not have a series DC supply as an added element.


Clampers

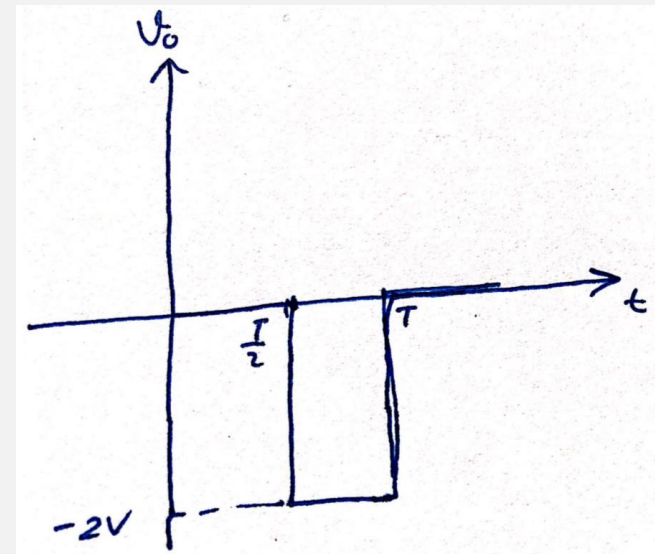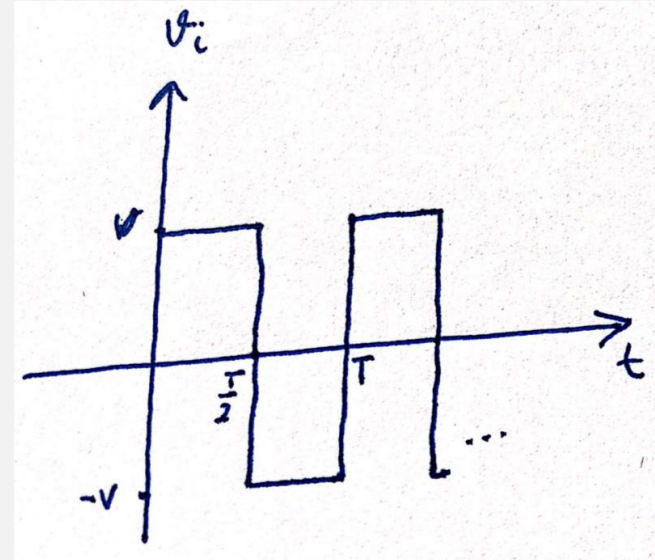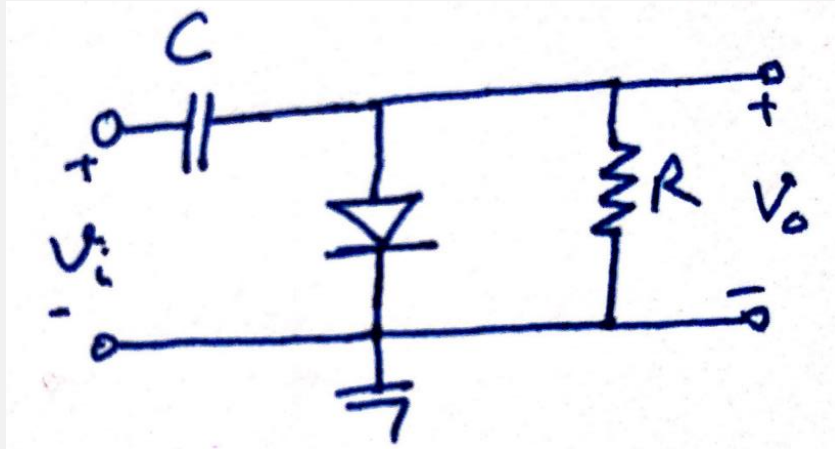



A **diode** and **capacitor** can be combined to “**clamp**” an AC signal to a specific DC level.

Biased Clamper Circuits

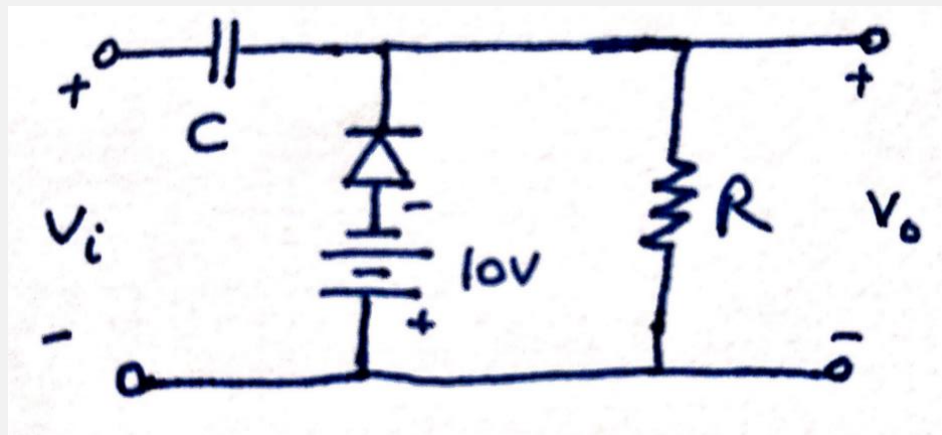The input signal can be any type of waveform such as a sine, square, or triangle wave.



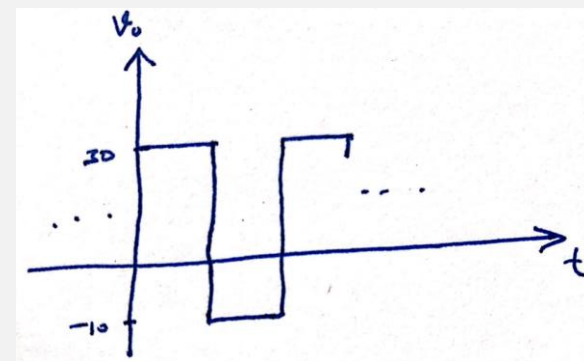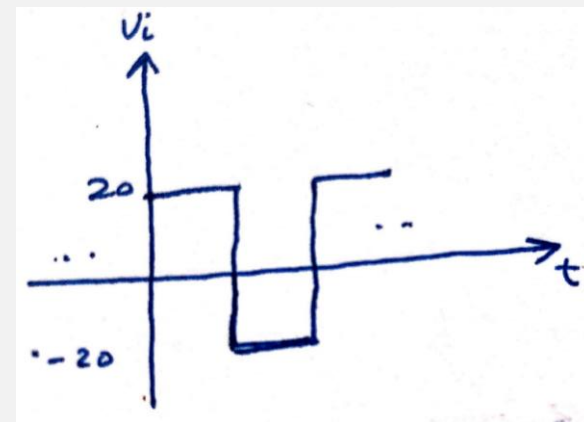The DC source lets you adjust the DC clamping level.



Zener Diodes



The Zener is a diode that is operated in reverse bias at the **Zener Voltage** (V_Z).

When $V_i \geq V_Z$

- The Zener is on
- Voltage across the Zener is V_Z
- Zener current: $I_Z = I_R - I_{RL}$
- The Zener Power: $P_Z = V_Z I_Z$

When $V_i < V_Z$

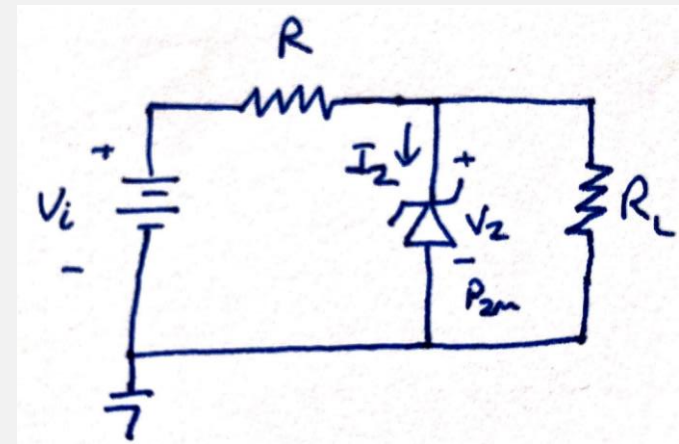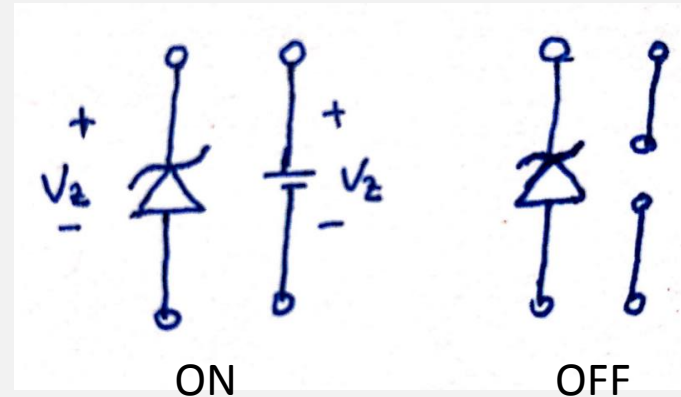- The Zener is off
- The Zener acts as an open circuit




Zener Diodes

If R is too large, the Zener diode cannot conduct because $I_Z < I_{ZK}$. The minimum current is given by:

$$I_{Lmin} = I_R - I_{ZK}$$

The *maximum* value of resistance is:

$$R_{Lmax} = \frac{V_Z}{I_{Lmin}}$$

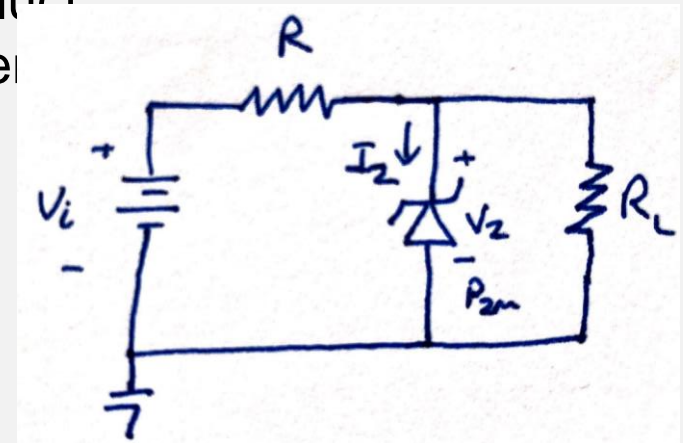

If R is too small, $I_Z > I_{ZM}$. The maximum allowable current for the circuit is given by:

$$I_{Lmax} = \frac{V_L}{R_L} = \frac{V_Z}{R_{Lmin}}$$

The *minimum* value of resistance is:

$$R_{Lmin} = \frac{RV_Z}{V_i - V_Z}$$

Voltage-Multiplier Circuits


Voltage multiplier circuits use a combination of **diodes** and **capacitors** to step up the output voltage of rectifier circuits. Three common voltage multipliers are the:

Voltage Doubler

Voltage Tripler

Voltage Quadrupler

Voltage Doubler

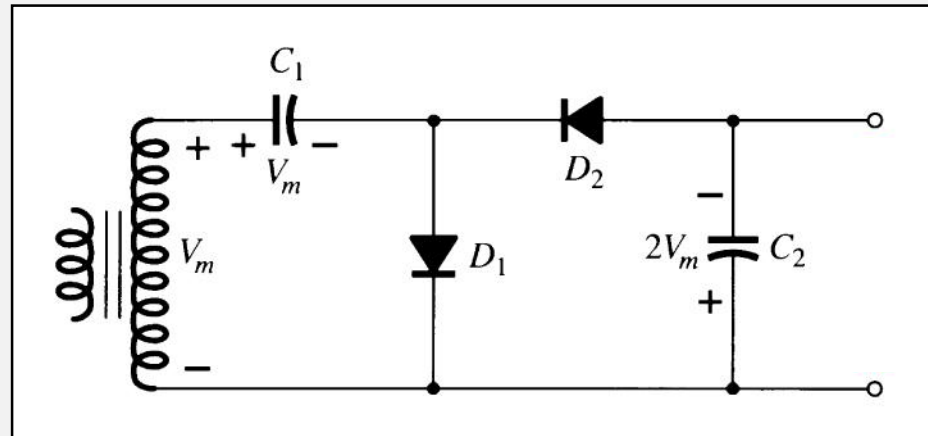

This half-wave voltage doubler's output can be calculated using:

$$V_{out} = V_{C2} = 2V_m$$

where V_m = peak secondary voltage of the transformer

Voltage Doubler

Positive Half-Cycle

D_1 conducts
 D_2 is switched off
Capacitor C_1 charges to V_m

Negative Half-Cycle

D_1 is switched off
 D_2 conducts
Capacitor C_2 charges to V_m

$$V_{\text{out}} = V_{C_2} = 2V_m$$

Practical Applications

Rectifier Circuits

Conversions of AC to DC for DC operated circuits
Battery Charging Circuits

Simple Diode Circuits

Protective Circuits against overcurrent
Polarity Reversal
Currents caused by an inductive kick in a relay circuit

Zener Circuits

Overvoltage Protection
Setting Reference Voltages