



# BME 202 Electronics

## Lecture 4: Bipolar Junction Transistors

# Outline

---



- Basic construction and operation of BJT transistors
- Proper biasing
- Characteristics of *npn* and *pnp* transistors
- Testing a transistor and identifying terminals

# Transistor Construction

---



There are two types of

**B**ipolar **J**unction **T**ransistors:

*pnp* and *npn*

The terminals are labeled:

**E - Emitter**


**B - Base**

**C - Collector**
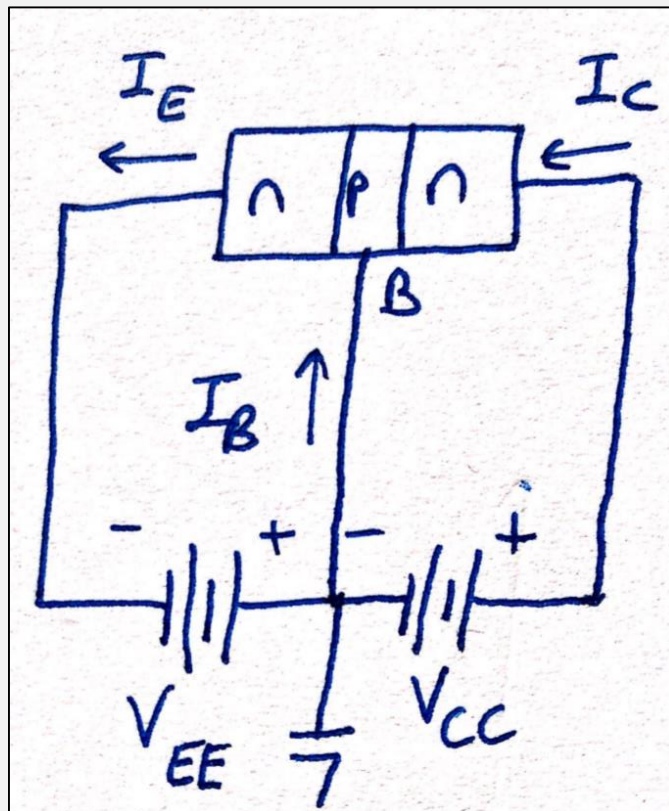
# Transistor Operation

With the external sources,  $V_{EE}$  and  $V_{CC}$ , connected as shown:

*One p-n junction of a transistor is reverse-biased whereas the other is forward biased.*



The **emitter-base** junction is forward biased

The **base-collector** junction is reverse biased

$$I_E = I_C + I_B$$


# Currents in a Transistor

The **emitter current** is the sum of the collector and base currents:

$$I_E = I_C + I_B$$



The **collector current** is comprised of two currents:
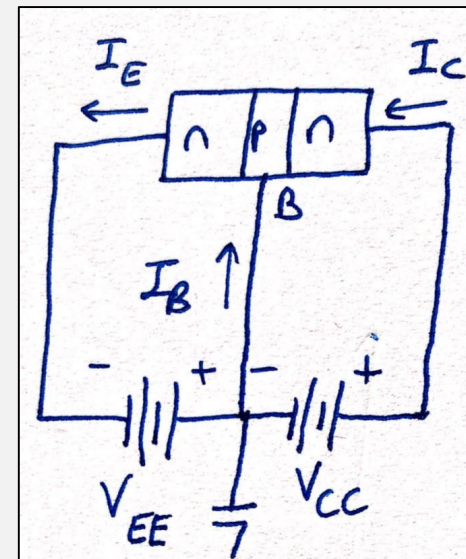
$$I_C = I_C(\text{majority}) + I_{CO}(\text{minority})$$





# Common-Base Configuration

NPN

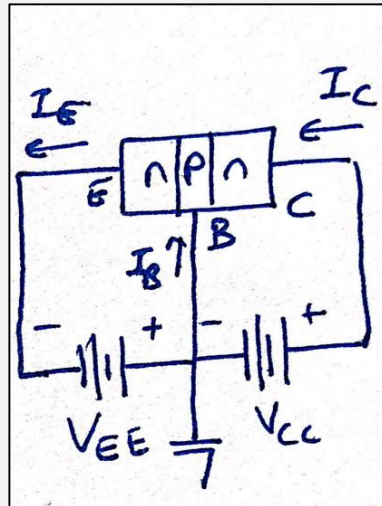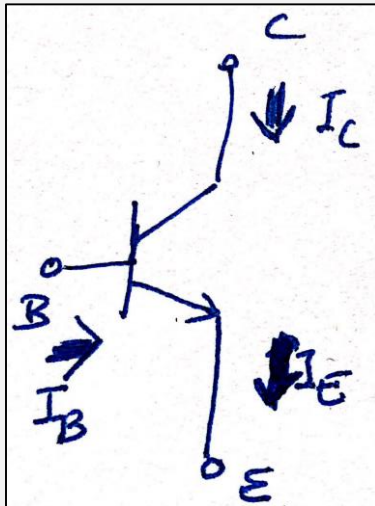

PNP

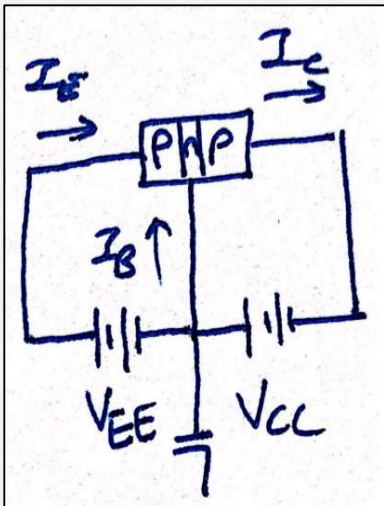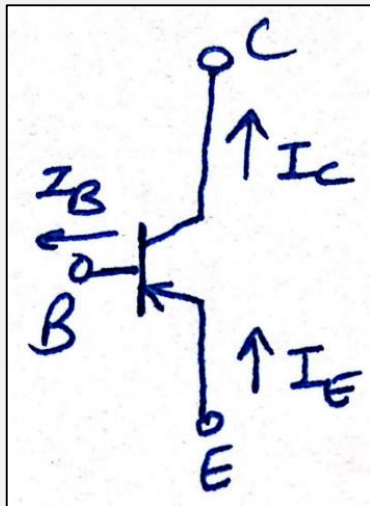

The base is common to both input (emitter–base) junction and output (collector–base) junction of the transistor.


*The arrow in the graphic symbol defines the direction of emitter current through the device*

# Common-Base Amplifier

Two sets of characteristics are required to describe a three terminal device: one for the *driving point or input* parameters and the other for the *output* side.
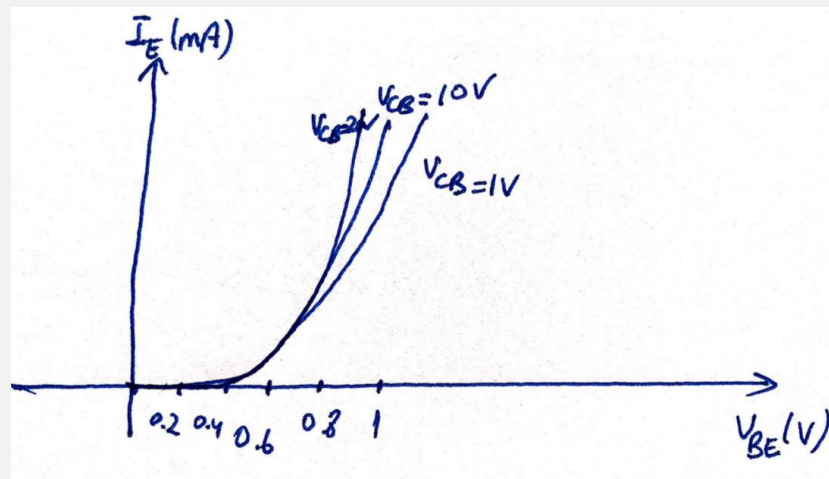
## Input Characteristics


This curve shows the relationship between of input current ( $I_E$ ) to input voltage ( $V_{BE}$ ) for three output voltage ( $V_{CB}$ ) levels.



# Common-Base Amplifier
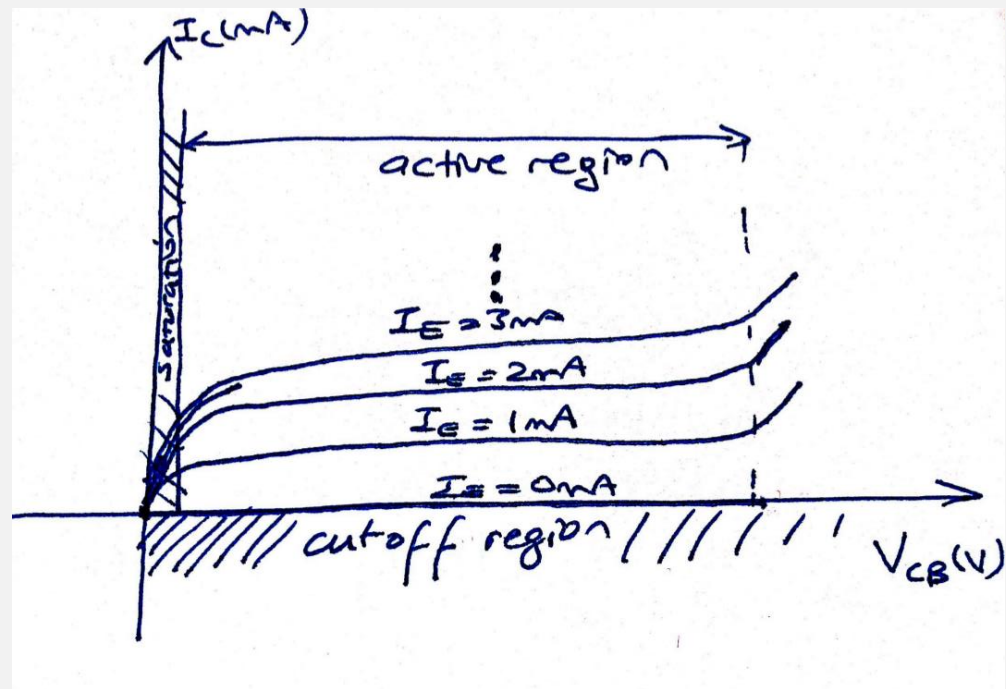
## Output Characteristics

This graph demonstrates the output current ( $I_C$ ) to an output voltage ( $V_{CB}$ ) for various levels of input current ( $I_E$ ).




The output or collector set of characteristics has three basic regions of interest: *active*, *cutoff* and *saturation*.



# Operating Regions
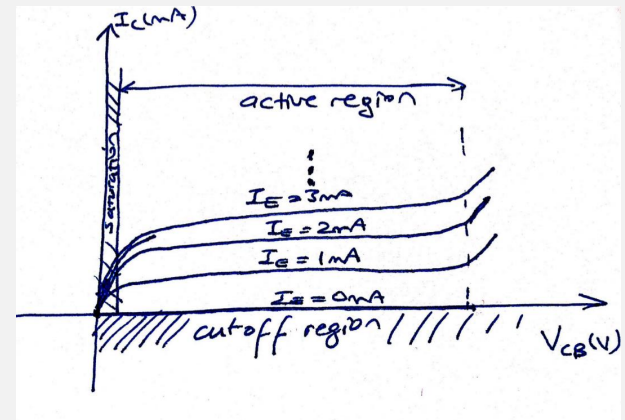
## Active:

- Operating range of the amplifier.
- Base-emitter junction is forward-biased whereas the collector base junction is reverse-biased.
- $I_C \cong I_E$



## Cutoff:

- The amplifier is basically off. There is voltage, but little current.
- Base-emitter and collector-base junctions are both reverse biased.

## Saturation:

- The amplifier is fully on. There is current, but little voltage.
- Base-emitter and collector-base junctions are both forward biased.

# Approximations

---

*Emitter and collector currents*: a first approximation to the relationship between  $I_E$  and  $I_C$

$$I_C \cong I_E$$

*Base-emitter voltage*: once a transistor is in the on state, the base-to-emitter voltage will be assumed

$$V_{BE} \cong 0.7V$$

*(for Silicon)*

# Alpha ( $\alpha$ )

---

**DC mode:** levels of  $I_E$  and  $I_C$  due to majority carriers are related by a quantity called alpha:

$$\alpha_{\text{dc}} = \frac{I_C}{I_E}$$

Ideally:  $\alpha = 1$

In reality:  $\alpha$  falls somewhere between  
0.9 and 0.998

**AC mode:** for ac situation where the point of operation moves on the characteristic curve, an average ac alpha is defined by:

$$\alpha_{\text{ac}} = \frac{\Delta I_C}{\Delta I_E}$$

# Common-Emitter Configuration

---

The emitter is common to both **input** (base-emitter) and **output** (collector-emitter) circuits.

The input is applied to the base and the output is taken from the collector.

# Common-Emitter Amplifier Currents

## Ideal Currents

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E$$

## Actual Currents

$$I_C = \alpha I_E + I_{CBO}$$

where  $I_{CBO}$  = minority collector current

$I_{CBO}$  is usually so small that it can be ignored, except in high power transistors and in high temperature environments.

When  $I_B = 0 \mu\text{A}$  the transistor is in cutoff, but there is some minority current flowing called  $I_{CEO}$ .

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \Big|_{I_B = 0 \mu\text{A}}$$

# Beta ( $\beta$ )

---

$\beta$  represents the amplification factor of a transistor.

*In DC mode:*

$$\beta_{dc} = \frac{I_C}{I_B}$$

*In AC mode:*

$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE}=\text{constant}}$$

$\beta_{ac}$  is sometimes referred to as  $h_{fe}$ , a term used in transistor modeling calculations

# Beta ( $\beta$ )



## Determining $\beta$ from a graph

$$\begin{aligned}\beta_{AC} &= \frac{(3.2 \text{ mA} - 2.2 \text{ mA})}{(30 \text{ }\mu\text{A} - 20 \text{ }\mu\text{A})} \\ &= \frac{1 \text{ mA}}{10 \text{ }\mu\text{A}} \Big|_{V_{CE}=7.5 \text{ V}} \\ &= 100\end{aligned}$$

$$\begin{aligned}\beta_{DC} &= \frac{2.7 \text{ mA}}{25 \text{ }\mu\text{A}} \Big|_{V_{CE}=7.5 \text{ V}} \\ &= 108\end{aligned}$$

# Beta ( $\beta$ )

---



Relationship between **amplification factors**  $\beta$  and  $\alpha$  :

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{\alpha - 1}$$

Relationship between **Currents**:

$$I_C = \beta I_B$$

$$I_E = (\beta + 1) I_B$$





# Common-Collector Configuration

---

The input is on the base and the output is on the emitter.

Primarily used for *impedance matching* purposes.

# Common-Collector Configuration

---

The characteristics are similar to those of the common-emitter amplifier, except the vertical axis is  $I_E$ .

# Operating Limits

---



$V_{CE}$  is maximum and  $I_C$  is minimum in the **cutoff region**.

$$I_{C(\max)} = I_{CEO}$$

$I_C$  is maximum and  $V_{CE}$  is minimum in the **saturation region**.

$$V_{CE(\max)} = V_{CE(\text{sat})} = V_{CEO}$$

The transistor operates in the **active region** between saturation and cutoff.

# Power Dissipation

---

Common-base:

$$P_{Cmax} = V_{CB} I_C$$

Common-emitter:

$$P_{Cmax} = V_{CE} I_C$$

Common-collector:

$$P_{Cmax} = V_{CE} I_E$$

# Transistor Specification Sheet



## MAXIMUM RATINGS

Rating	Symbol	2N4123	Unit
Collector-Emitter Voltage	$V_{CEO}$	30	Vdc
Collector-Base Voltage	$V_{CBO}$	40	Vdc
Emitter-Base Voltage	$V_{EBO}$	5.0	Vdc
Collector Current – Continuous	$I_C$	200	mAdc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above $25^\circ\text{C}$	$P_D$	625 5.0	mW mW $^\circ\text{C}$
Operating and Storage Junction Temperature Range	$T_j, T_{stg}$	-55 to +150	$^\circ\text{C}$

## THERMAL CHARACTERISTICS

Characteristic	Symbol	Max	Unit
Thermal Resistance, Junction to Case	$R_{\theta JC}$	83.3	$^\circ\text{C W}$
Thermal Resistance, Junction to Ambient	$R_{\theta JA}$	200	$^\circ\text{C W}$



# Transistor Testing

---



**Curve Tracer** Provides a graph of the characteristic curves.

**DMM** Some DMMs measure  $\beta_{DC}$  or  $h_{FE}$ .

**Ohmmeter**