
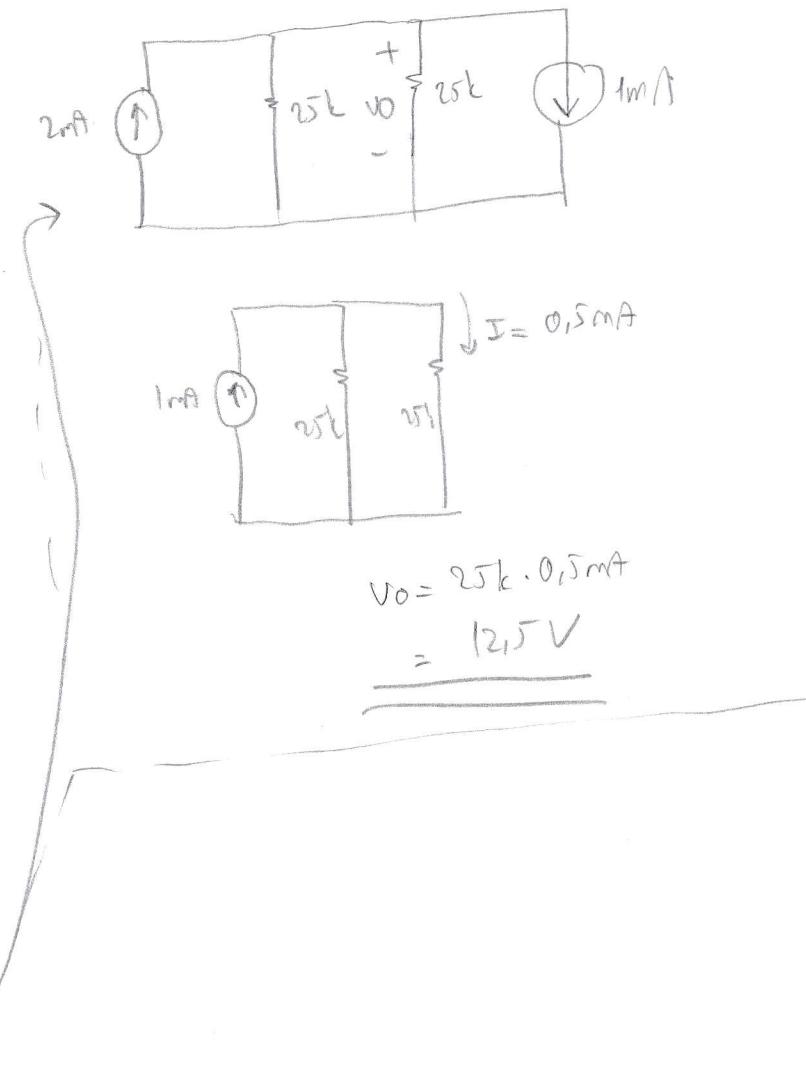
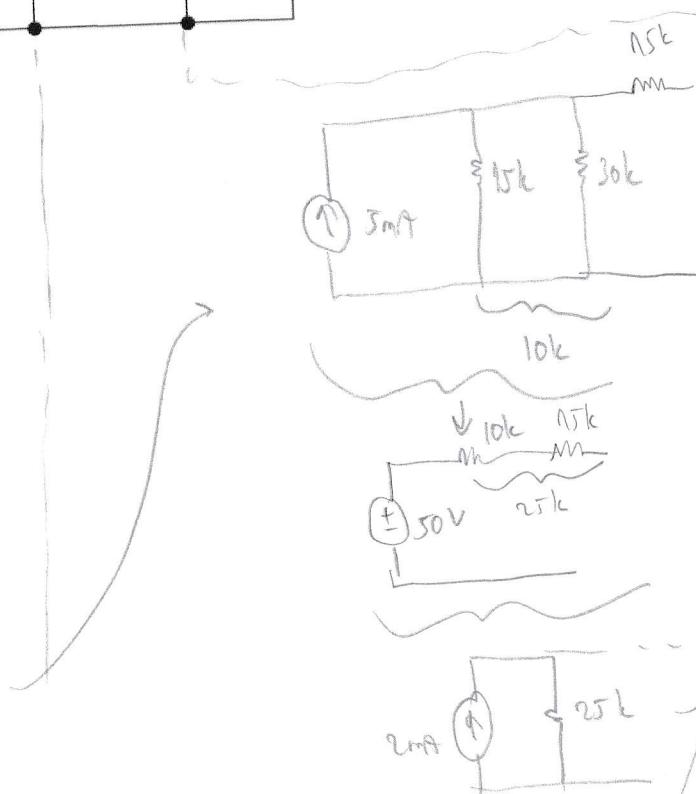
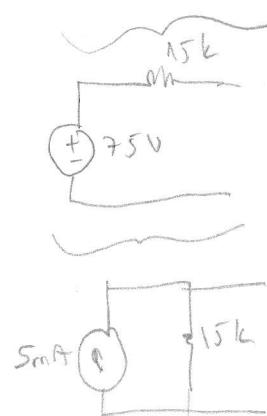


- 4.59 a) Make a series of source transformations to find the voltage v_0 in the circuit in Fig. P4.59.
 b) Verify your solution using the mesh-current method.


Figure P4.59

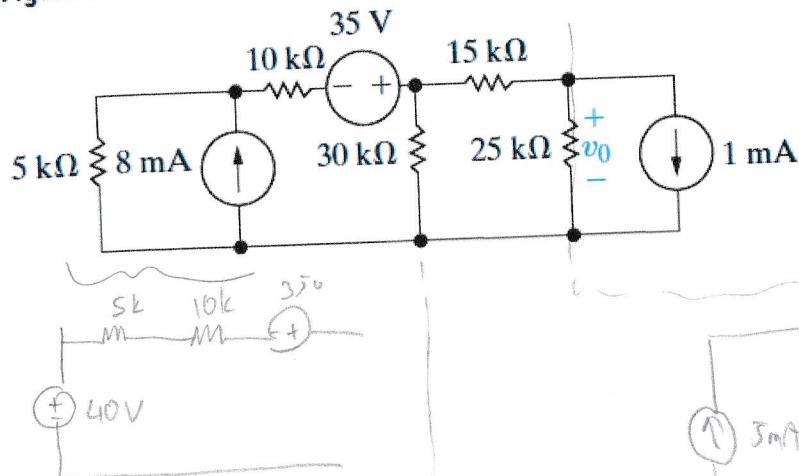

- 4.22** a) Use the node-voltage method to find v_o and the power delivered by the 2 A current source in the circuit in Fig. P4.22. Use node a as the reference node.
- b) Repeat part (a), but use node b as the reference node.
- c) Compare the choice of reference node in (a) and (b). Which is better, and why?

PSPICE
MULTISIM

Figure P4.22

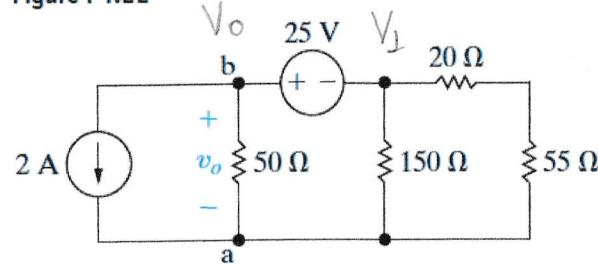

$$-v_o + 25 + v_1 = 0$$

$$\underline{v_o = v_1 + 25}$$

$$v_1 = \frac{v_o - 25}{55}$$

Supernode

$$2 + \frac{v_o}{50} + \frac{v_1}{150} + \frac{v_1}{75} = 0$$

$$3v_o + v_1 + 4v_1 = -300$$

$$3v_o + 5v_1 = -300$$


$$3v_o + 5v_1 - 125 = -300$$

$$8v_o = -175$$

$$\underline{\underline{v_o = -21.875 V}}$$

- 4.13** Use the node-voltage method to find v_1 and v_2 in the circuit shown in Fig. P4.13.

Figure P4.13

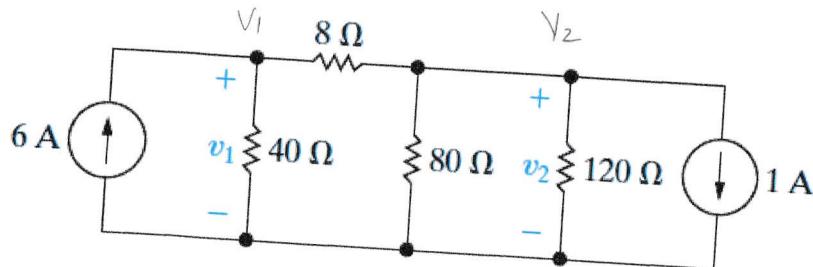

$$-6 + \frac{V_1}{40} + \frac{V_1 - V_2}{8} = 0$$

$$1 + \frac{V_2}{120} + \frac{V_2 - V_1}{80} = 0$$

$$V_1 + 5V_1 - 5V_2 = 240$$

$$6V_1 - 5V_2 = 240$$

$$2V_2 + 3V_2 + 30V_2 - 30V_1 = -240$$

$$-30V_1 + 35V_2 = -240$$

$$6V_1 - 5V_2 = 30V_1 - 35V_2$$

$$30V_2 = 24V_1$$

$$5V_2 = 4V_1$$

$$5V_2 = 4.120$$

$$V_2 = 96 V$$

$$6V_1 - 4V_1 = 240$$


$$2V_1 = 240$$

$$\underline{\underline{V_1 = 120}}$$

- 4.61** a) Use source transformations to find the current i_o in the circuit in Fig. P4.61.
- b) Verify your solution by using the node-voltage method to find i_o .

PSPIKE
MULTISIM

Figure P4.61

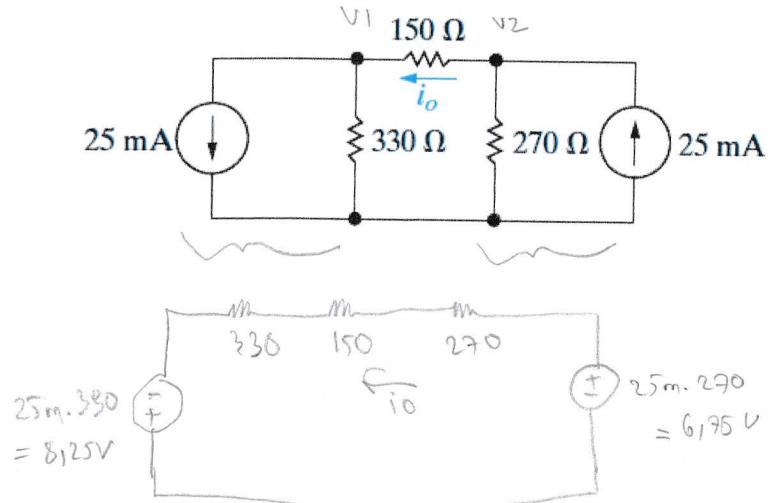

$$i_o = \frac{6,75 + 8,25}{750} = 0,02 \text{ A}$$

$$\underline{i_o = +2 \text{ mA}}$$

$$\begin{aligned} 25m + \frac{V_1}{330} + \frac{V_1 - V_2}{150} &= 0 & -25m + \frac{V_2}{270} + \frac{V_2 - V_1}{150} &= 0 \\ 150V_1 + 330V_1 - 330V_2 &= -1237,5 & 150V_2 + 270V_2 - 270V_1 &= 1012,5 \\ 480V_1 - 330V_2 &= -1237,5 & -270V_1 + 420V_2 &= 1012,5 \end{aligned}$$

$$\begin{aligned} 420V_2 &= 480V_1 - 330V_2 = -1237,5 \\ -270V_1 &+ 420V_2 = 1012,5 \\ 20160V_1 - 13860V_2 &= -51975 \\ -8910V_1 + 13860V_2 &= 33412,5 \\ \hline 11250V_1 &= -18562,5 \\ V_1 &= -1,65 \end{aligned}$$

$$480 \cdot (-1,65) - 330V_2 = -1237,5$$

$$-330V_2 = -445,5$$

$$\underline{V_2 = +1,35}$$

$$\begin{aligned} i_o &= \frac{V_2 - V_1}{150} = \frac{1,35 - (-1,65)}{150} = \frac{3}{150} = 0,02 \text{ A} \\ &= \underline{2 \text{ mA}} \end{aligned}$$