



BME 212 Electronics Laboratory

Experiment #3 Examination of BJT Characteristics



Objective





The objective of this experiment is to study the characteristic of a BJT transistor.





Preliminary Work

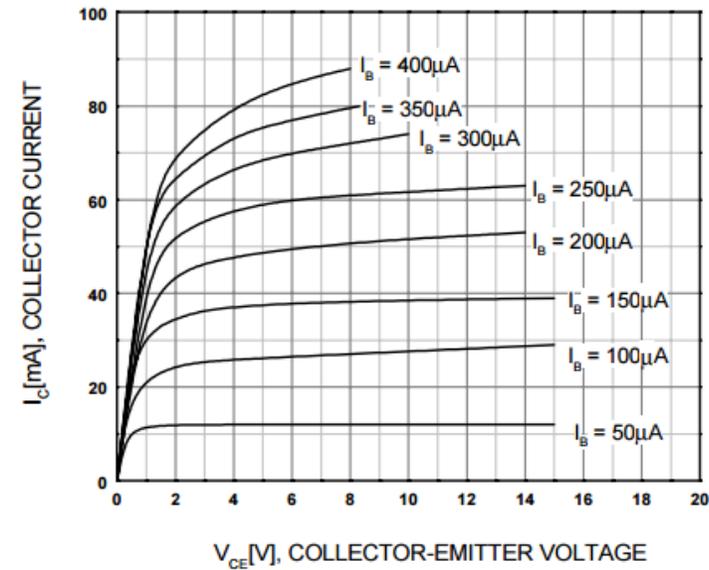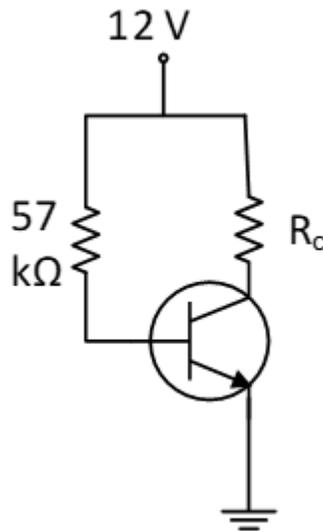1- Find the minimum R_c value for safe operation of transistor in active region if $P_{max} = 500 \text{ mW}$.



Preliminary Work (Cont.)

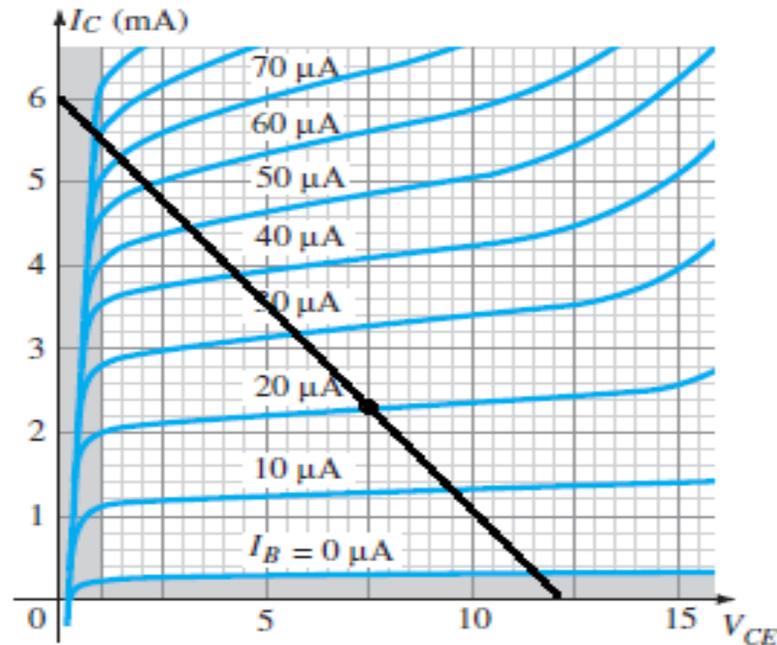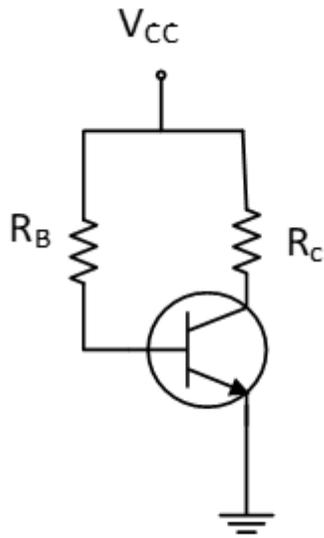2- Find V_{CC} , R_B and R_C to achieve the Q point given in the figure and calculate the β value of the transistor.





Procedure

Warning: Before starting the experiment, adjust the P_1 and P_2 potentiometers to maximum value and then decrease to have given I_B currents in a. and b.

1) For given circuit below,

a) Adjust the P_1 (100 k Ω) potentiometer value to have $I_B = 50$ μ A.


Adjust the P_2 (10 k Ω) potentiometer value for each V_{CE} voltage shown in table and measure the corresponding I_C values.

V_{CE} (V)	0.5	1	2	4	6	8	10	12
--------------	-----	---	---	---	---	---	----	----

b) Adjust the P_1 potentiometer value to have $I_B = 100$ μ A.

Adjust the P_2 potentiometer value for each V_{CE} voltage shown in table and measure the corresponding I_C values.


V_{CE} (V)	0.5	1	2	4	6	8	10	12
--------------	-----	---	---	---	---	---	----	----

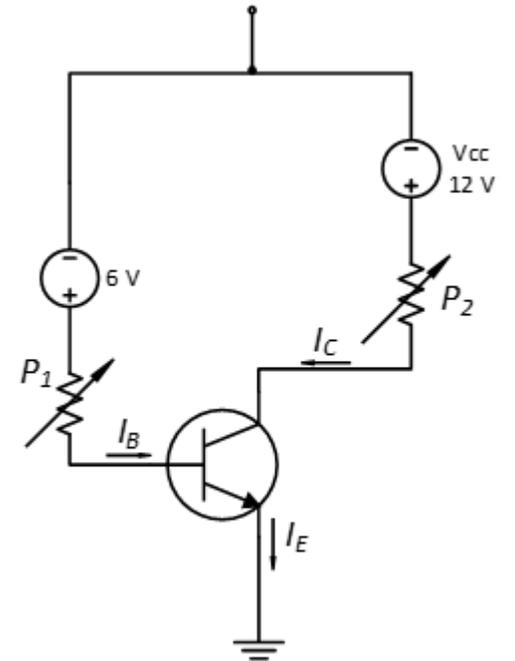



Procedure (Cont.)

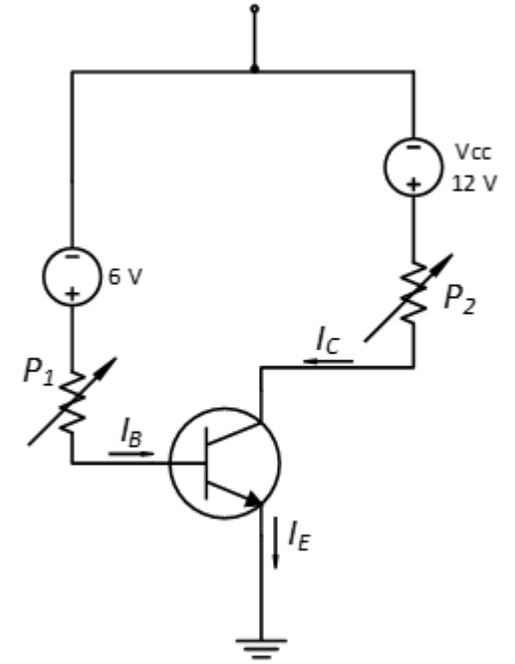c) Using measurements in steps a and b plot the $I_C - V_{CE}$ characteristic (Indicate I_B on the graph).





BME212 Report#3

Results



1) a) Obtaining I_C values when $I_B = 50 \mu\text{A}$ for following V_{CE} values.

V_{CE} (V)	0.5	1	2	4	6	8	10
I_C							


b) Obtaining I_C values when $I_B = 220 \mu\text{A}$ for following V_{CE} values.

V_{CE} (V)	0.5	1	2	4	6	8	10
I_C							



BME212 Report#2 Results (Cont.)

c) Plot transistor characteristics

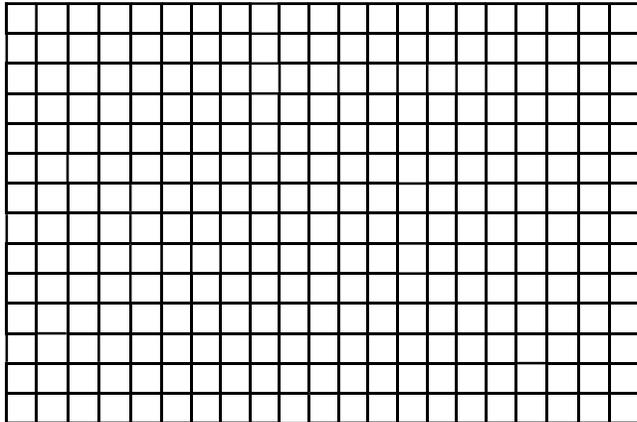

Comment: