



# BME 212 Electronics Laboratory

**Experiment #6 Transfer Characteristics of FET and DC**




# Objective



The objective of this experiment is understanding the characteristics of the FET and to become familiar in the use of load-line analysis to examine FET networks.
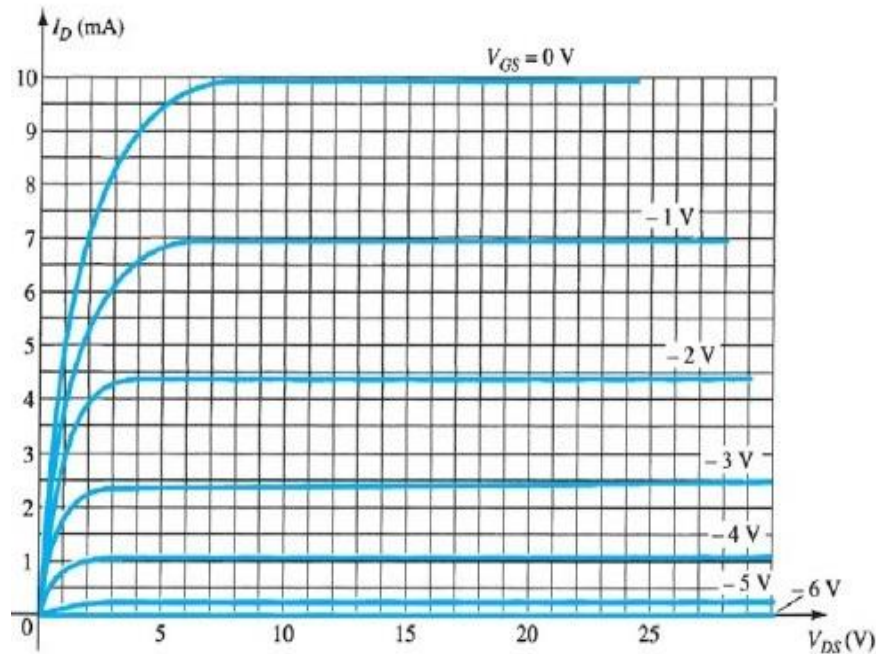
# Preliminary Work

1- Using figure given below determine the values of  $I_{DSS}$  and  $V_P$ , plot the transfer characteristics using Shockley's equation.



The level of  $V_{GS}$  that results in  $I_D = 0$  mA is defined by  $V_{GS} = V_P$ , with  $V_P$  being a negative voltage for n-channel devices and a positive voltage for p-channel JFETs.

## Shockley's Equation

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

↑ constants
↑ control variable

# Preliminary Work (Cont.)

2) For given circuit below using given biasing conditions calculate the  $V_{GSQ}$ ,  $I_{DQ}$ ,  $V_{DS}$ ,  $V_D$ ,  $V_G$ , and  $V_S$ .


Plot the transfer characteristic (Shockley curve) of the circuit and repeat the step a.

Hints:

$$V_{GSQ} = -V_{GG}$$

$$I_{DQ} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{DS} = V_{DD} - I_D R_D$$

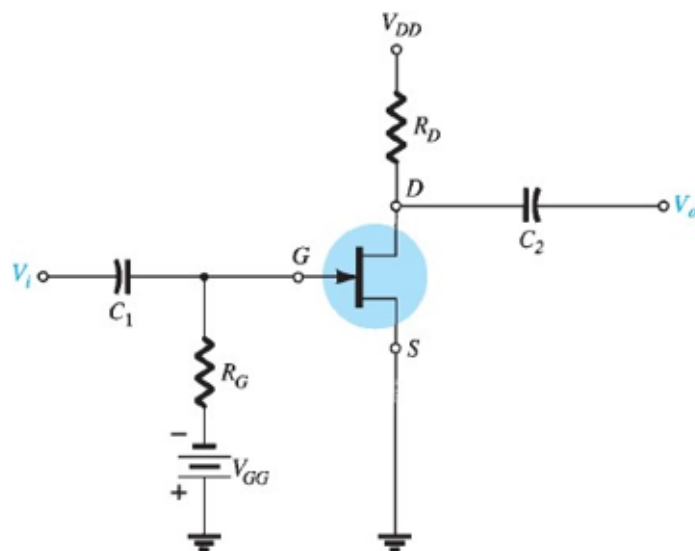


$$V_{DD} = 12 \text{ V}, V_{GG} = -1.5 \text{ V}$$

$$R_D = 1 \text{ k}\Omega, R_G = 470 \text{ k}\Omega$$

$$I_{DSS} = 10 \text{ mA}, V_P = -4 \text{ V}$$

# Preliminary Work (Cont.)

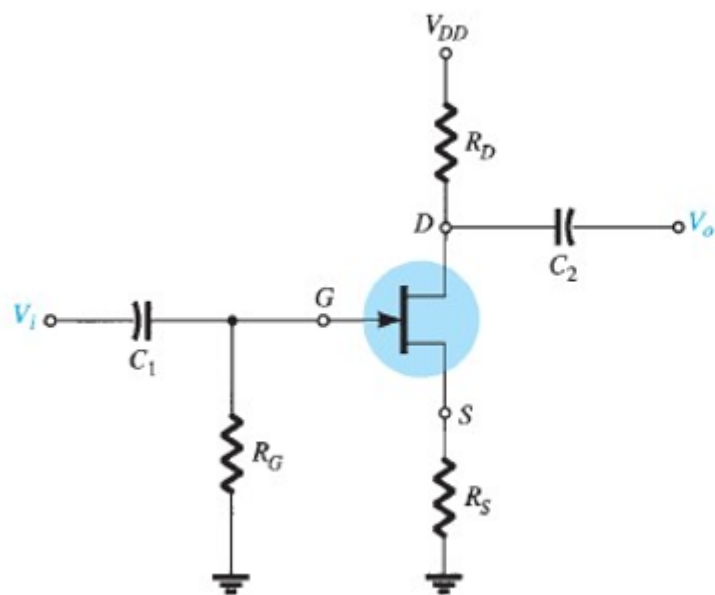3) For given circuit below using given biasing conditions, determine the Q point and calculate the  $V_{GSQ}$ ,  $I_{DQ}$ ,  $V_{DS}$ ,  $V_D$ ,  $V_G$ , and  $V_S$



$$V_{DD} = 15 \text{ V}$$

$$R_D = 3.3 \text{ k}\Omega, R_G = 1 \text{ M}\Omega, R_S = 2 \text{ k}\Omega$$

$$I_{DSS} = 8 \text{ mA}, V_P = -6 \text{ V}$$

Hints:  $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$

$$V_{GS} = -I_D R_S$$

$$I_D = \frac{I_{DSS}}{2}$$


$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

$$V_{GS} = -I_D R_S = -\frac{I_{DSS} R_S}{2}$$

$$V_S = I_D R_S$$

$$V_G = 0 \text{ V}$$
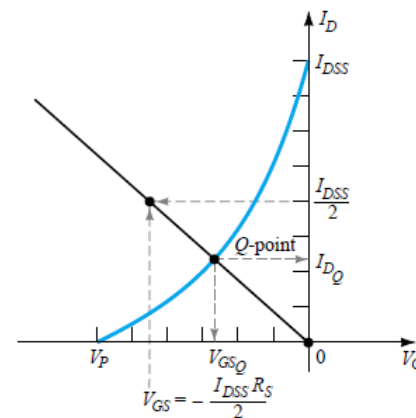
$$V_D = V_{DS} + V_S = V_{DD} - V_{R_D}$$



# Preliminary Work (Cont.)

4) For given circuit below using given biasing conditions,

a) Determine the Q point and calculate the  $V_{GSQ}$ ,  $I_{DQ}$ ,  $V_{DS}$ ,  $V_D$ ,  $V_G$ , and  $V_S$ .

b) If,  $R_S = 560 \Omega$  repeat the step a.

Hints:

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$I_D = \frac{V_G}{R_S} \Big|_{V_{GS} = 0 \text{ V}}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_{GS} = V_G \Big|_{I_D = 0 \text{ mA}}$$




$$V_D = V_{DD} - I_D R_D$$

$$V_S = I_D R_S$$

$$V_{DD} = 15 \text{ V},$$

$$R_D = 2.2 \text{ k}\Omega, R_S = 1.5 \text{ k}\Omega, R_1 = 2 \text{ M}\Omega, R_2 = 270 \text{ k}\Omega,$$
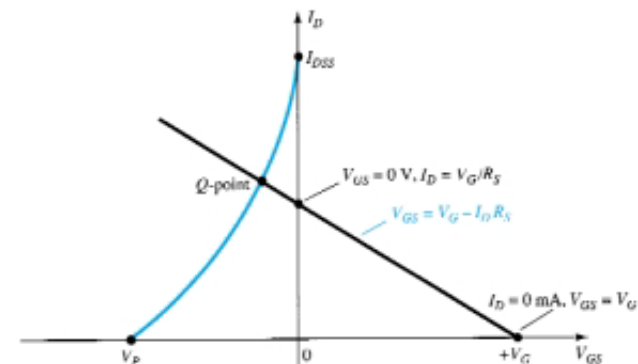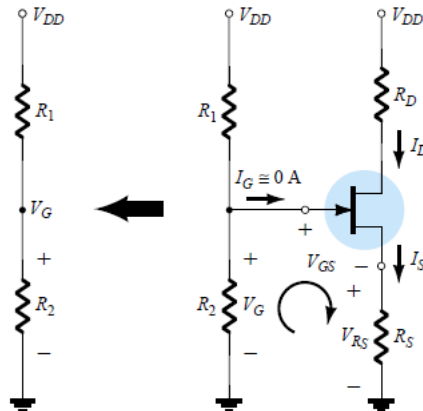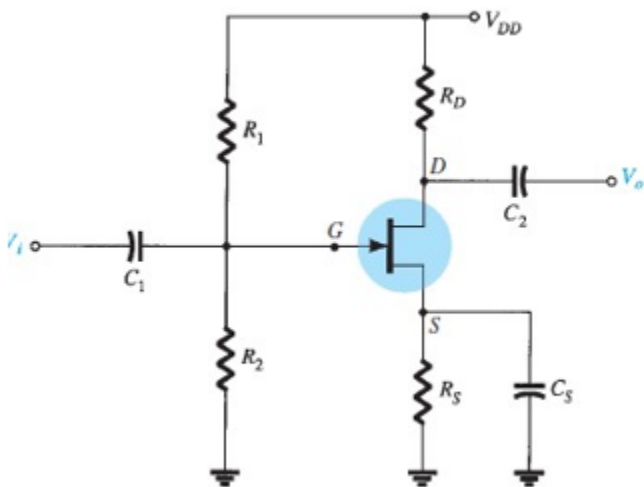
$$I_{DSS} = 8 \text{ mA}, V_P = -5 \text{ V}$$




# Procedure



1) For given circuit below

a) Adjust the  $V_{GG}$  voltage to have following  $V_{GS}$  values and measure the corresponding  $I_D$  current value.

$V_{GS}$ (V)	0.0	-0.1	-0.2	-0.4	-0.6	-0.8	-1.0
$I_D$ (mA)							

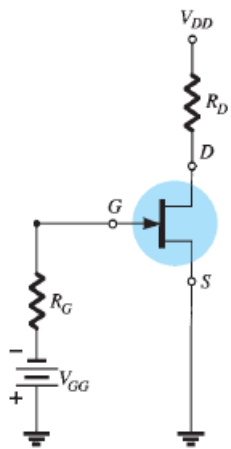

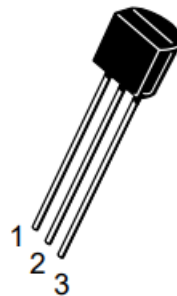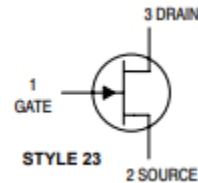$V_{DD} = 12\text{ V}$   
 $R_D = 1\text{ k}\Omega$ ,  $R_G = 560\text{ k}\Omega$





# Procedure

b) Adjust the  $V_{GG}$  value to have  $V_{GS} = -0.1$  V. Adjust the  $V_{DD}$  voltage value to have  $V_{DS}$  voltage shown in table and measure the corresponding  $I_D$  values.

$V_{DS}$ (V)	1.0	3.0	6.0	8.0	10.0
$I_D$ (mA)					

c) Adjust the  $V_{GG}$  value to have  $V_{GS} = -0.2$  V. Adjust the  $V_{DD}$  voltage value to have  $V_{DS}$  voltage shown in table and measure the corresponding  $I_D$  values.

$V_{DS}$ (V)	1.0	3.0	6.0	8.0	10.0
$I_D$ (mA)					





# Procedure

d) Using measurements in step a plot the  $I_D - V_{GS}$  characteristic , using measurements in steps b and c plot the  $I_D - V_{DS}$  characteristic.

e) As  $V_{GS} = -0.15$  V calculate the  $I_D$  point from the  $I_D - V_{GS}$  characteristic, measure the  $I_{DQ}$  and  $V_{GSQ}$  and compare the results.



# BME212 Report#6

## Results

1) a) Obtaining  $I_D$  values.

$V_{GS}$ (V)	0.0	-0.1	-0.2	-0.4	-0.6	-0.8	-1.0
$I_D$ (mA)							

b) Obtaining  $I_D$  values for  $V_{GS} = -0.1$  V.


$V_{DS}$ (V)	1.0	3.0	6.0	8.0	10.0
$I_D$ (mA)					

c) Obtaining  $I_D$  values for  $V_{GS} = -0.4$  V.


$V_{DS}$ (V)	1.0	3.0	6.0	8.0	10.0
$I_D$ (mA)					

d) Plot characteristics

$I_D - V_{GS}$  characteristic

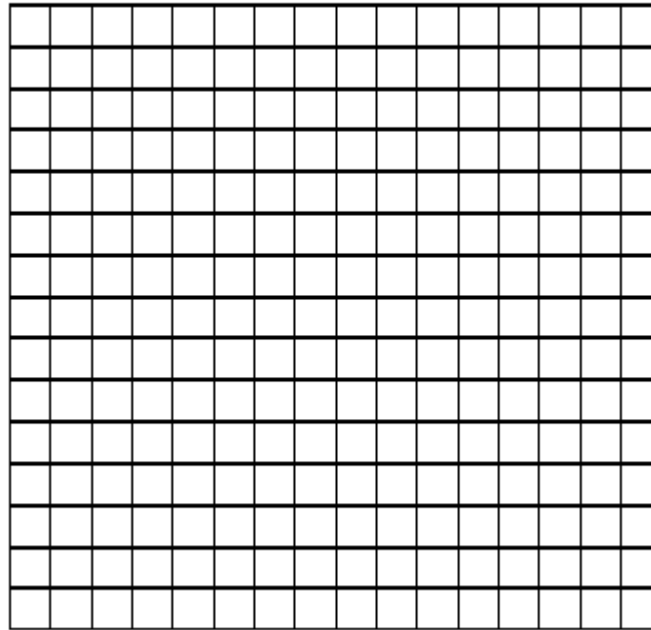

$I_D - V_{DS}$  characteristic

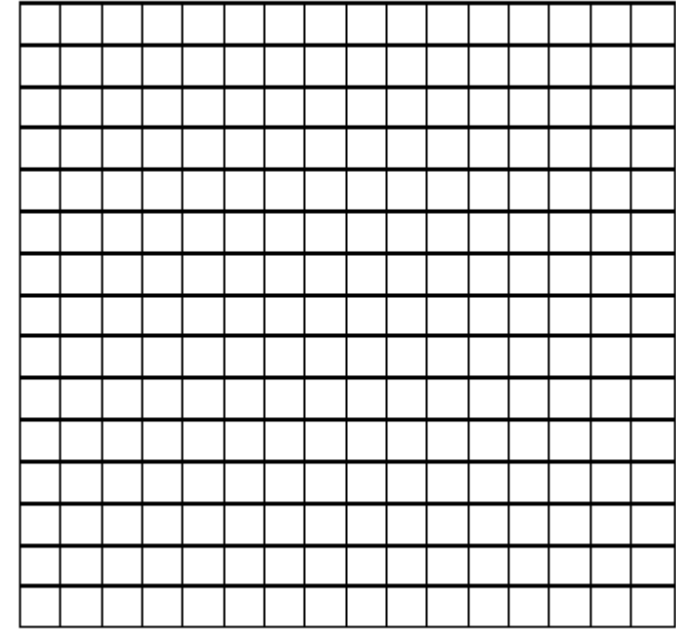



# BME212 Report#6 Results (Cont.)



e) Obtaining  $I_{DQ}$  and  $V_{GSQ}$  values

	$I_{DQ}$	$V_{GSQ}$
Calculated		
Measured		

**Comment:**