



BME 212 Electronics Laboratory

Experiment #7 OPAMP Characteristics and Basic OPAMP Circuits



Objective



The objective of this experiment is understanding opamp characteristics and applications of inverting, non-inverting and unity-follower circuits.

Preliminary Work

- 1-) Derive the output voltage expression given in background information of the the inverting, non-inverting and unity-follower circuits.
- 2-) Design an amplifier using an inverting and a non-inverting circuit with Voltage Gain (A_{CL}) = -100 (10x-10). Then, draw your final circuit diagram. To implement the circuit, design it using close nominal resistor values from your component list.



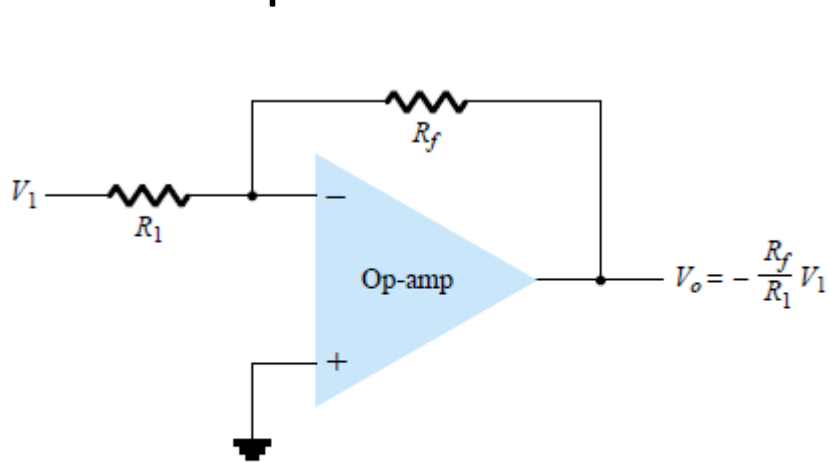


Figure 14.15 Inverting constant-gain multiplier.

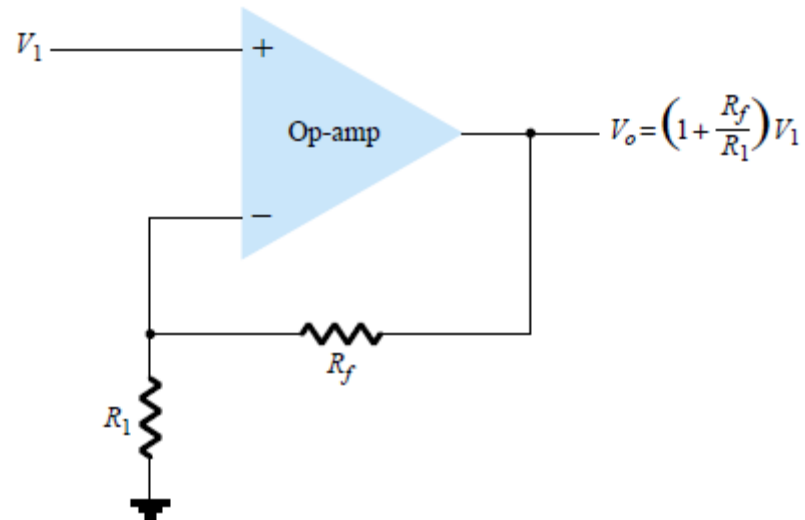

(a)


Figure 14.16 Noninverting constant-gain multiplier.

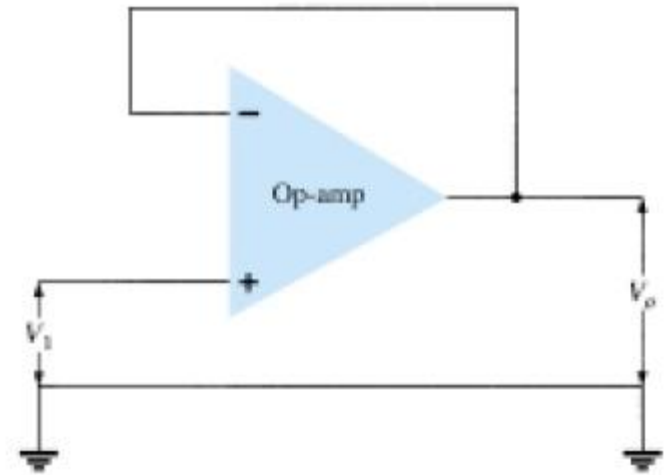


Procedure

1) Set up the circuits a, b, and c given below. For all circuits observe $v_{in}(t)$ and $v_o(t)$ then draw into the graph paper and calculate closed-loop gains (A_{CL}). Also for circuit b plot the V_{out} vs. V_{in} using the X-Y plot function on the oscilloscope and draw the graph into the result paper.

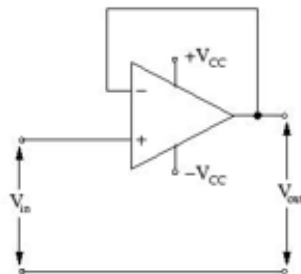
a) $v_{in}(t) = 2 \sin(2000\pi t)$ V
 $V_{CC} = \pm 15V$



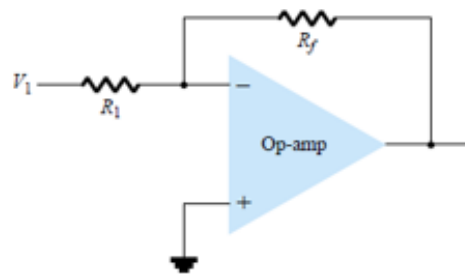b) $v_{in}(t) = 0.1 \sin(2000\pi t)$ V
 $V_{CC} = \pm 15V$
 $R_1 = 1k\Omega, R_f = 100k\Omega$



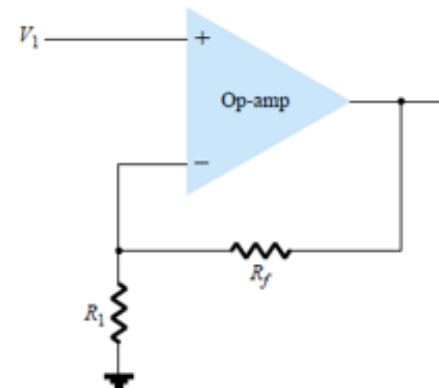c) $v_{in}(t) = 1 \sin(2000\pi t)$ V
 $V_{CC} = \pm 15V$
 $R_1 = 1k\Omega, R_f = 2.2k\Omega$





Procedure (Cont.)

2) Set up your circuit designed in Preliminary Work 2. For 10 mV_{pp} sinusoidal input voltage plot the output voltage of the circuit, calculate the A_{CL} and compare with Preliminary Work 2.

