
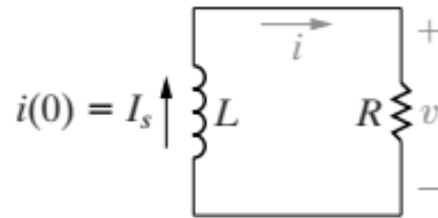


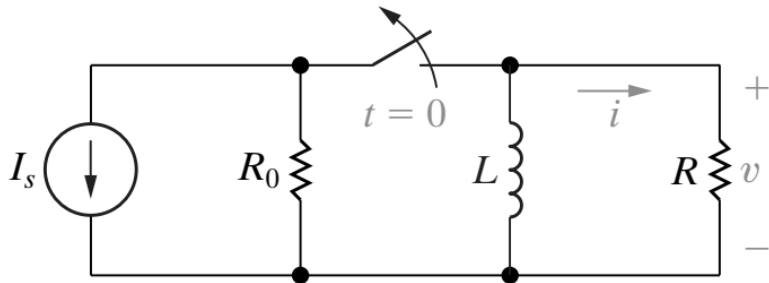RL and RC circuits are also known as **first-order circuits**, because their voltages and currents are described by first-order differential equations



$$L \frac{di}{dt} + Ri = 0,$$


$$\frac{di}{dt} dt = -\frac{R}{L} i dt, \quad \frac{di}{i} = -\frac{R}{L} dt, \quad \int_{i(t_0)}^{i(t)} \frac{dx}{x} = -\frac{R}{L} \int_{t_0}^t dy,$$

$$\ln \frac{i(t)}{i(0)} = -\frac{R}{L} t, \quad i(t) = i(0) e^{-(R/L)t}.$$

Known as a first-order ordinary differential equation, because it contains terms involving the ordinary derivative of the unknown

$$i(0^-) = i(0^+) = I_0,$$
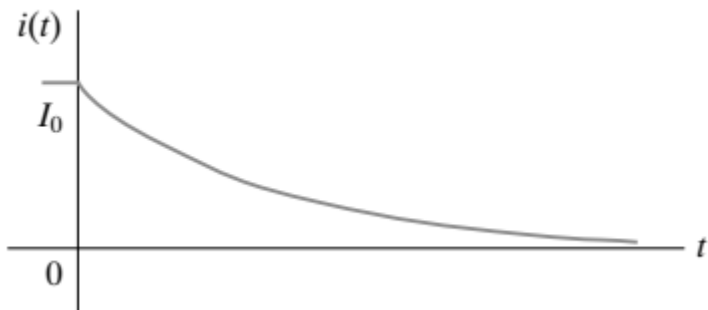
$$i(t) = I_0 e^{-(R/L)t}, \quad t \geq 0,$$



$$v = iR = I_0 R e^{-(R/L)t}, \quad t \geq 0^+.$$

Lets find by using Laplace Transform

$$\begin{aligned}
 w &= \int_0^t p dx = \int_0^t I_0^2 R e^{-2(R/L)x} dx \\
 &= \frac{1}{2(R/L)} I_0^2 R (1 - e^{-2(R/L)t}) \\
 &= \frac{1}{2} L I_0^2 (1 - e^{-2(R/L)t}), \quad t \geq 0.
 \end{aligned}$$

$$p = vi, \quad p = i^2 R, \quad \text{or} \quad p = \frac{v^2}{R}.$$

$$p = I_0^2 R e^{-2(R/L)t}, \quad t \geq 0^+.$$

The Significance of the Time Constant

Determines the rate at which the current or voltage approaches zero. The reciprocal of this ratio is the **time constant** of the circuit, denoted

$$i(t) = I_0 e^{-t/\tau}, \quad t \geq 0,$$


$$v(t) = I_0 R e^{-t/\tau}, \quad t \geq 0^+,$$

$$p = I_0^2 R e^{-2t/\tau}, \quad t \geq 0^+,$$

$$w = \frac{1}{2} L I_0^2 (1 - e^{-2t/\tau}), \quad t \geq 0.$$

$$\tau = \text{time constant} = \frac{L}{R}.$$

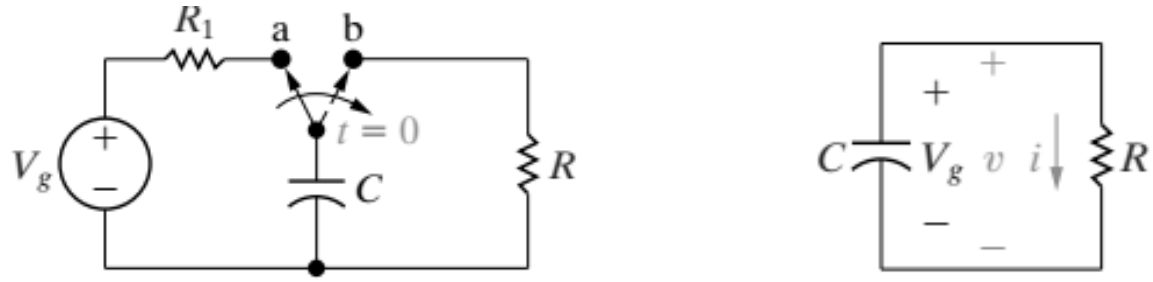The natural response of an RC circuit is developed from the circuit shown in Fig



We begin by assuming that the switch has been in position a for a long time, allowing the loop made up of the dc voltage source the resistor and the capacitor C to reach a steady-state condition.

we will discuss how the capacitor voltage actually builds to the steady-state value of the dc voltage source, but for now the important point is that when the switch is moved from position a to position b (at $t=0$), the voltage on the capacitor is. Because there can be no instantaneous change in the voltage at the terminals of a capacitor, the problem reduces to solving the circuit shown in Fig.

Deriving the Expression for the Voltage

$$C \frac{dv}{dt} + \frac{v}{R} = 0.$$

$$v(t) = v(0)e^{-t/RC}, \quad t \geq 0.$$

$$v(0^-) = v(0) = v(0^+) = V_g = V_0,$$

$$\tau = RC.$$


$$v(t) = V_0 e^{-t/\tau}, \quad t \geq 0,$$

$$i(t) = \frac{v(t)}{R} = \frac{V_0}{R} e^{-t/\tau}, \quad t \geq 0^+,$$

$$p = vi = \frac{V_0^2}{R} e^{-2t/\tau}, \quad t \geq 0^+,$$

$$\begin{aligned} w &= \int_0^t p \, dx = \int_0^t \frac{V_0^2}{R} e^{-2x/\tau} \, dx \\ &= \frac{1}{2} C V_0^2 (1 - e^{-2t/\tau}), \quad t \geq 0. \end{aligned}$$

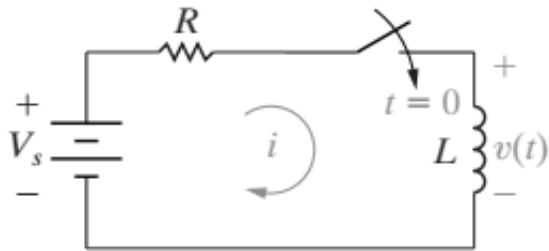We are now ready to discuss the problem of finding the currents and voltages generated in first-order RL or RC circuits when either dc voltage or current sources are suddenly applied.



Energy stored in the inductor at the time the switch is closed is given in terms of a nonzero initial current. The task is to find the expressions for the current in the circuit and for the voltage across the inductor after the switch has been closed.

$$V_s = Ri + L \frac{di}{dt},$$

$$\frac{di}{i - (V_s/R)} = \frac{-R}{L} dt,$$

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-(R/L)t}.$$

$$\frac{di}{dt} = \frac{-Ri + V_s}{L} = \frac{-R}{L} \left(i - \frac{V_s}{R} \right).$$

$$\int_{I_0}^{i(t)} \frac{dx}{x - (V_s/R)} = \frac{-R}{L} \int_0^t dy,$$

When the initial energy in the inductor is zero, is zero.



$$\frac{di}{dt} dt = \frac{-R}{L} \left(i - \frac{V_s}{R} \right) dt,$$

$$\ln \frac{i(t) - (V_s/R)}{I_0 - (V_s/R)} = \frac{-R}{L} t,$$

$$di = \frac{-R}{L} \left(i - \frac{V_s}{R} \right) dt.$$

$$\frac{i(t) - (V_s/R)}{I_0 - (V_s/R)} = e^{-(R/L)t},$$
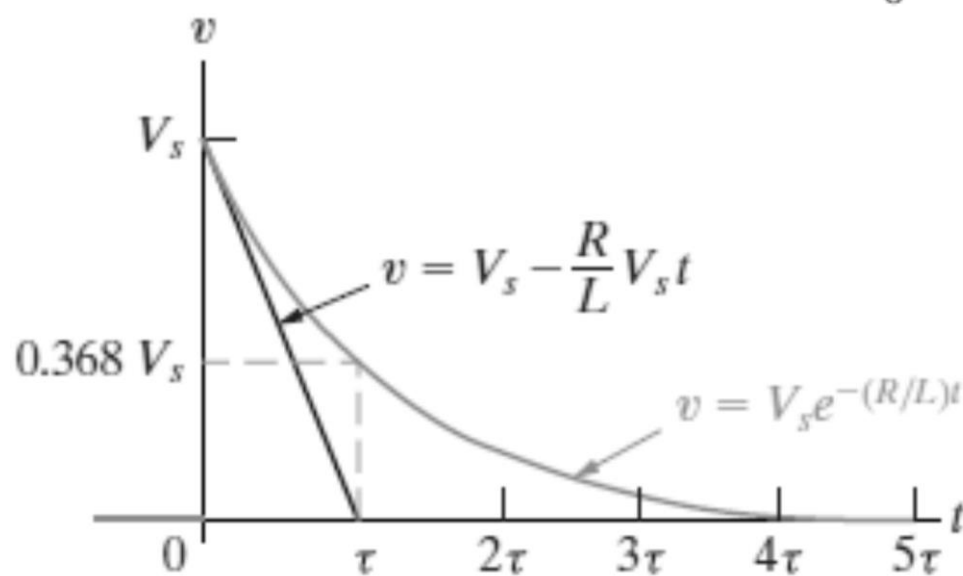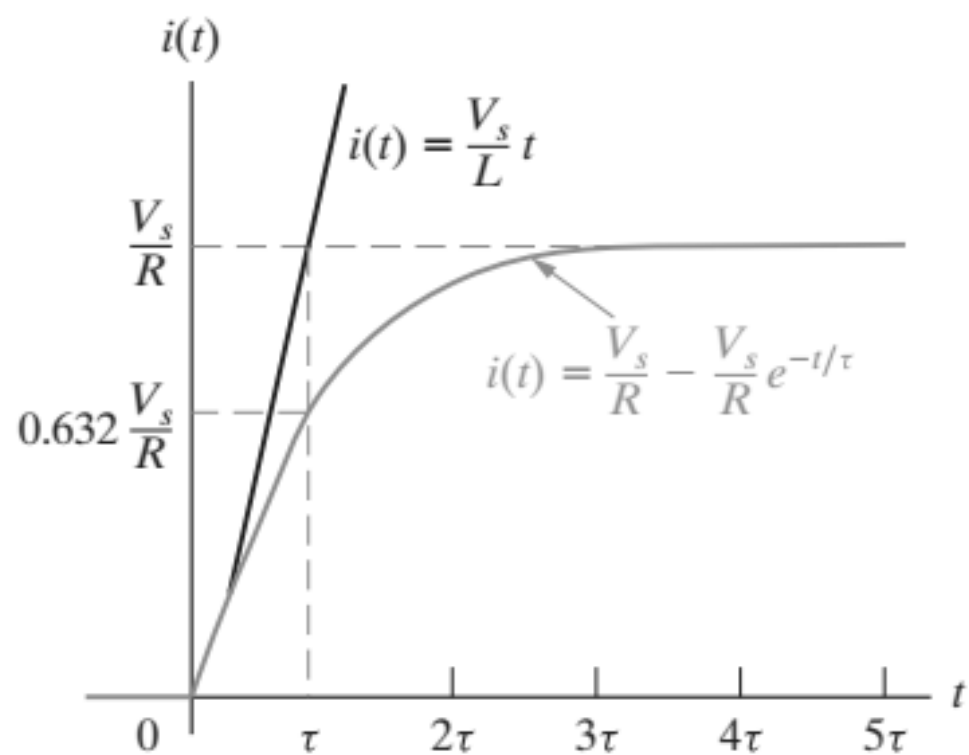
$$i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-(R/L)t}.$$




$$i(t) = \frac{V_s}{R} - \frac{v(t)}{R},$$

$$\frac{di}{dt} = -\frac{1}{R} \frac{dv}{dt}.$$

multiply by L

$$v = -\frac{L}{R} \frac{dv}{dt}.$$


$$\frac{dv}{dt} + \frac{R}{L} v = 0.$$

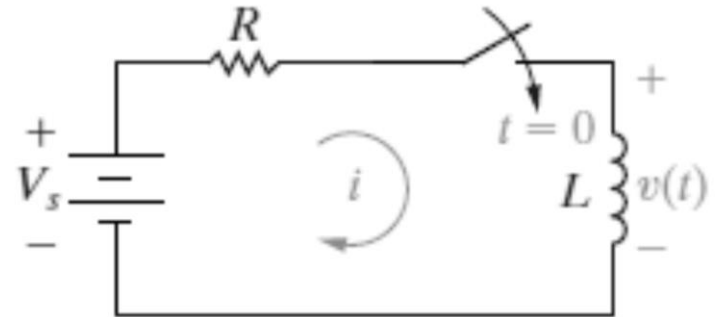

$$V_s = Ri + L \frac{di}{dt},$$

$$\frac{di}{dt} + \frac{R}{L} i = \frac{V_s}{L}.$$

The Step Response of an RC Circuit

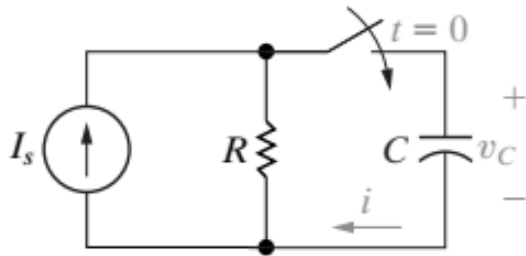

We can find the step response of a first order RC circuit by analyzing the circuit shown in Fig.

$$C \frac{dv_C}{dt} + \frac{v_C}{R} = I_s.$$

$$v_C = I_s R + (V_0 - I_s R) e^{-t/RC}, \quad t \geq 0.$$

$$\frac{di}{dt} + \frac{1}{RC} i = 0.$$

$$i = \left(I_s - \frac{V_0}{R} \right) e^{-t/RC}, \quad t \geq 0^+,$$


$$\frac{dx}{dt} + \frac{x}{\tau} = K, \quad x_f = K\tau,$$

$$\frac{dx}{dt} = \frac{-x}{\tau} + K = \frac{-(x - K\tau)}{\tau} = \frac{-(x - x_f)}{\tau}.$$


$$\frac{dx}{x - x_f} = \frac{-1}{\tau} dt.$$

$$\int_{x(t_0)}^{x(t)} \frac{du}{u - x_f} = -\frac{1}{\tau} \int_{t_0}^t dv.$$

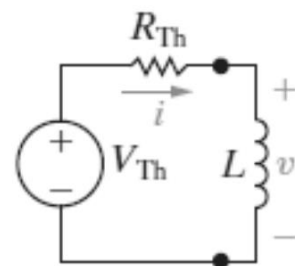
$$x(t) = x_f + [x(t_0) - x_f]e^{-(t-t_0)/\tau}.$$




(a)

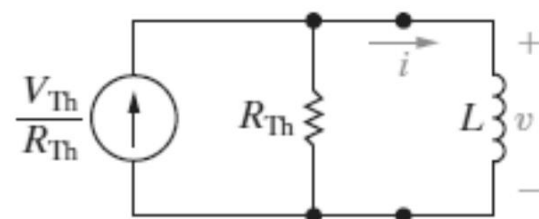

(b)

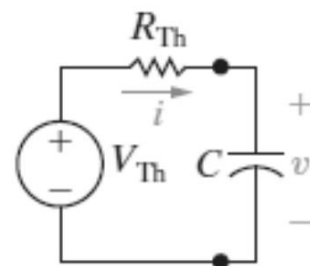

(c)

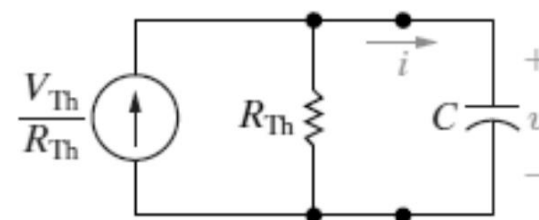

(d)

