

Instantaneous Power

$$p = vi. \quad \text{instantaneous power.}$$

$$v = V_m \cos(\omega t + \theta_v),$$
$$i = I_m \cos(\omega t + \theta_i),$$

$$v = V_m \cos(\omega t + \theta_v - \theta_i),$$
$$i = I_m \cos \omega t.$$

$$p = V_m I_m \cos(\omega t + \theta_v - \theta_i) \cos \omega t.$$

$$\cos \alpha \cos \beta = \frac{1}{2} \cos(\alpha - \beta) + \frac{1}{2} \cos(\alpha + \beta)$$


$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v - \theta_i).$$

$$\cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta$$

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t$$
$$- \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t.$$

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t$$
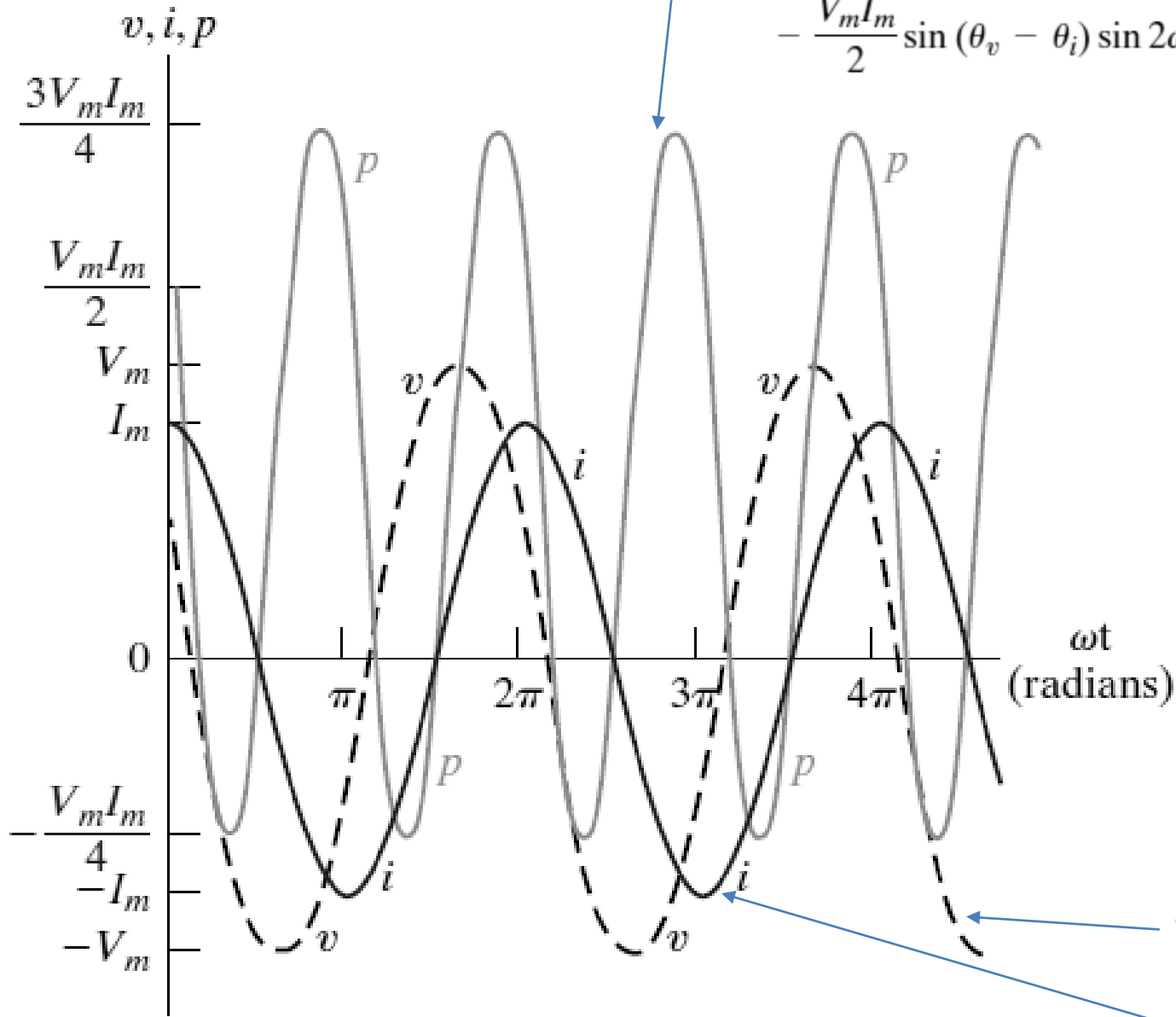
$$- \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t.$$



Average and Reactive Power

$$p = \underbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)}_P + \underbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t}_P - \underbrace{\frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t}_Q$$

$$p = P + P \cos 2\omega t - Q \sin 2\omega t,$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i),$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i).$$

P is called the **average power**, and *Q* is called the **reactive power**. **Average** power is sometimes called **real power**, because it describes the power in a circuit that is transformed from electric to nonelectric energy.

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p dt,$$

$$p = P + P \cos 2\omega t - Q \sin 2\omega t,$$


Power for Purely Resistive Circuits

$$\theta_v = \theta_i$$

$$p = P + P \cos 2\omega t - Q \sin 2\omega t, \quad =0$$

$$p = P + P \cos 2\omega t.$$

instantaneous real power

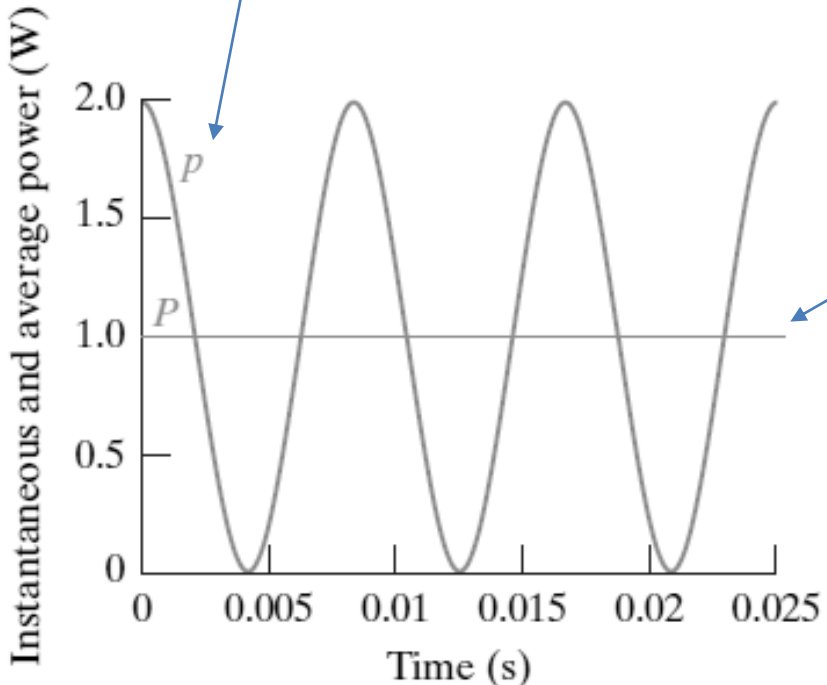

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i),$$

instantaneous real power can **never be negative**. in other words, **power cannot be extracted from a purely resistive network**. Rather, all the electric energy is dissipated in the form of thermal energy.


Power for Purely Inductive Circuits

$$p = -Q \sin 2\omega t.$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i).$$

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t.$$

$\theta_v - \theta_i = +90^\circ$

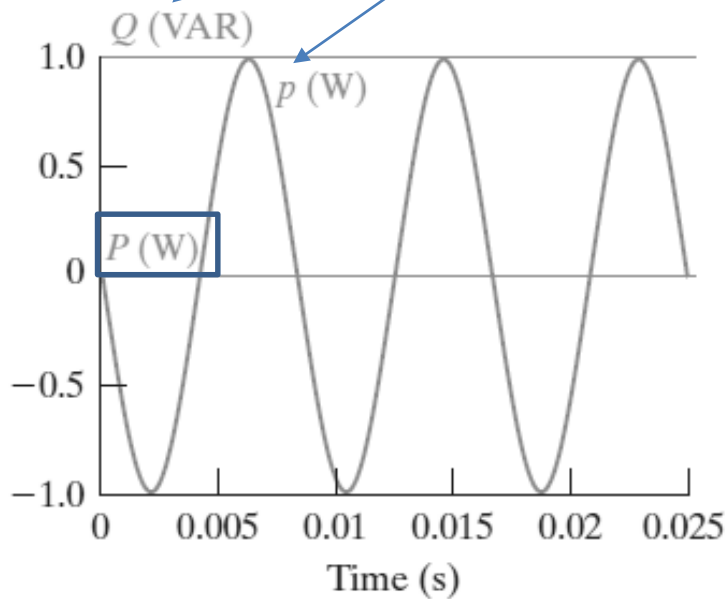

A measure of the power associated with purely inductive circuits is the reactive power Q . *The name reactive power comes from the characterization of an inductor as a reactive element; its impedance is purely reactive.* Note that average power P and reactive power Q carry the same dimension. To distinguish between average and reactive power, we use the units **watt (W)** for average power and **var (volt-amp reactive, or VAR)** for reactive power.

Figure 10.4 ▲ Instantaneous real power, average power, and reactive power for a purely inductive circuit.


Power for Purely Capacitive Circuits

$$p = -Q \sin 2\omega t.$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i).$$

$$\theta_v - \theta_i = -90^\circ.$$
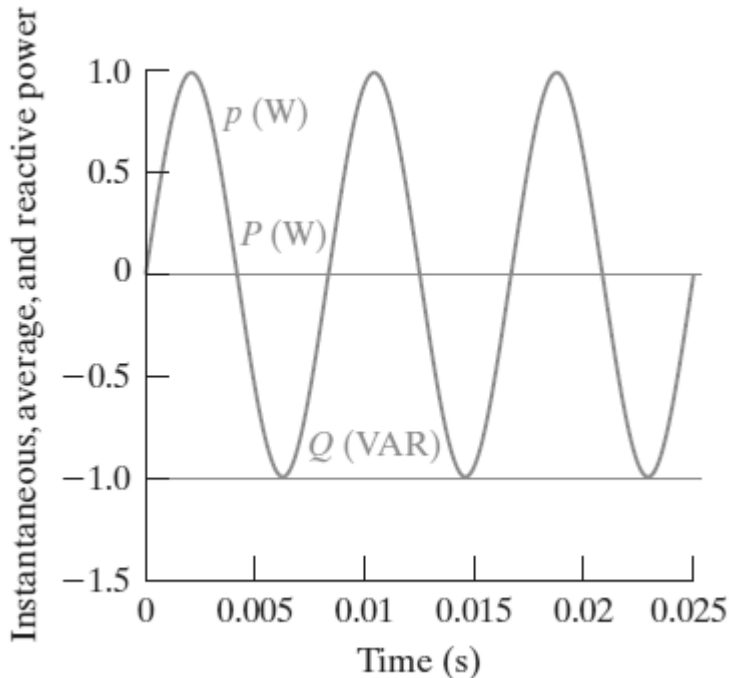
$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t.$$



Average power is zero, so there is no transformation of energy from electric to nonelectric form. In a purely capacitive circuit, the power is continually exchanged between the source driving the circuit and the electric field associated with the capacitive elements.

The Power Factor


$\theta_v - \theta_i$ plays a role in the computation of both average and reactive power and is referred to as the **power factor angle**. The **cosine** of this angle is called the **power factor, abbreviated pf**, and the **sine** of this angle is called the **reactive factor, abbreviated rf**. Thus

$$\text{pf} = \cos(\theta_v - \theta_i),$$

$$\text{rf} = \sin(\theta_v - \theta_i).$$

To completely describe this angle, we use the descriptive phrases **lagging power factor and leading power factor**. **Lagging power factor implies that current lags voltage**—hence an inductive load. **Leading power factor implies that current leads voltage**—hence a capacitive load. Both the power factor and the reactive factor are convenient quantities to use in describing electrical loads.

The rms Value and Power Calculations

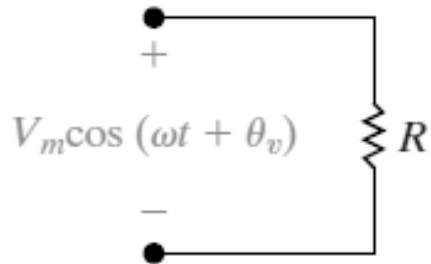

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} \frac{V_m^2 \cos^2(\omega t + \phi_v)}{R} dt$$

$$= \frac{1}{R} \left[\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi_v) dt \right].$$

$$P = \frac{V_{\text{rms}}^2}{R}. \quad P = I_{\text{rms}}^2 R.$$

The rms value is also referred to as the **effective value of the sinusoidal** voltage (or current). The rms value has an interesting property: Given an equivalent resistive load, R , and an equivalent time period, T , the rms value of a sinusoidal source delivers the same energy to R as does a dc source of the same value


and, by similar manipulation,

$$Q = V_{\text{eff}} I_{\text{eff}} \sin(\theta_v - \theta_i).$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i)$$
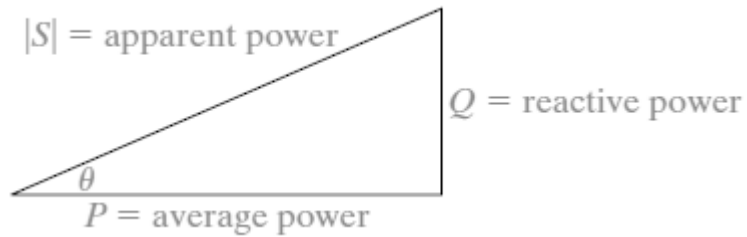
$$= V_{\text{eff}} I_{\text{eff}} \cos(\theta_v - \theta_i);$$




$$\tan \theta = \frac{Q}{P}.$$

$$\begin{aligned} \frac{Q}{P} &= \frac{(V_m I_m / 2) \sin(\theta_v - \theta_i)}{(V_m I_m / 2) \cos(\theta_v - \theta_i)} \\ &= \tan(\theta_v - \theta_i). \end{aligned}$$

The magnitude of complex power is referred to as **apparent power**

$$|S| = \sqrt{P^2 + Q^2}.$$

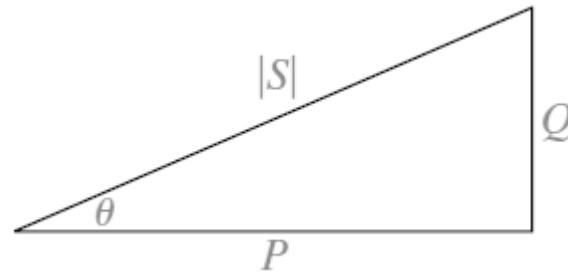

Power Calculations

We are now ready to develop additional equations that can be used to calculate real, reactive, and complex power

$$\begin{aligned} S &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + j \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \\ &= \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)] \\ &= \frac{V_m I_m}{2} e^{j(\theta_v - \theta_i)} = \frac{1}{2} V_m I_m \underline{/(\theta_v - \theta_i)}. \end{aligned}$$

$$S = V_{\text{eff}} I_{\text{eff}} \underline{/(\theta_v - \theta_i)}$$

$$= V_{\text{eff}} I_{\text{eff}} e^{j(\theta_v - \theta_i)}$$

$$= V_{\text{eff}} e^{j\theta_v} I_{\text{eff}} e^{-j\theta_i}$$

$$= \mathbf{V}_{\text{eff}} \mathbf{I}_{\text{eff}}^*$$