


Patch Clamp Methods

Lecture 10

Assoc. Prof. Erkan Tuncay
Department of Biophysics



The patch clamp technique



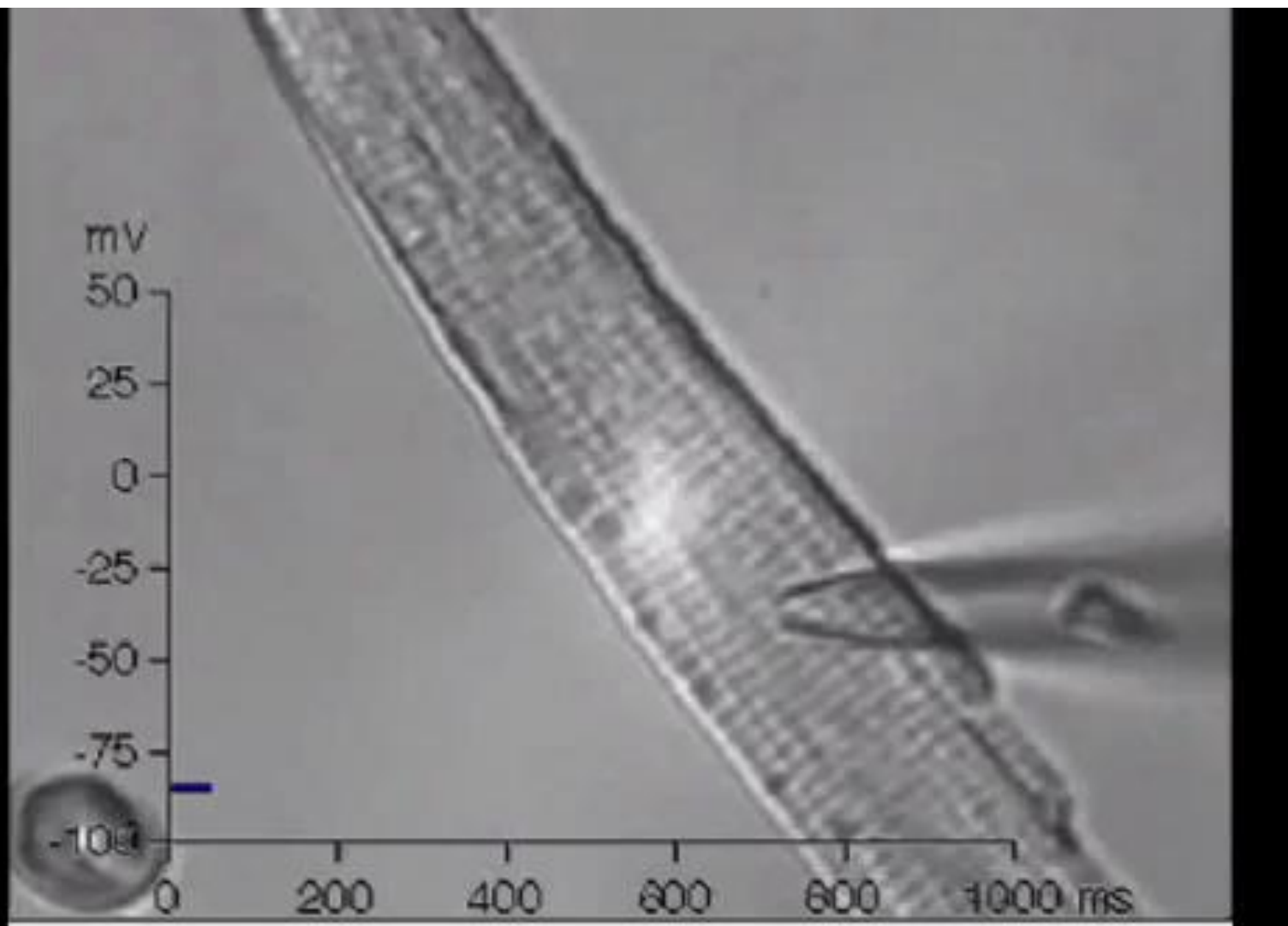

Courtesy of Anja Verkerk and Antoni van Ginneken, AMC, Amsterdam, The Netherlands


The patch clamp technique

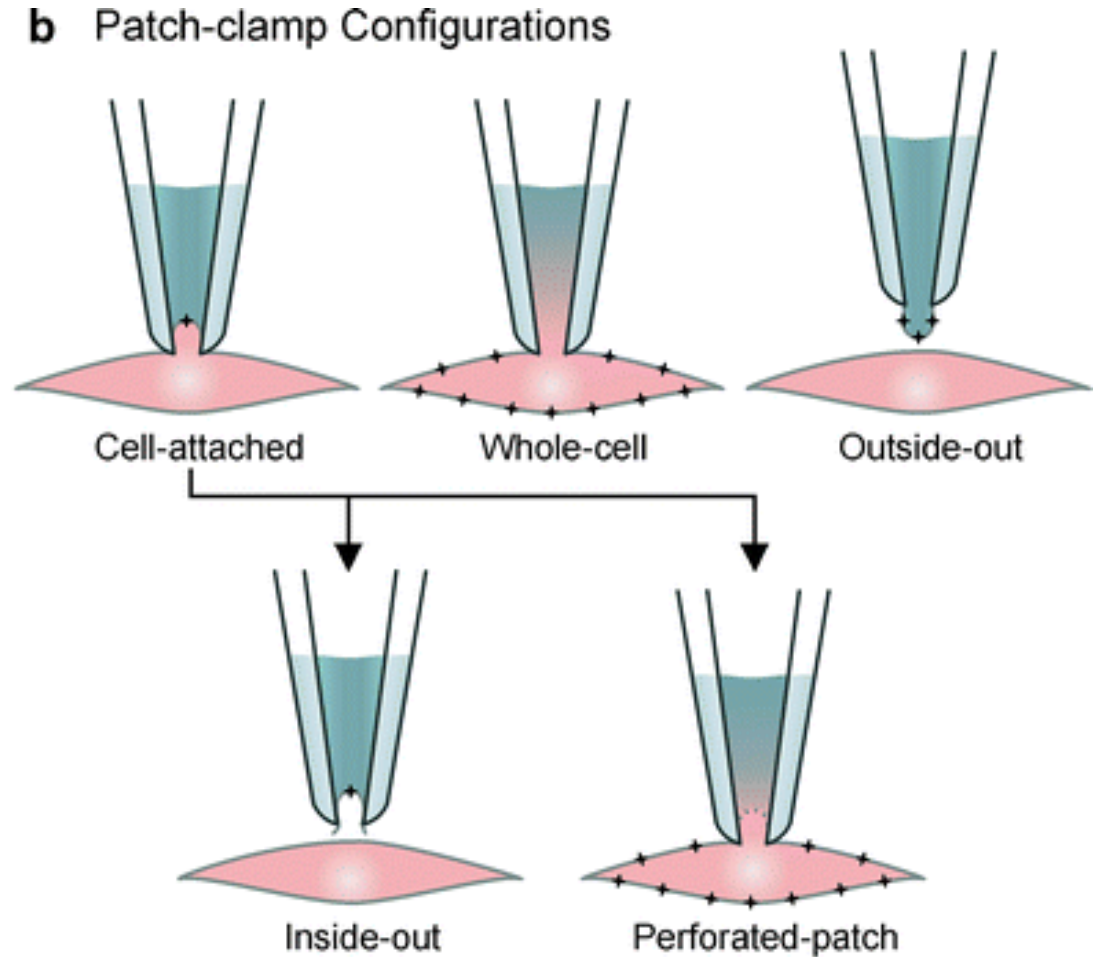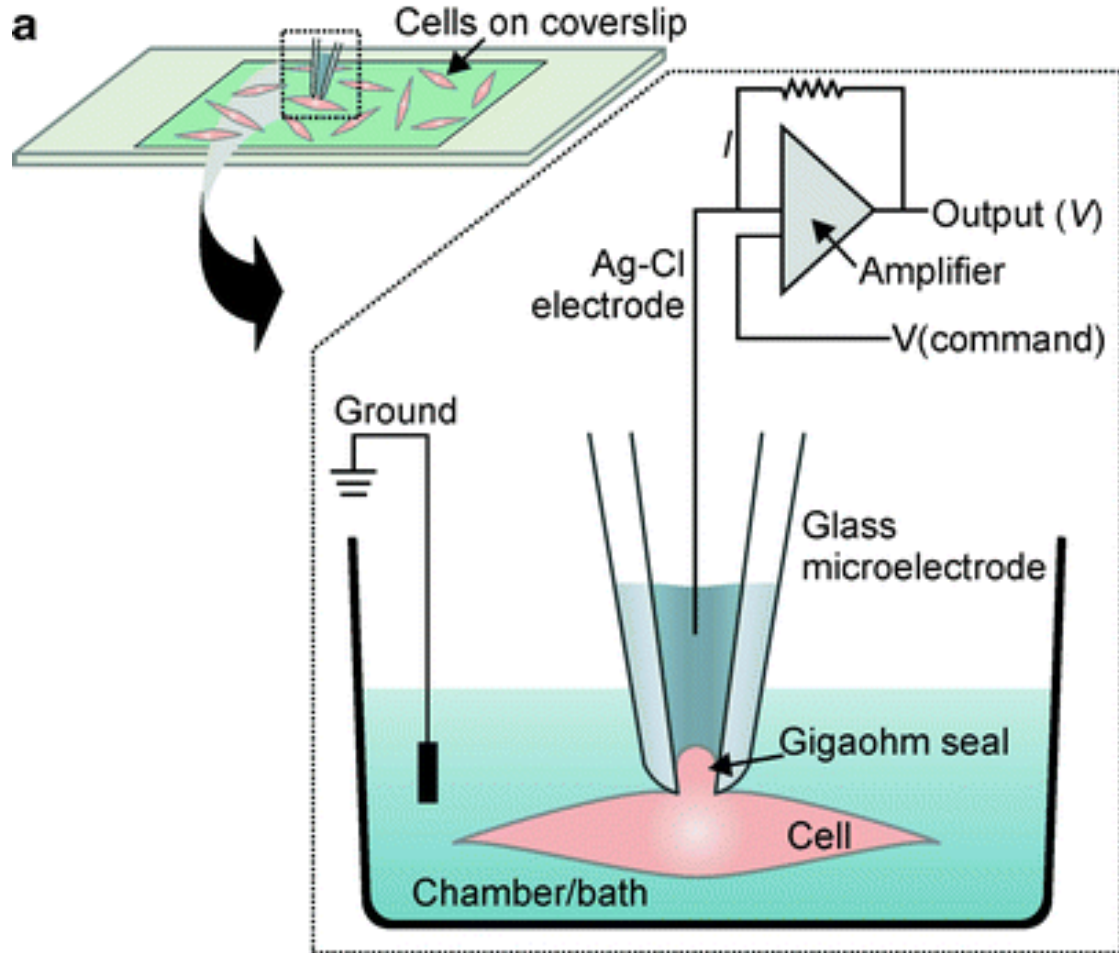


The patch clamp technique

The voltage clamp technique shown before was adequate for large currents, but produced large 'background noise'

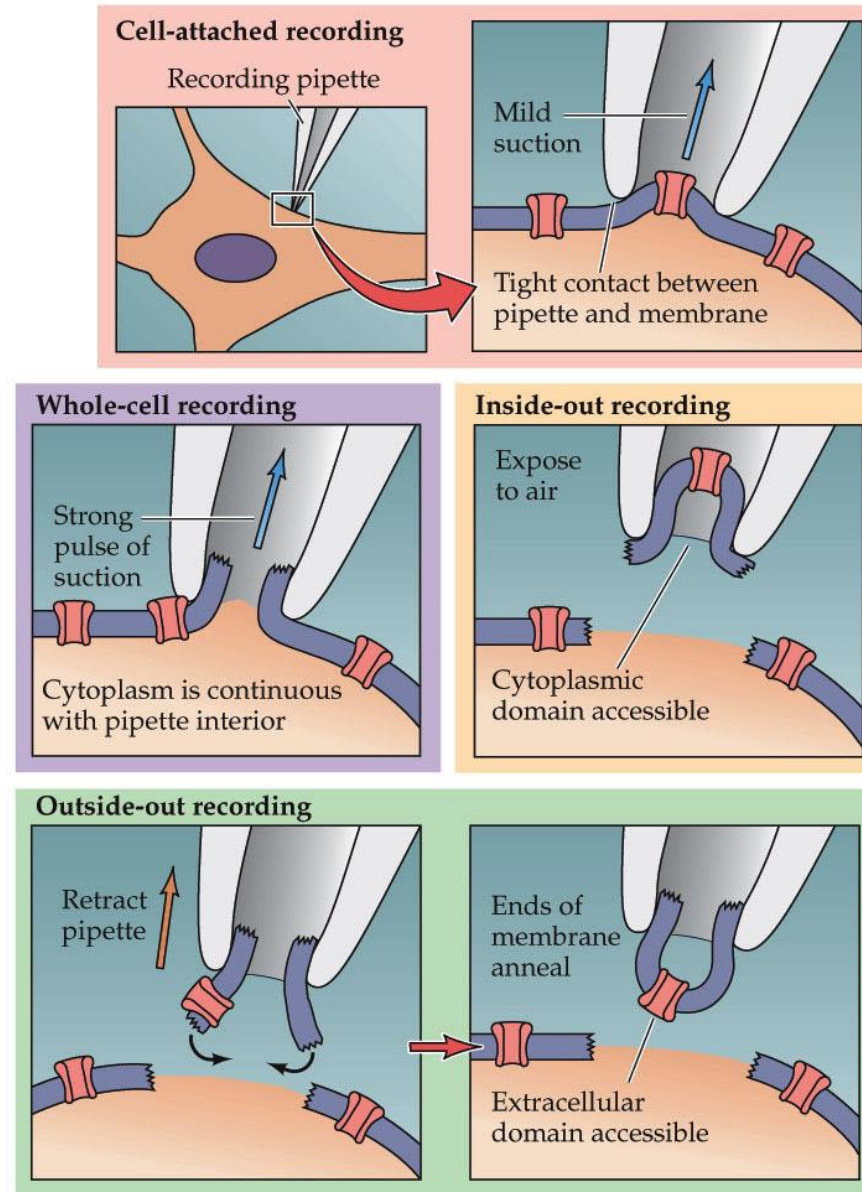'Patch clamp' technique has superior signal-to-noise ratio, so very small currents can be measured, even down to the current passed through a single ion channel!






Combining R_M and C_M – the RC circuit

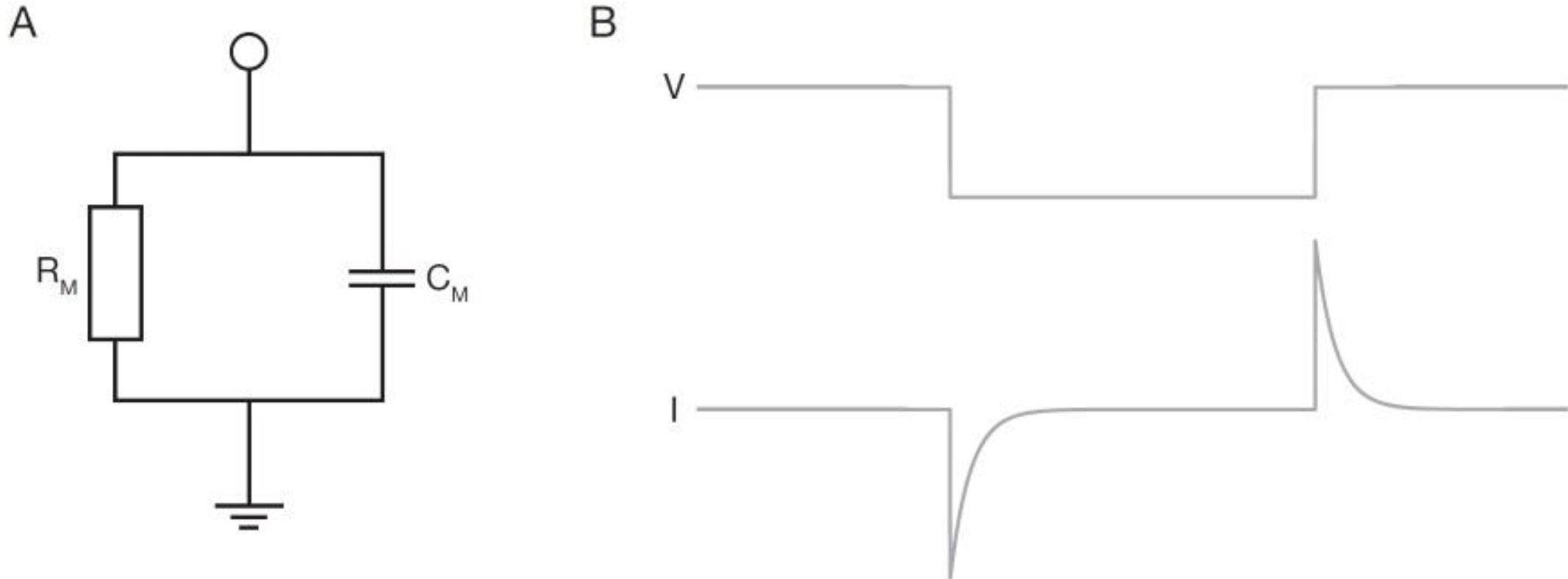


Basic schematic of the electrical properties of a plasma membrane. A: A circuit diagram showing the membrane capacitance and membrane resistance in parallel to each other. **B:** Traces showing a command voltage step (top) and the resulting current response (bottom) for a simple plasma membrane being voltage clamped.

Pipette in bath

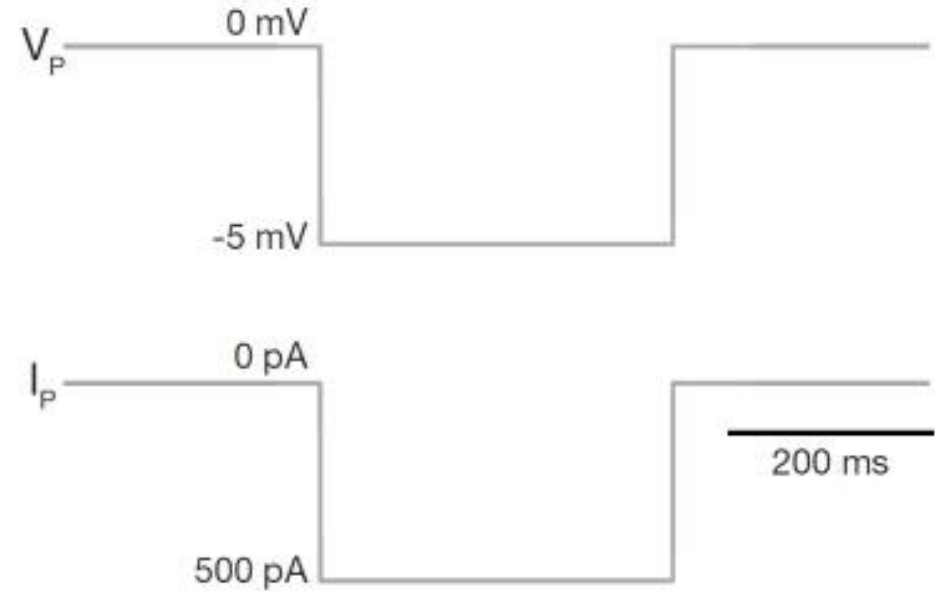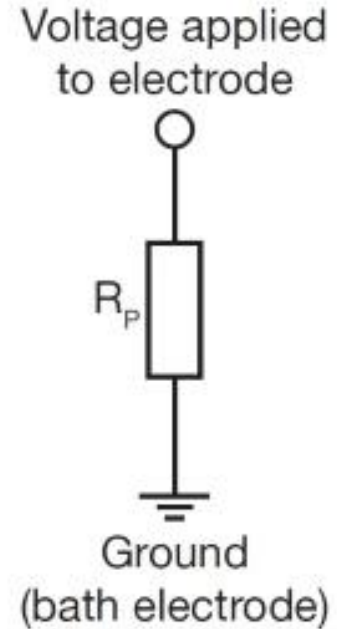
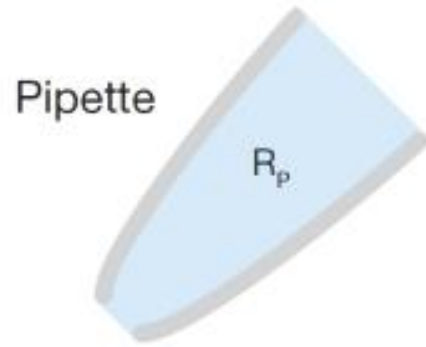


Schematic explaining the ‘pipette in bath’ configuration. In this configuration, the current is determined solely by the pipette resistance. The pipette is indicated on the left. The corresponding electrical circuit is shown in the middle with the voltage and current traces depicted on the right.


On-cell

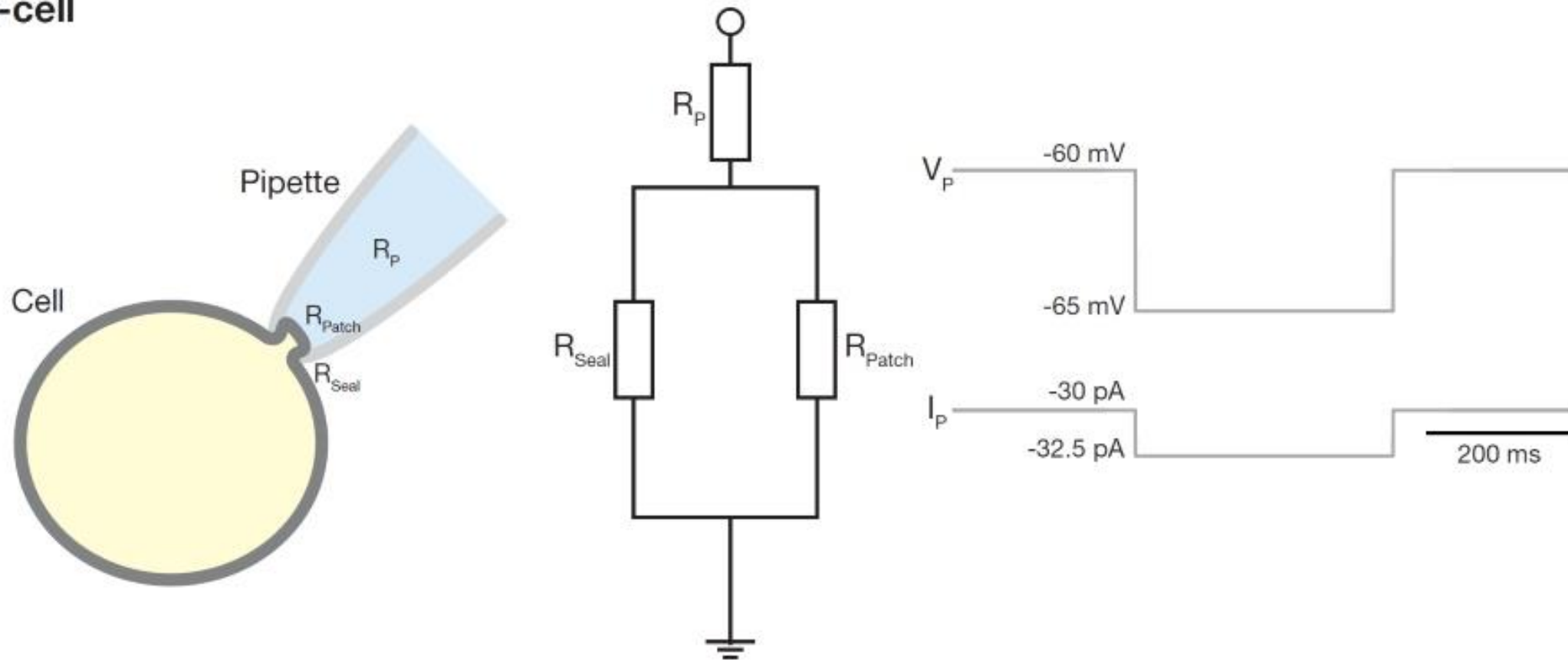

Schematic explaining the 'on-cell' configuration. In this configuration, the current is determined by the pipette resistance in series to a parallel circuit of the patch and seal resistances. The pipette with cell is indicated on the left. The corresponding electrical circuit is shown in the middle with the voltage and current traces depicted on the right. Note that as the patch resistance is very high, the current over this resistance is negligible.

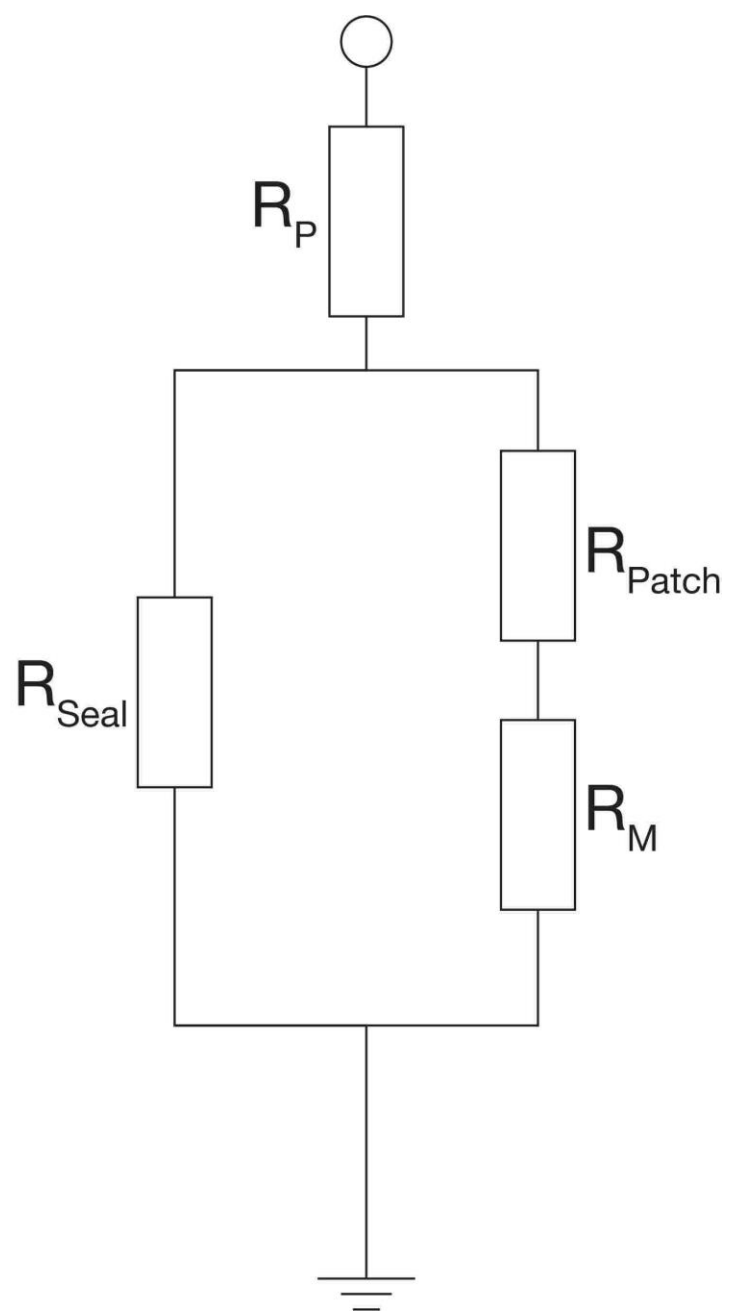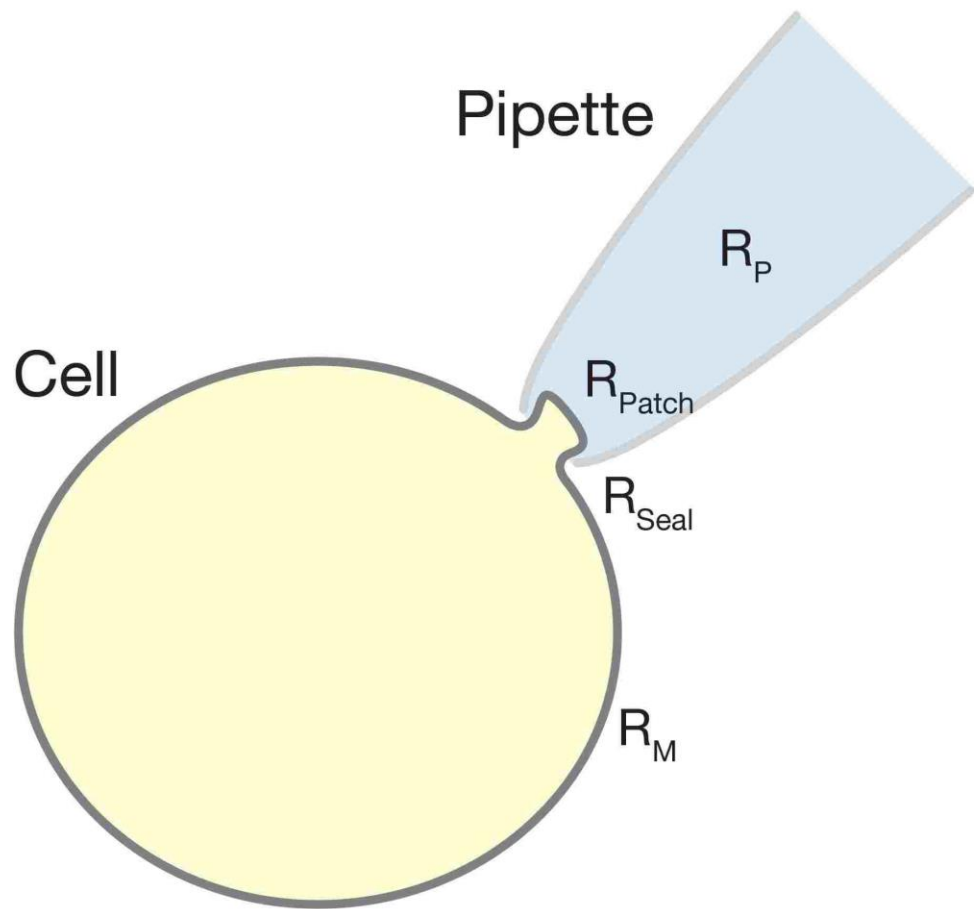

Whole-cell

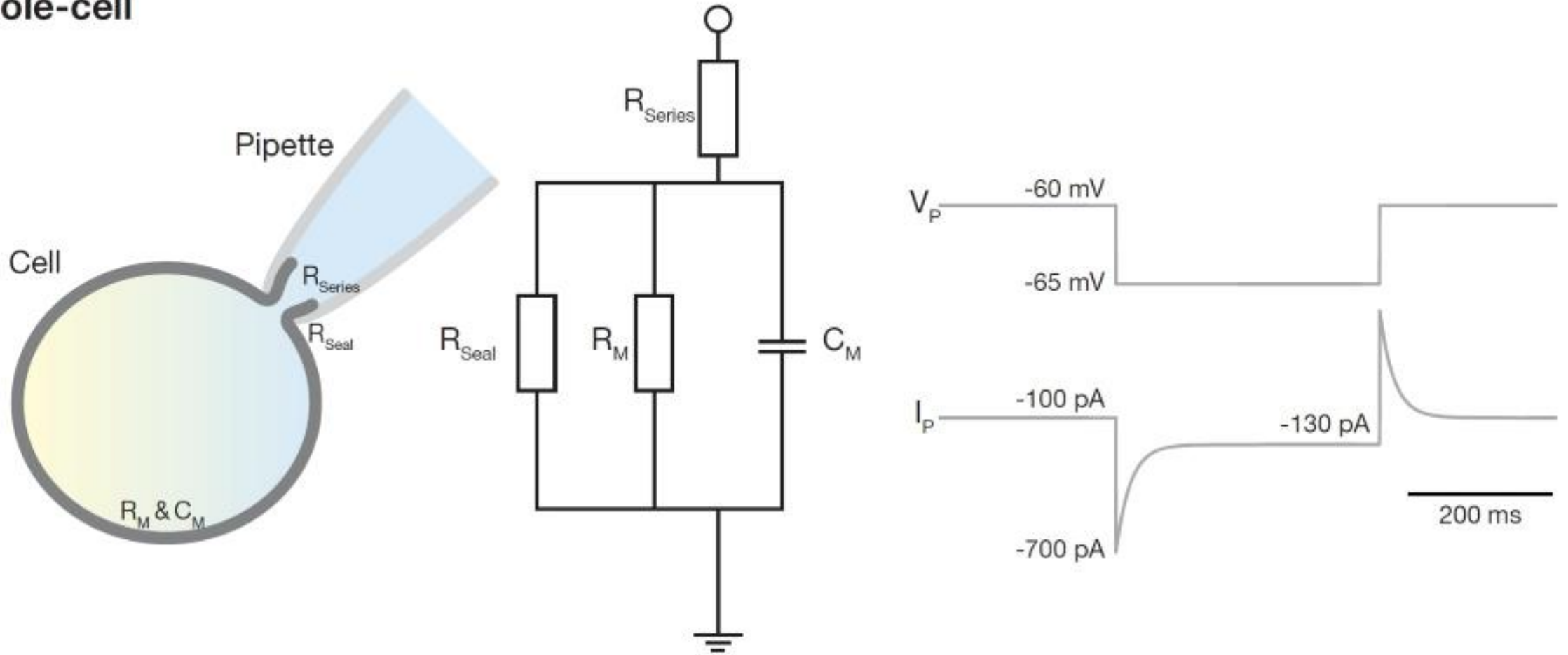

Schematic explaining the 'whole-cell' configuration. In this configuration, the current is determined by the series resistance in series with a parallel circuit of the seal and membrane resistances as well as the membrane capacitance. The pipette with cell is indicated on the left. The corresponding electrical circuit is shown in the middle with the voltage and current traces depicted on the right.