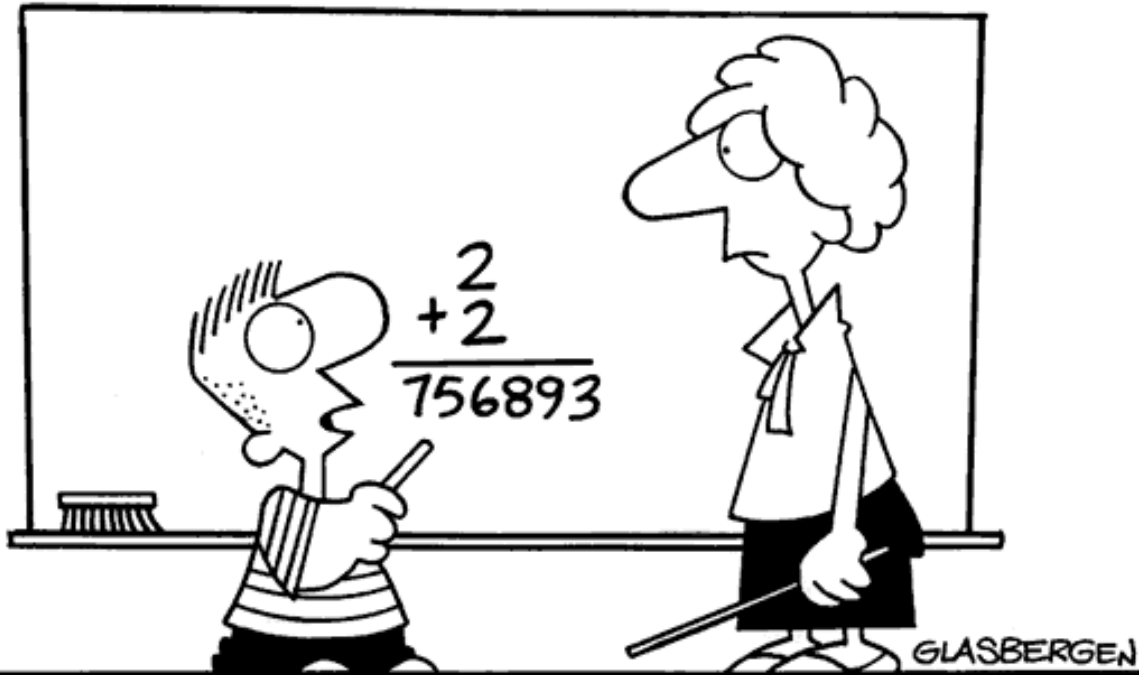


Circuits Containing Resistors & Capacitors (RC Circuits)


Copyright 1996 Randy Glasbergen. www.glasbergen.com



**“In an increasingly complex world,
sometimes old questions require new answers.”**

RC Circuits

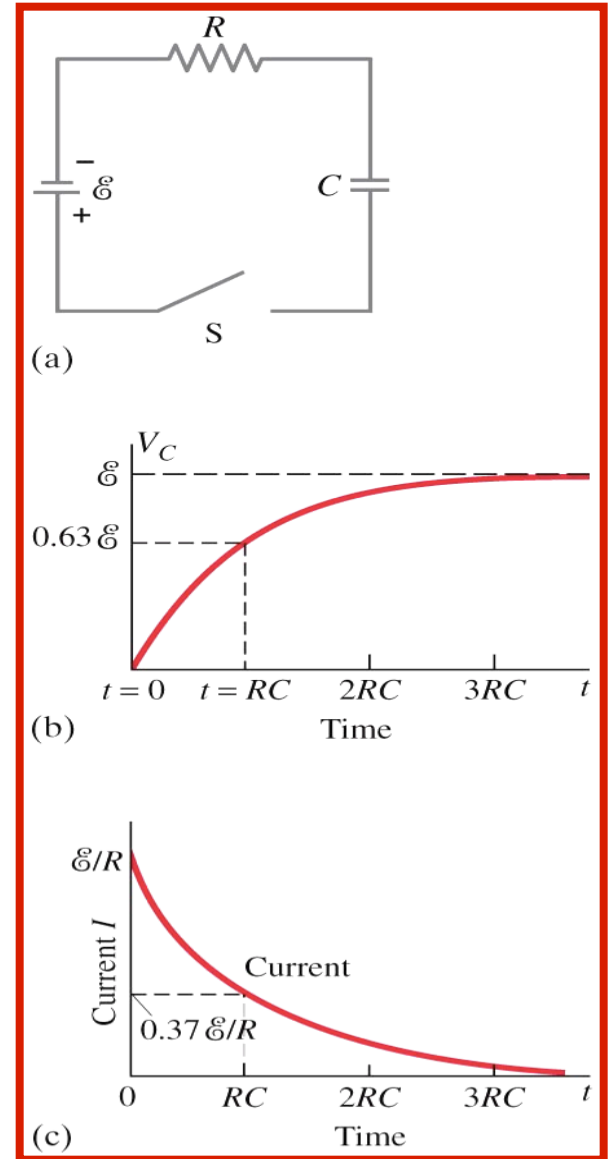When the switch is closed, the capacitor will begin to charge. As it does, the voltage across it increases, and the current through the resistor decreases.



- To find the voltage as a function of time, use the **Loop Rule** to write the equation for the **voltage changes** around the loop:

$$\mathcal{E} = IR + \frac{Q}{C}.$$

- **$I = dQ/dt$** , so integrate to find the charge as a function of time:

$$Q = C\mathcal{E}(1 - e^{-t/RC}).$$

- The voltage across the capacitor is **$V_C = Q/C$** . The current **I** at time **t** is found by differentiating the charge:

$$I = \frac{dQ}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}.$$

- The quantity **RC** that appears in the exponent is called **the time constant** of the circuit:

$$\tau = RC.$$

Example

RC Circuit, with EMF.


•The capacitance in the circuit shown is

$C = 0.30 \mu\text{F}$, the total resistance is

$R = 20 \text{ k}\Omega$, the battery emf is

$E = 12 \text{ V}$. Calculate:

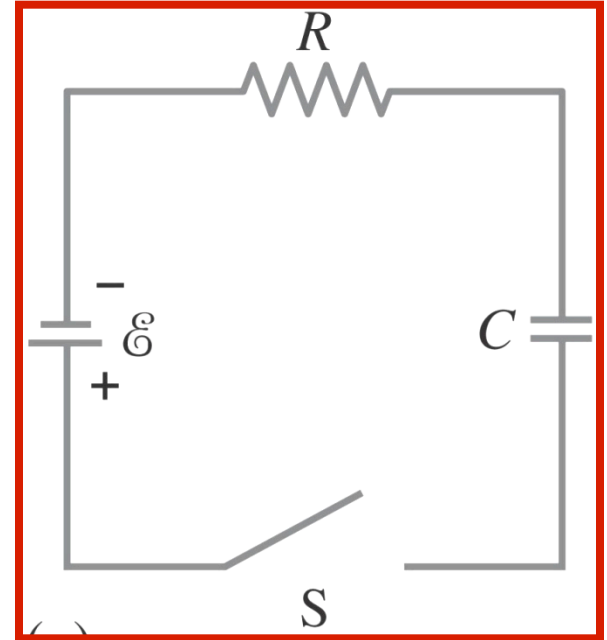- the time constant,
- the maximum charge the capacitor could acquire,
- the time it takes for the charge to reach **99%** of this value,
- the current **I** when the charge **Q** is half its maximum value,
- the maximum current,
- the charge **Q** when the current **I** is **0.20** of its maximum value.



- If an isolated charged capacitor is connected across a resistor, it discharges:


$$Q = Q_0 e^{-t/RC}.$$

- The voltage & current as functions of time can be found from the charge:

$$V_C = V_0 e^{-t/RC}$$

and
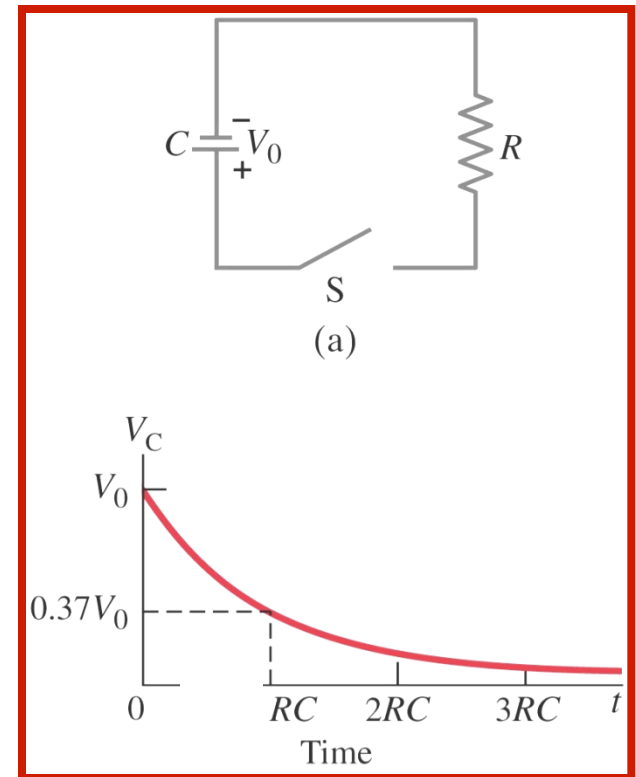
$$I = -\frac{dQ}{dt} = \frac{Q_0}{RC} e^{-t/RC} = I_0 e^{-t/RC}.$$




Example: Discharging RC circuit.

• In the RC circuit shown, the battery has fully charged the capacitor, so $Q_0 = C E$. Then at $t = 0$ the switch is thrown from position a to b. The battery emf is 20.0 V , and the capacitance $C = 1.02 \mu\text{F}$. The current I is observed to decrease to 0.50 of its initial value in $40 \mu\text{s}$.


(a) What is the value of Q , the charge on the capacitor, at $t = 0$?

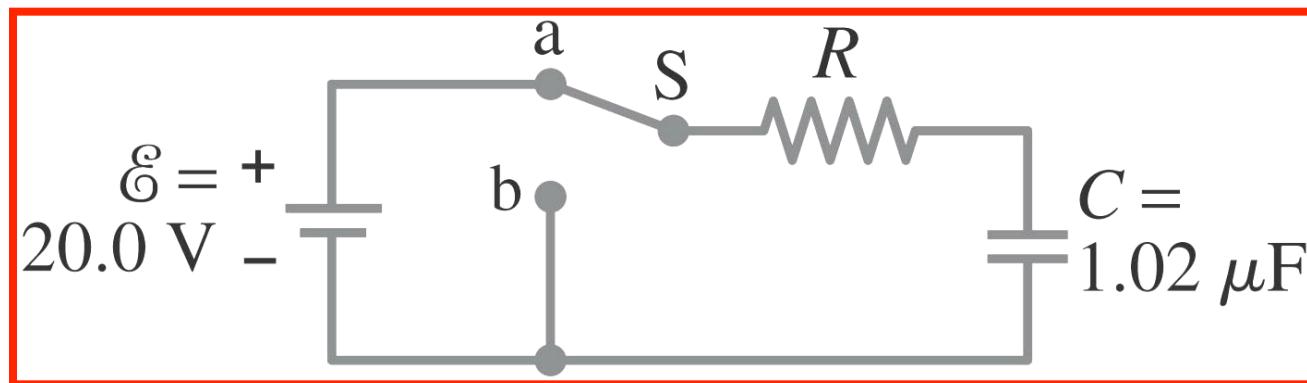(b) What is the value of R ? (c) What is Q at $t = 60 \mu\text{s}$?



Conceptual Example: Bulb in RC circuit.

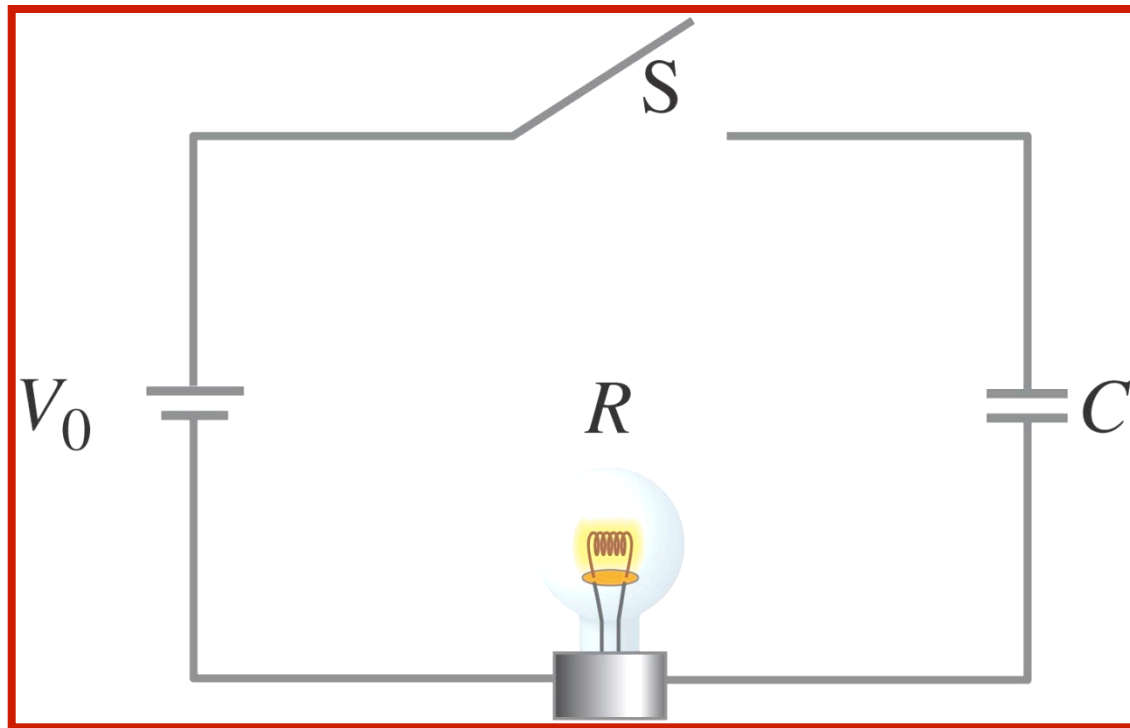
- In the circuit shown, the capacitor is originally uncharged.
- Describe the behavior of the lightbulb from the instant switch S is closed until a long time later.



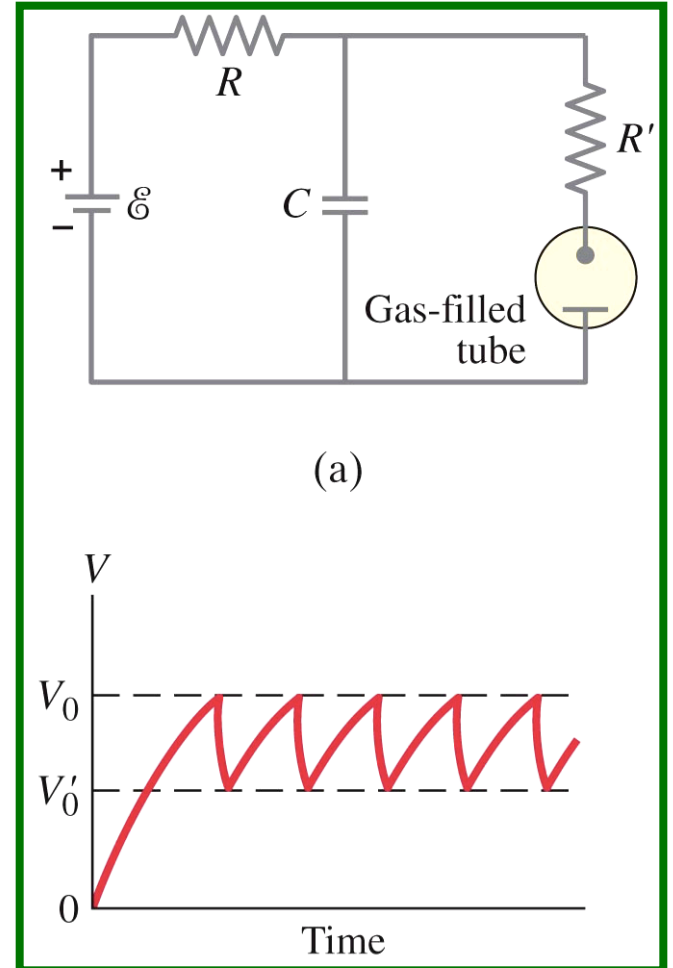Example

Resistor in a turn signal.


Estimate the order of magnitude of the resistor in a turn-signal circuit.




Electric Hazards

- Most people can “feel” a current of **1 mA**; a few **mA** of current begins to be painful. Currents above **10 mA** may cause uncontrollable muscle contractions, making rescue difficult.
- Currents around **100 mA** passing through the torso can cause death by ventricular fibrillation.
- Higher currents may not cause fibrillation, but can cause severe burns.
- Household voltage can be lethal if you are wet and in good contact with the ground. Be careful!

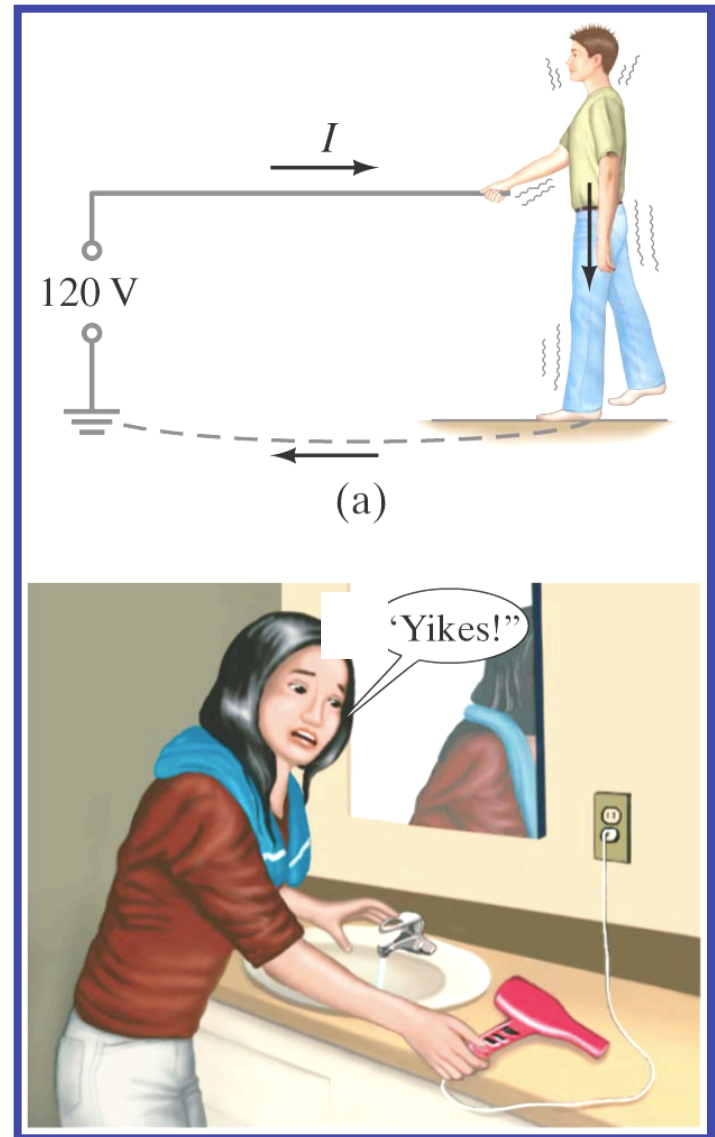A person receiving a shock has become part of a complete circuit.



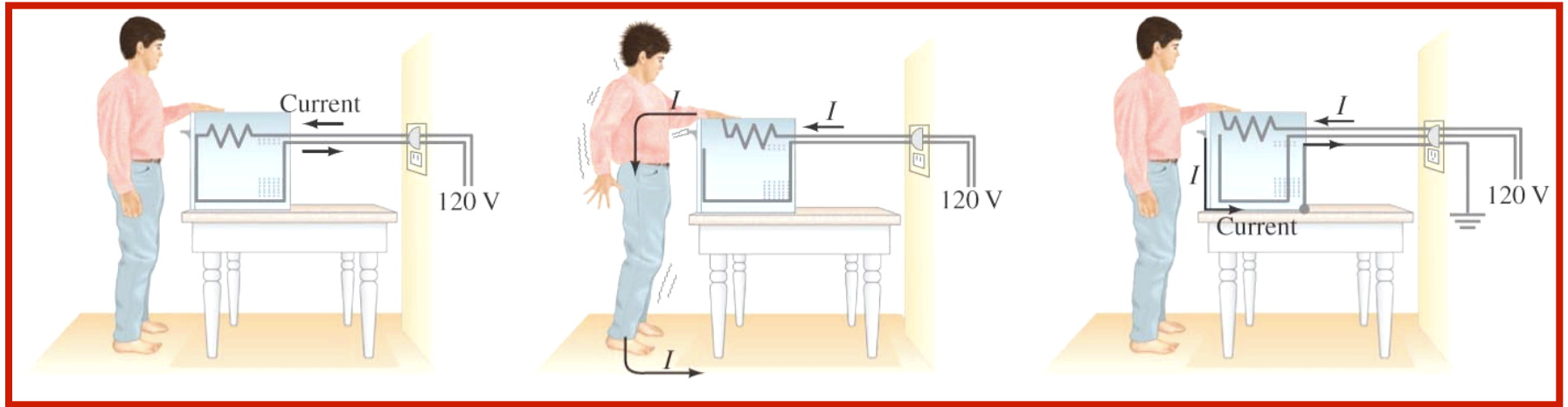Faulty wiring and improper grounding can be hazardous. Make sure electrical work is done by a professional.



- The safest plugs are those with three prongs; they have a separate ground line.
- Here is an example of household wiring – colors can vary, though! Be sure you know which is the hot wire before you do anything.

