

BME 311

Biomedical Instrumentation I



04 – Instrumentation Amplifier



Faculty of Engineering

Department of Biomedical Engineering

Dr. Mehmet Yüksekaya

Differential Amplifier



Operation modes



- Common mode signals appear simultaneously and in-phase on both inputs.
- The **common mode rejection ratio (CMRR)** is a metric used to quantify the ability of the amplifier to reject common-mode signals.
- The **common-mode rejection ratio (CMRR)** is the ratio of the common-mode gain to differential-mode gain.

Instrumentation Amplifier



$$V_0 = A_d V_D + A_{CM} V_{CM}$$

$$CMRR = \frac{A_d}{A_{CM}} = \frac{\left(\frac{R_3}{R_1 + R_3}\right) \left(\frac{R_2 + R_4}{R_2}\right) \left(\frac{R_A}{R_P} + \frac{1}{2}\right) + \left(\frac{R_4}{R_2}\right) \left(\frac{R_B}{R_P} + \frac{1}{2}\right)}{\left(\frac{R_3}{R_1 + R_3}\right) \left(\frac{R_2 + R_4}{R_2}\right) - \left(\frac{R_4}{R_2}\right)}$$

Instrumentation Amplifier



$$V_0 = A_d V_D + A_{CM} V_{CM}$$

$$CMRR = \frac{A_d}{A_{CM}} = \frac{\left(\frac{R_3}{R_1 + R_3}\right) \left(\frac{R_2 + R_4}{R_2}\right) \left(\frac{R_A}{R_P} + \frac{1}{2}\right) + \left(\frac{R_4}{R_2}\right) \left(\frac{R_B}{R_P} + \frac{1}{2}\right)}{\left(\frac{R_3}{R_1 + R_3}\right) \left(\frac{R_2 + R_4}{R_2}\right) - \left(\frac{R_4}{R_2}\right)}$$

$$R_4 = R_3, R_2 = R_1 \text{ and } R_A = R_B$$

Instrumentation Amplifier



$$V_0 = A_d V_D + A_{CM} V_{CM}$$

$$R_4 = R_3, R_2 = R_1 \text{ and } R_A = R_B$$

$$A_d = \left(\frac{2R_A}{R_P} + 1 \right) \left(\frac{R_4}{R_2} \right)$$
$$A_{CM} = \left[\left(\frac{R_4}{R_2 + R_4} \right) \left(\frac{R_2 + R_4}{R_2} \right) - \left(\frac{R_4}{R_2} \right) \right] = 0$$

Instrumentation Amplifier



$$\text{CMRR} = \frac{A_d}{A_{\text{cm}}} \quad ; \quad A_{\text{cm}} \rightarrow 0 \quad \text{CMRR} \rightarrow \infty$$

$$V_0 = A_d V_D + A_{CM} V_{CM}$$