


# **BME 311 Biomedical Instrumentation I**

---

11-Active Filters


# ECG Example

---

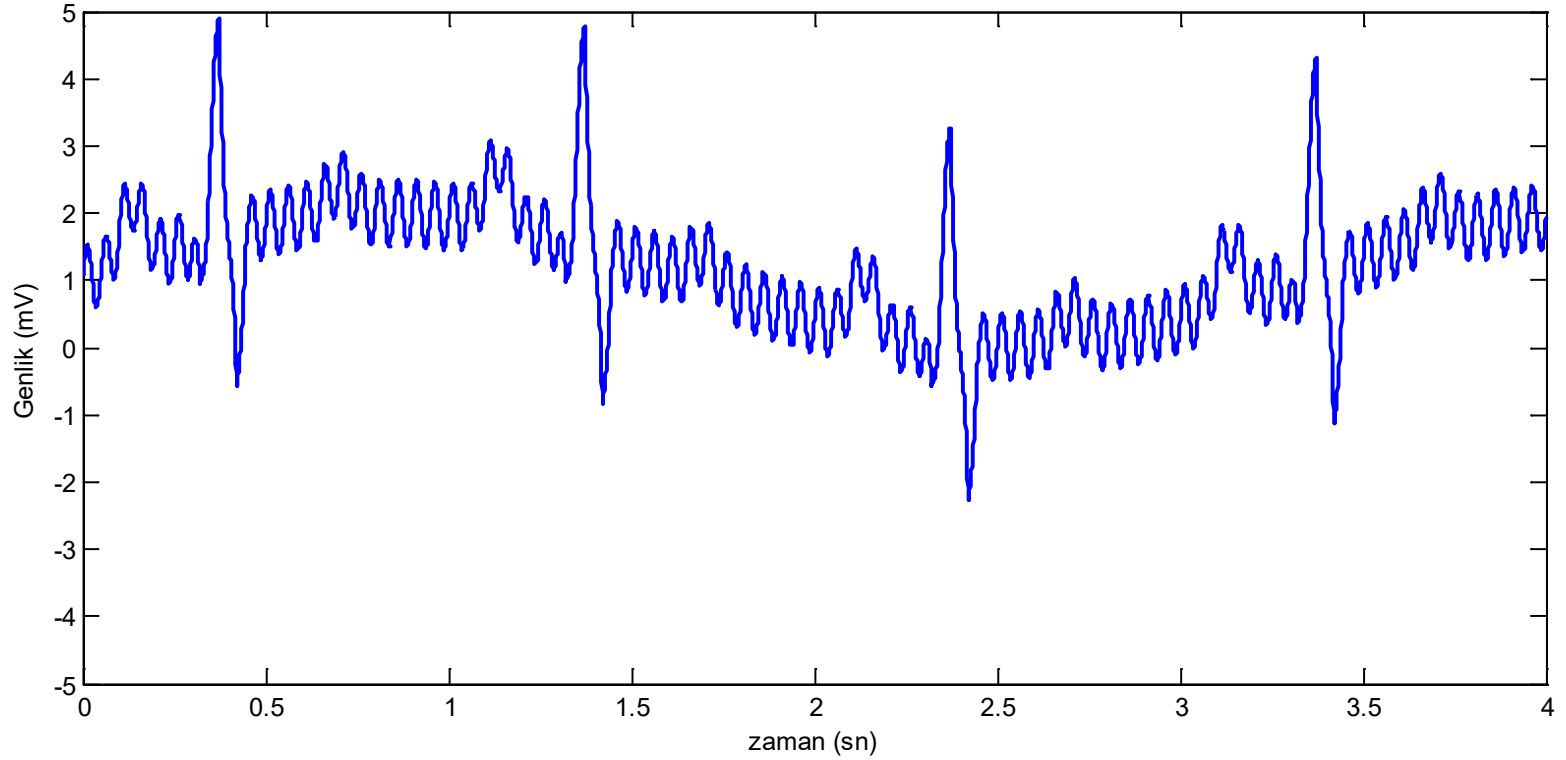


# ECG Example


---

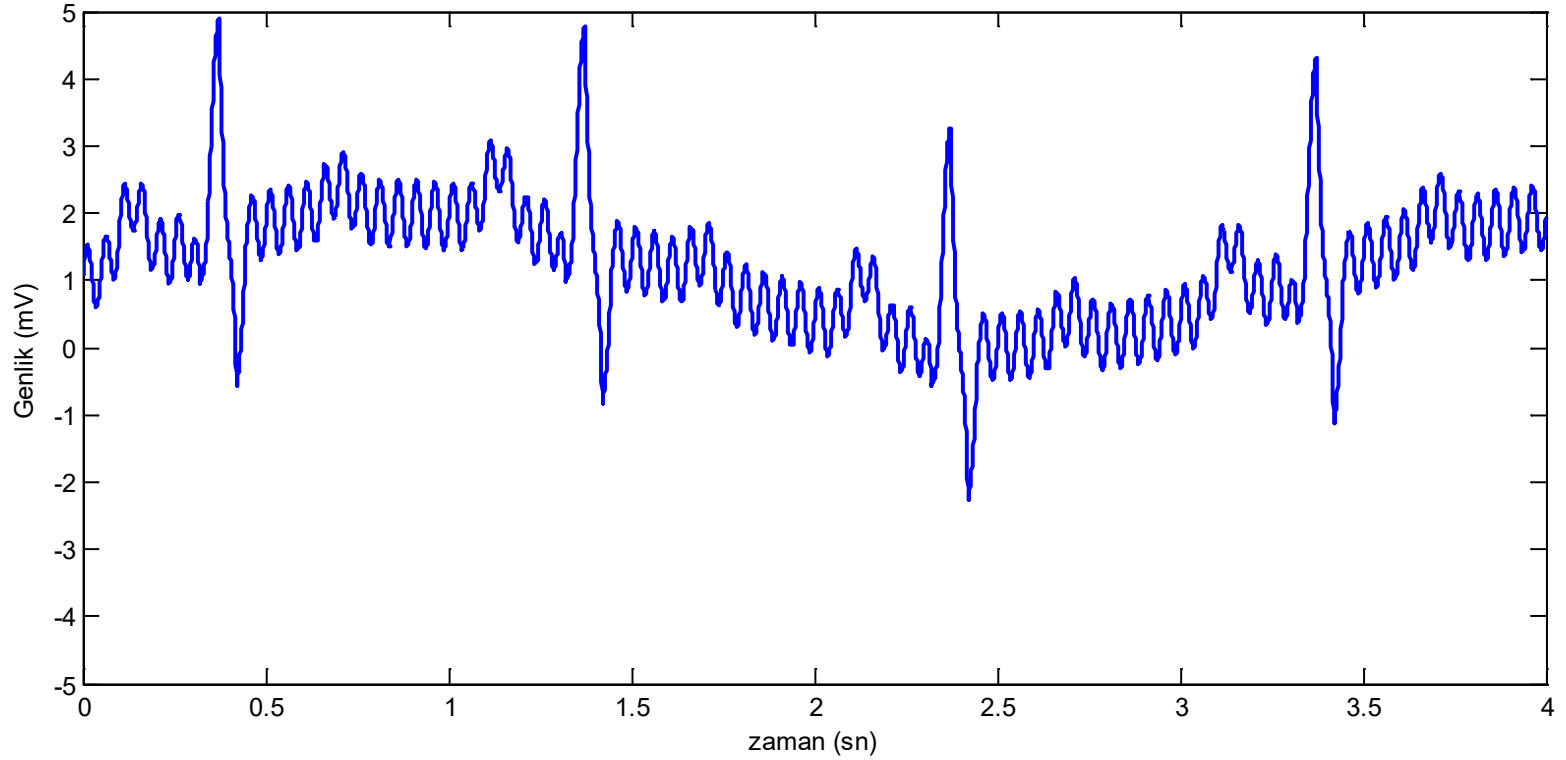


# ECG Example

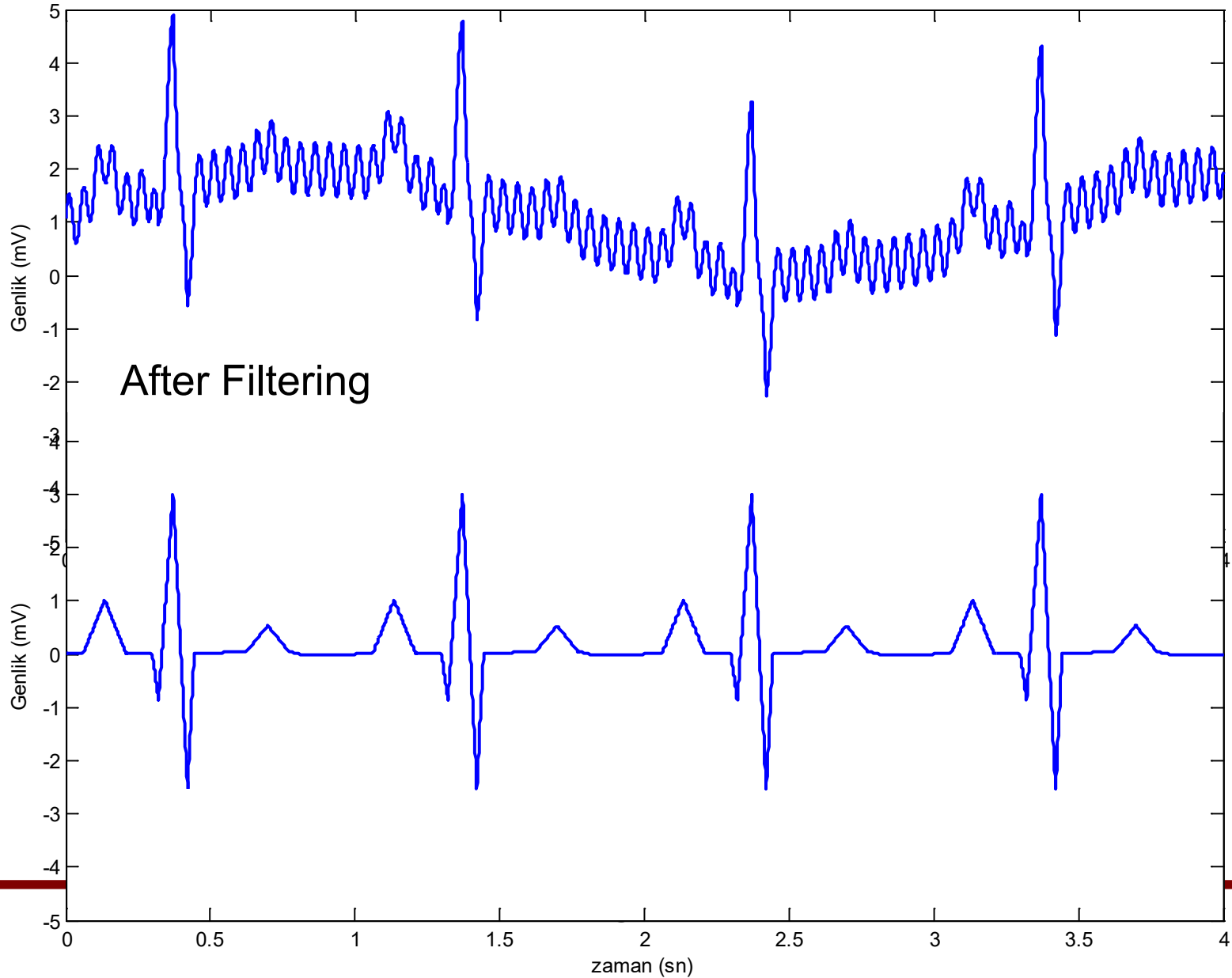


# ECG Example

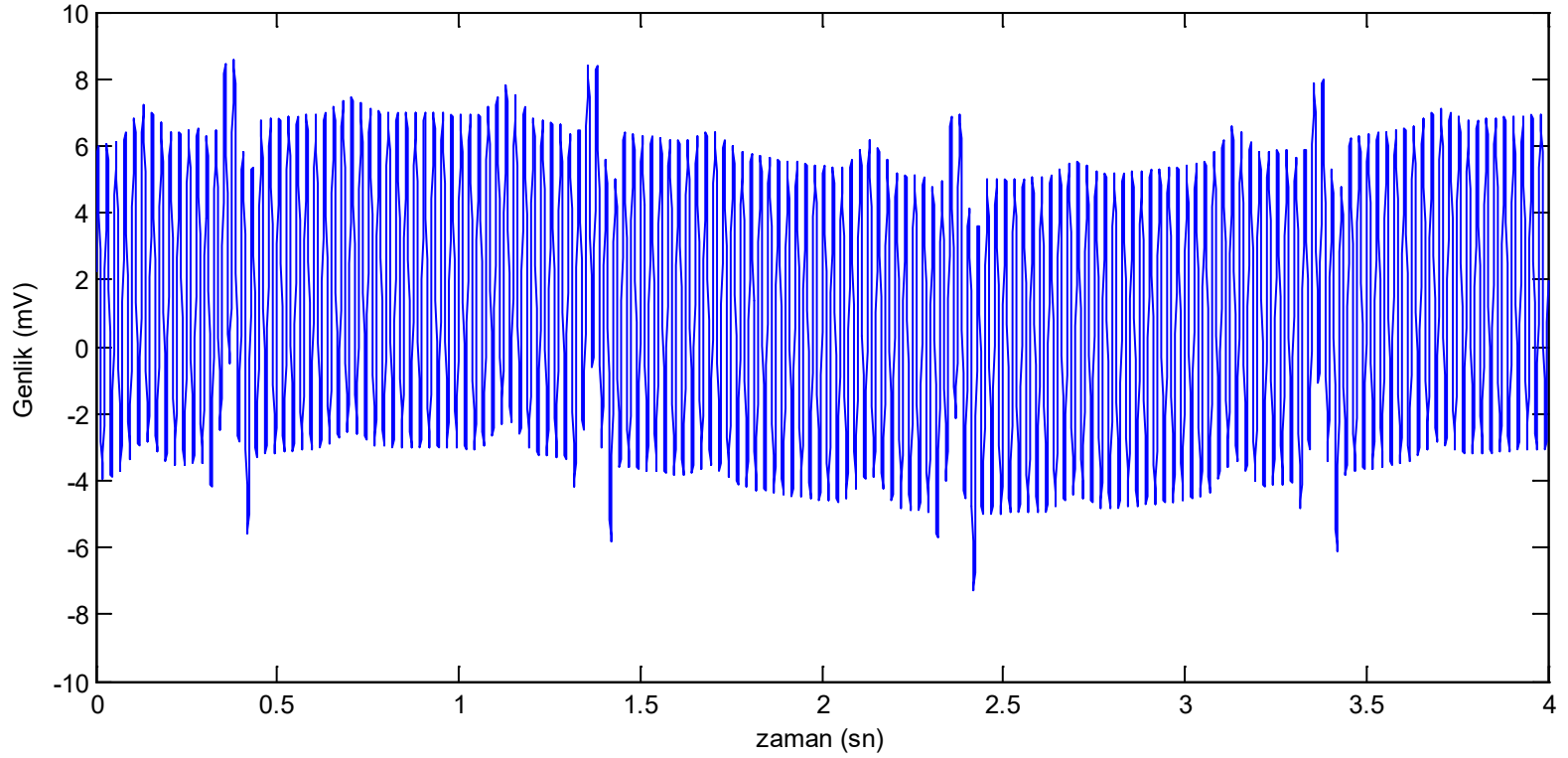


# ECG Example

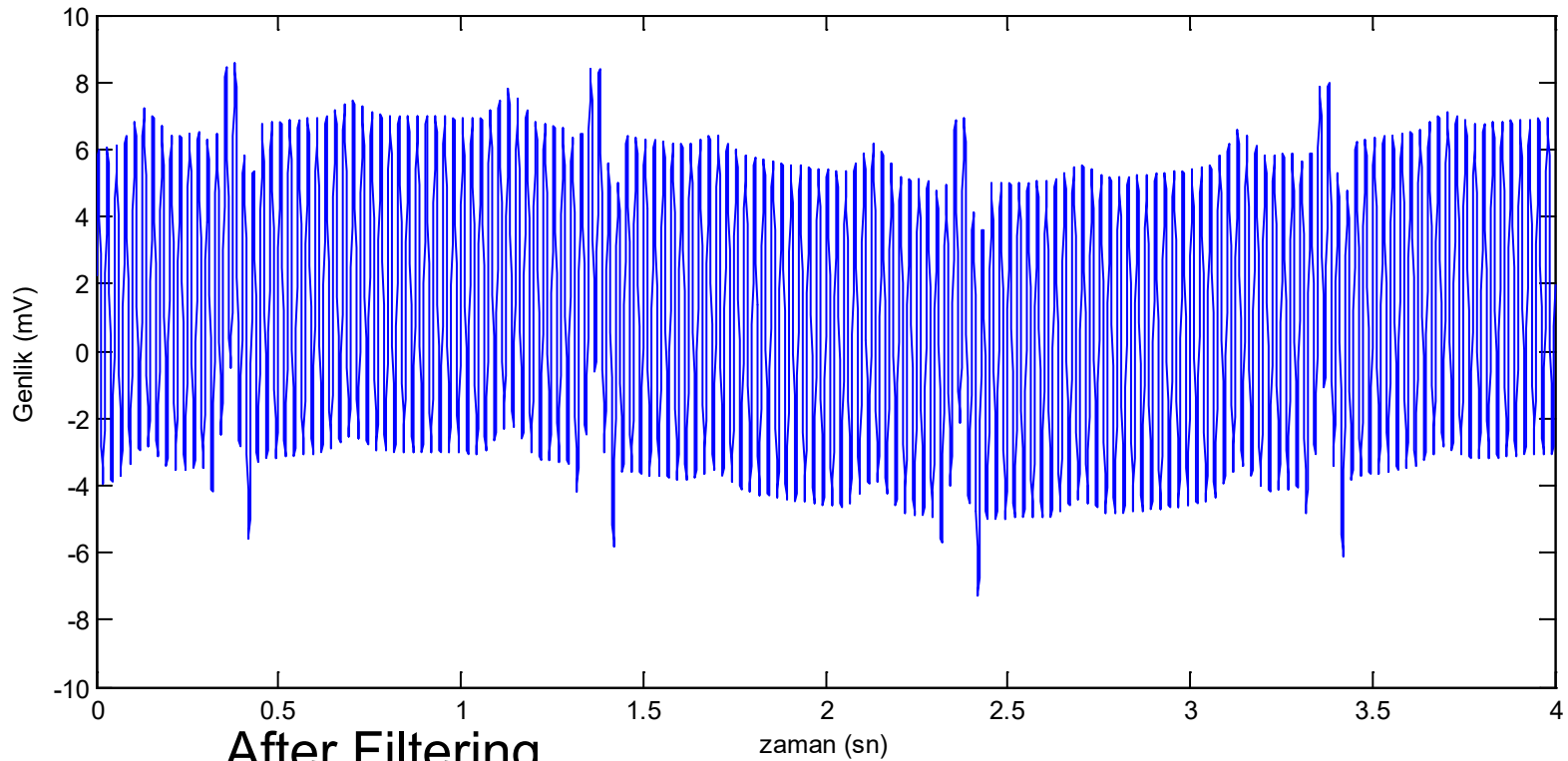


After Filtering

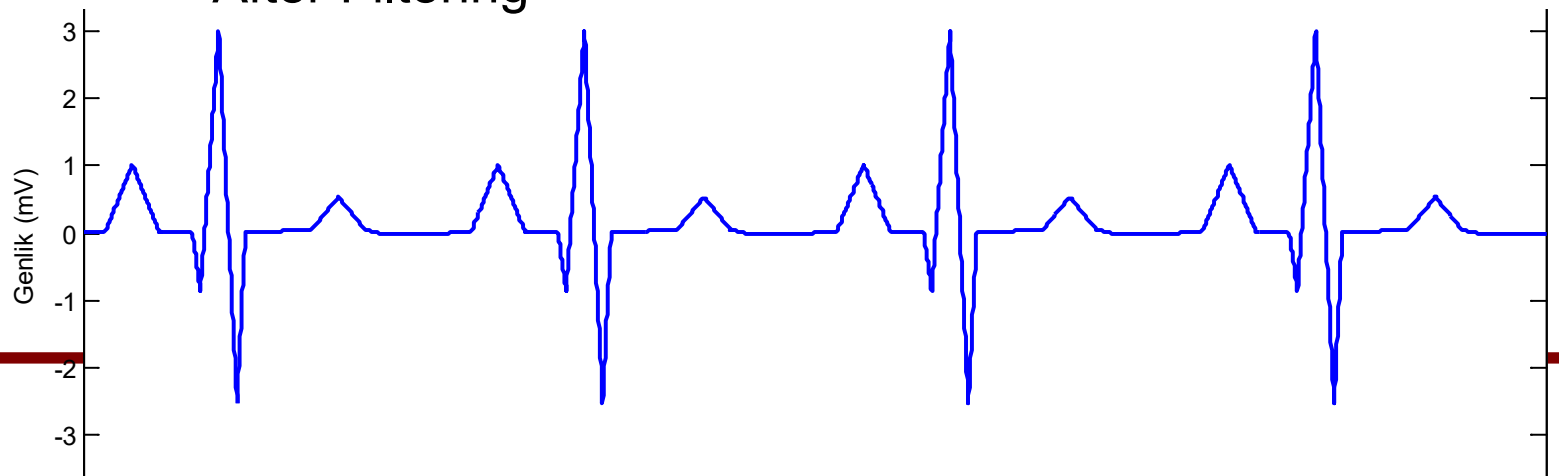

# High Frequency Analysis

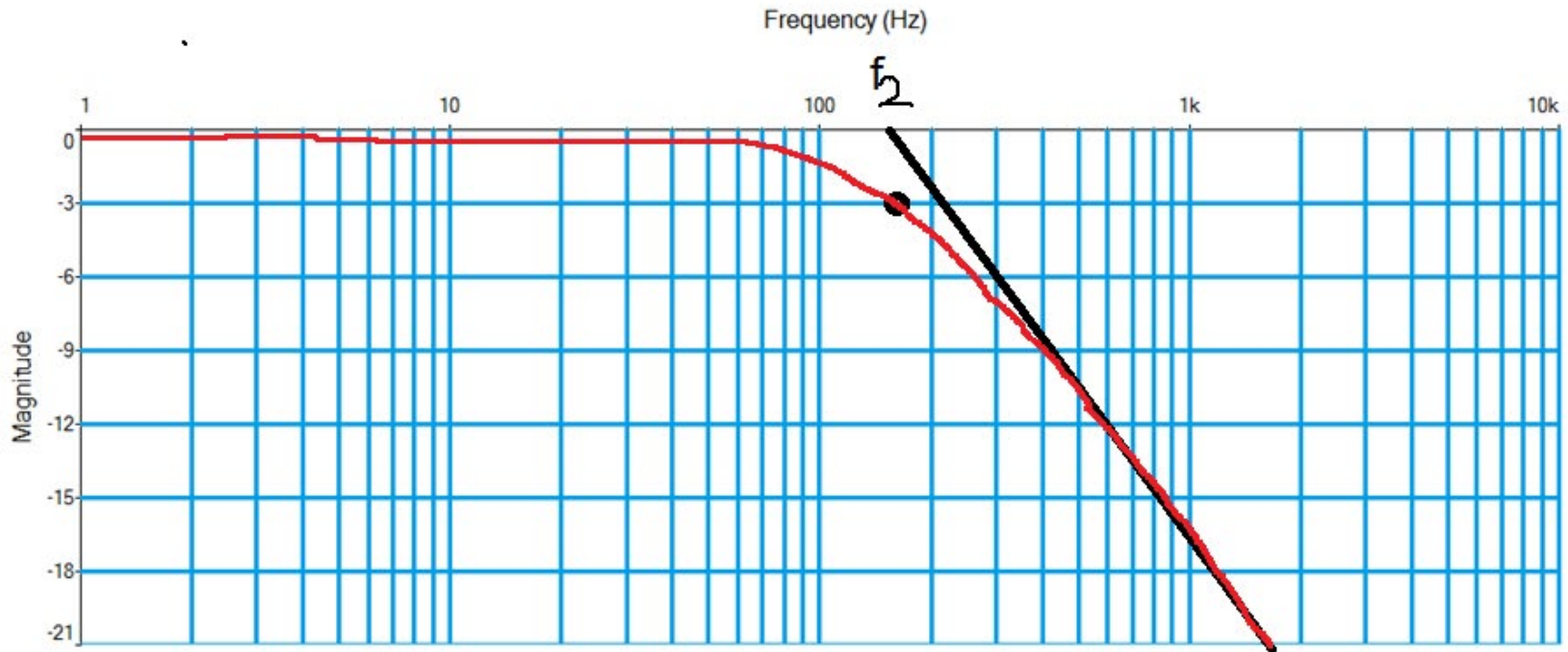

# Low Frequency Analysis

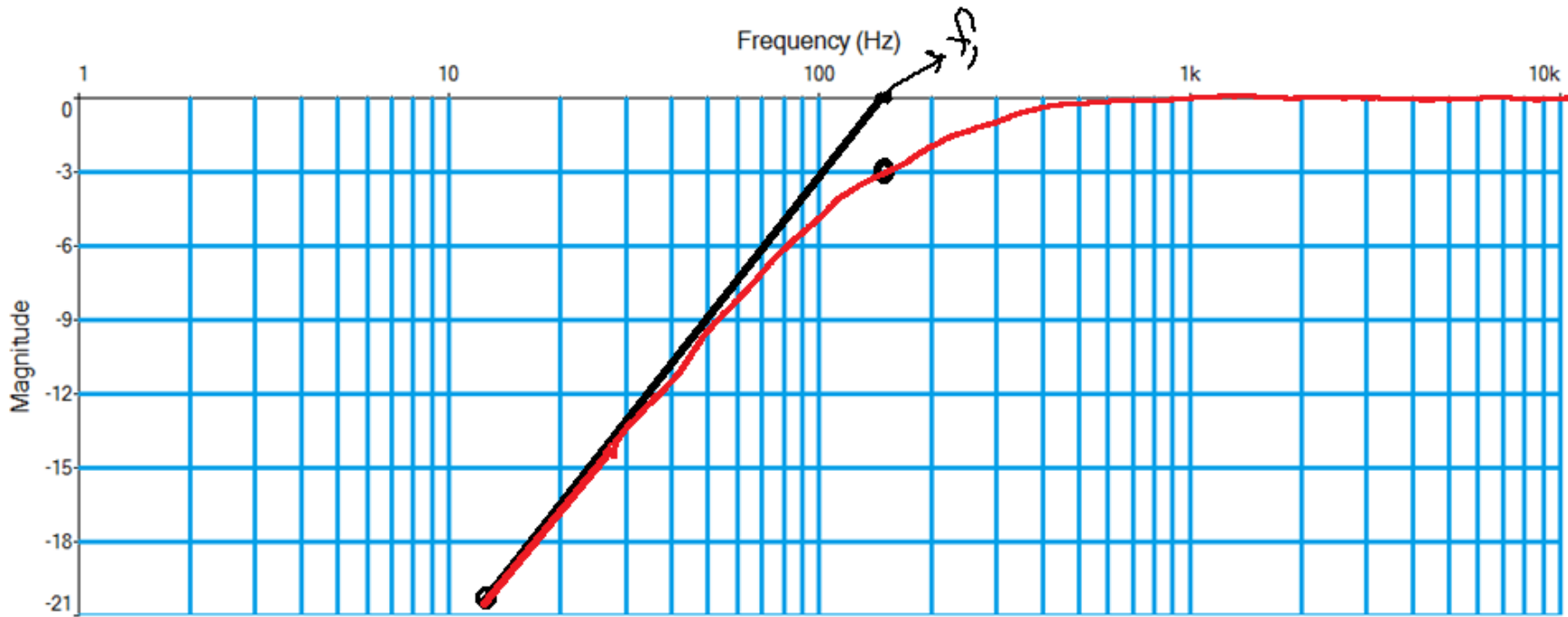



# Filters

---


$$f_1 = \frac{1}{2\pi R_1 C_1}$$



$$f_1 = \frac{1}{2\pi \cdot 1 \cdot 79.577 \Omega \cdot 1 \cdot 10^{-6} F}$$

$$f_1 = 2000 Hz = 2 kHz$$

# Filters

---

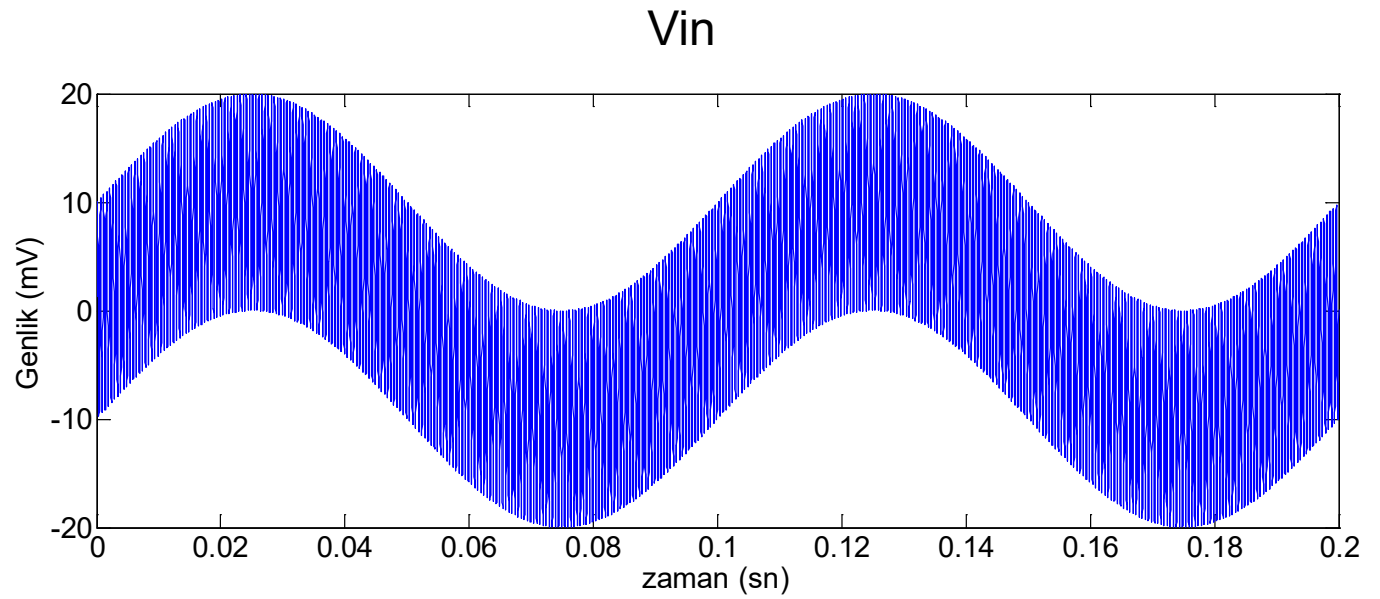

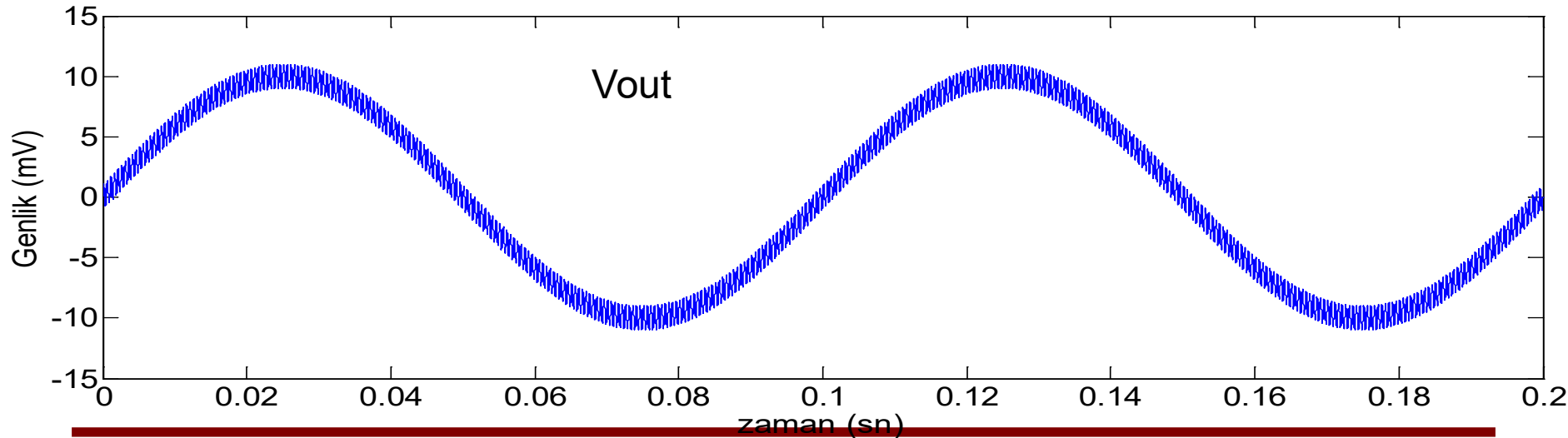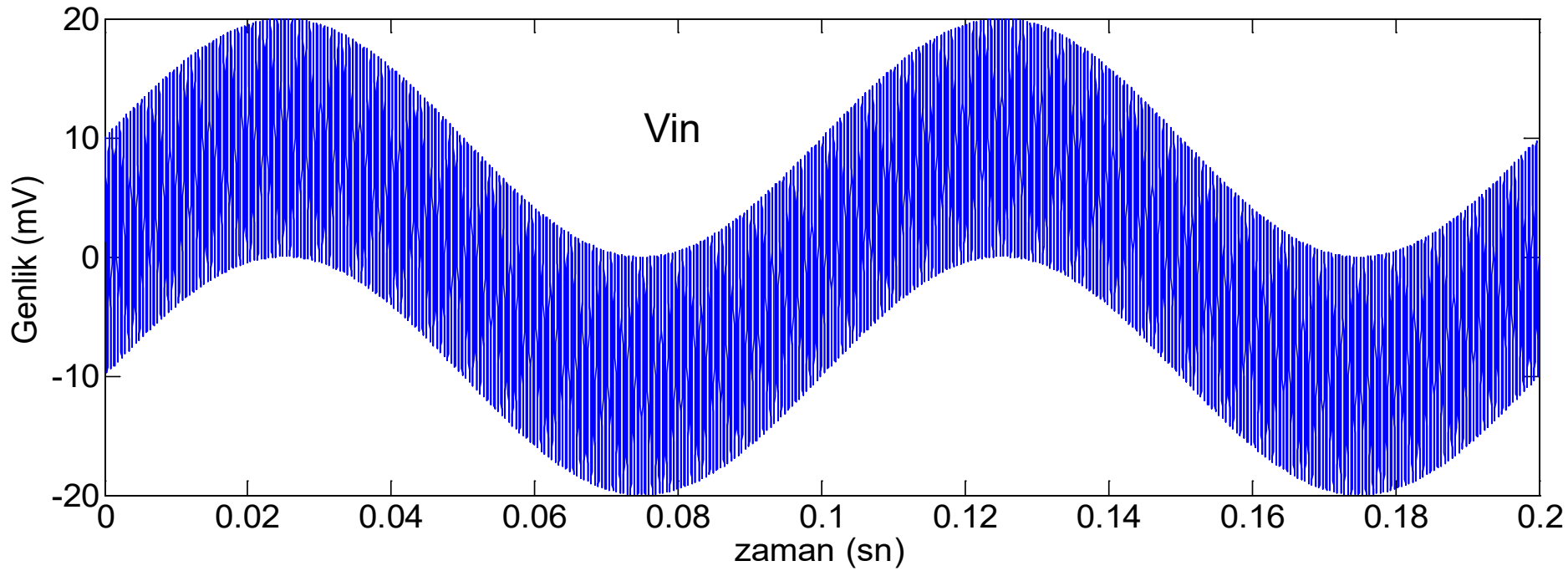

Mehmet YÜKSEKKAYA

# Band Pass Filter

---

$f_r$  = Resonans Frequency  
 $f_L$  = Low cut off frequency  
 $f_H$  = High cut off frequency  
 $BW$  = Bandwidth

$$f_r = \sqrt{f_L \cdot f_H}$$

$$BW = f_H - f_L$$

$$f_L = \sqrt{\frac{BW^2}{4} + f_r^2} - \frac{BW}{2}$$

$$f_H = f_L + BW$$