


EE-202 Electronics-I-

Chapter :9
BJT DC Biasing

Miscellaneous Bias Configurations

Transistor Switching Circuits

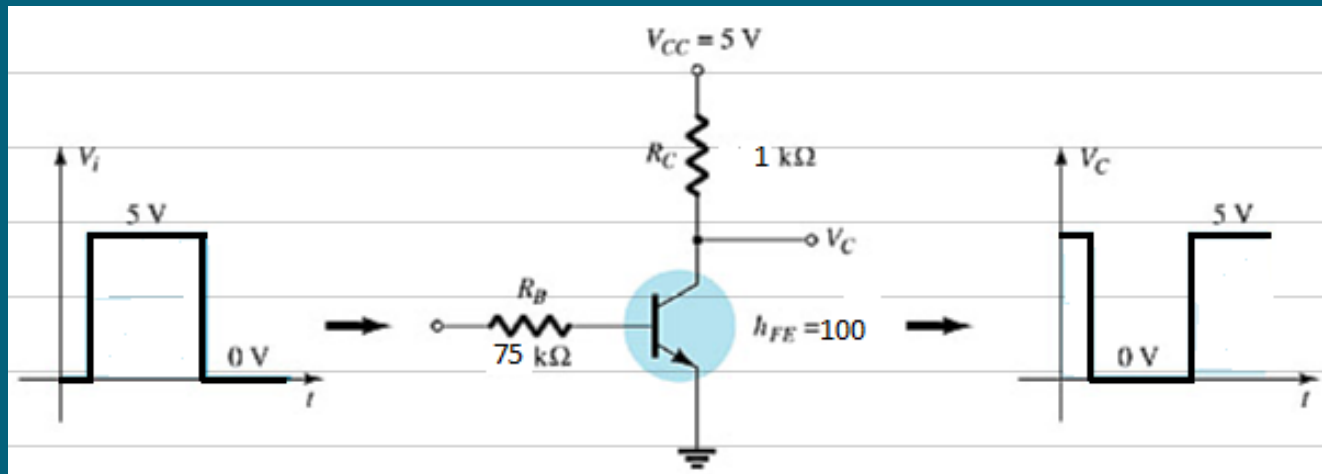Transistors can be used as electronic switches, when only the DC source is applied




Switching Circuit Calculations

Saturation current:

$$I_{C\text{sat}} = \frac{V_{CC}}{R_C}$$

For saturation:
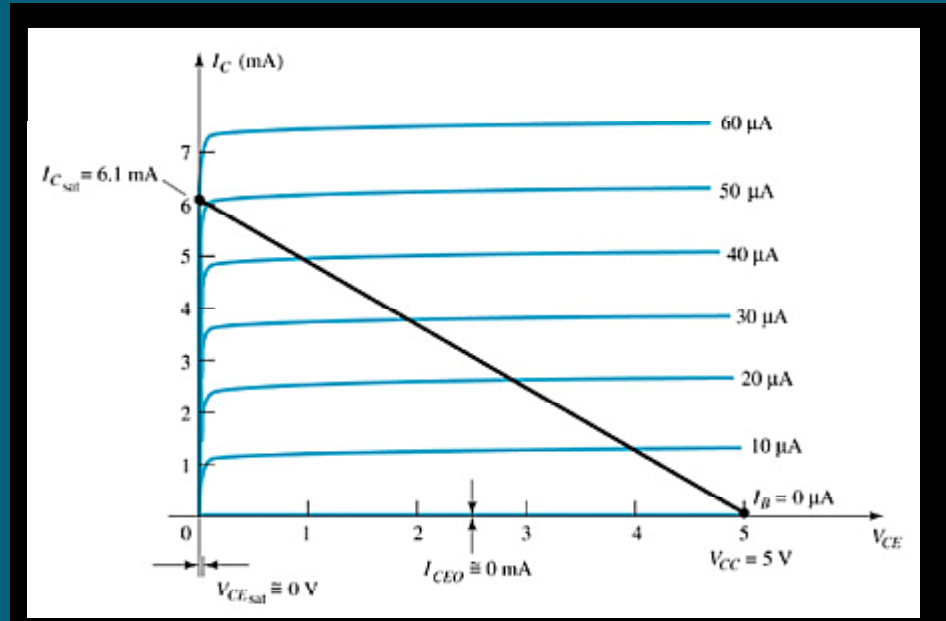
$$I_B > \frac{I_{C\text{sat}}}{\beta_{dc}}$$



Emitter-collector resistance:

saturation

$$R_{\text{sat}} = \frac{V_{CE\text{sat}}}{I_{C\text{sat}}}$$

cutoff


$$R_{\text{cutoff}} = \frac{V_{CC}}{I_{CEO}}$$

Switching Time

Transistor switching times:

$$t_{\text{on}} = t_r + t_d$$

$$t_{\text{off}} = t_s + t_f$$

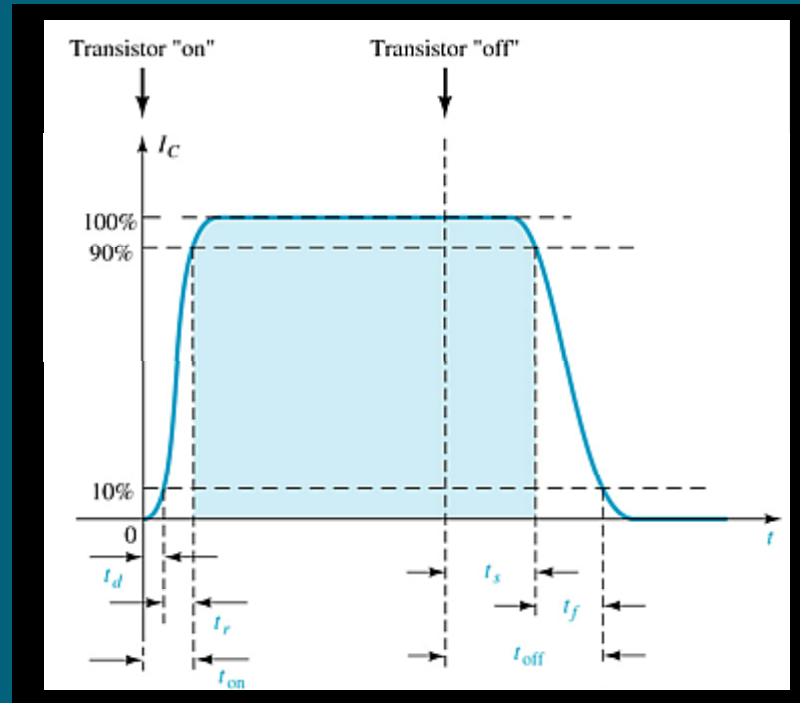

Troubleshooting Hints

- **Approximate voltages**
 - $V_{BE} \cong 0.7 \text{ V}$ for silicon transistors
 - $V_{CE} \cong 25\% \text{ to } 75\% \text{ of } V_{CC}$
- **Open and short circuits can be tested with an ohmmeter.**
- **Test the solder joints.**
- **A transistor tester can be used to test the transistor.**

PNP Transistors

The analysis for *pnp* transistor biasing circuits is the same for *npn* transistor circuits. The only difference is the currents are flowing in the opposite direction.