

# **EE-202 Electronics-I-**

## **Chapter 12:**

# **JFET DC Biasing Circuits**

# Common FET Biasing Circuits

## JFET

- Fixed – Bias
- Self-Bias
- Voltage-Divider Bias

## Depletion-Type MOSFET

- Self-Bias
- Voltage-Divider Bias

## Enhancement-Type MOSFET

- Feedback Configuration
- Voltage-Divider Bias

# General Relationships

**For all FETs:**

$$I_G \cong 0A$$

$$I_D = I_S$$

**For JFETs and depletion-type MOSFETs:**

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

**For enhancement-type MOSFETs:**

$$I_D = k(V_{GS} - V_T)^2$$

# JFETs

**JFETs are different from BJTs as;**

- **Nonlinear relationship between input ( $V_{GS}$ ) and output ( $I_D$ )**
- **JFETs , voltage controlled  
BJTs, current controlled devices**

# Fixed-Bias Configuration


$$V_{DS} = V_{DD} - I_D R_D$$

$$V_S = 0V$$


$$V_C = V_{DS}$$

$$V = V_{GS}$$

$$V_{GS} = -V_{GG}$$

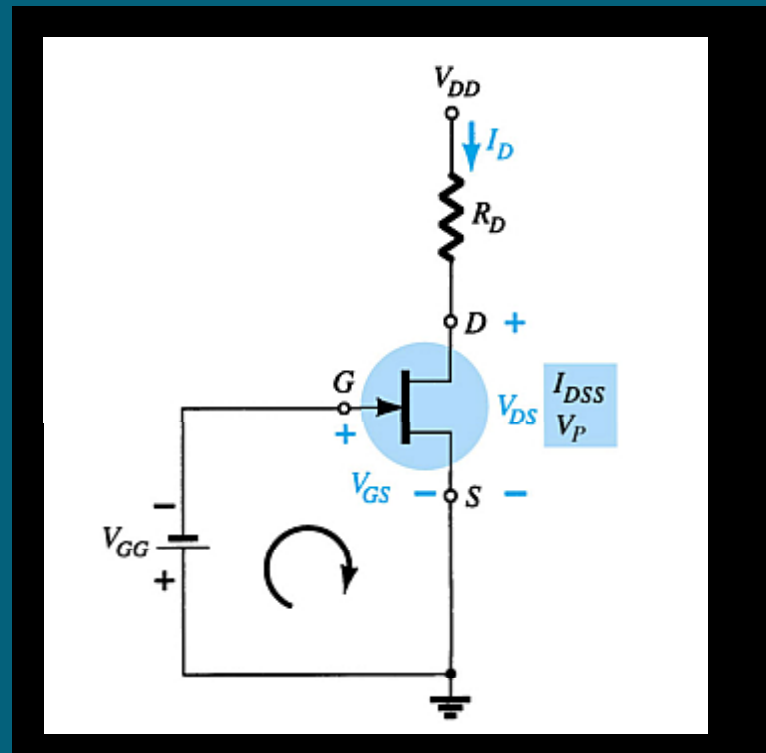

# Self-Bias Configuration

 


# Self-Bias Calculations

$$V_{GS} = -I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

$$V_S = I_D R_S$$


$$V_D = V_{DS} + V_S = V_{DD} - V_{RD}$$

 
 
# Voltage-Divider Bias

$$I_G = 0A$$

- In BJTs,  $I_B$  affected  $I_C$
- in FETs,  $V_{GS}$  controls  $I_D$ .





# Voltage-Divider Bias Calculations

$V_G$  is calculated by the voltage divider resistor  $R_2$ :

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

By using Kirchhoff's Law:

$$V_{GS} = V_G - I_D R_S$$

By using Q-point values, the other variables in the voltage-divider bias circuit can be calculated as;

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_D = V_{DD} - I_D R_D$$

$$V_S = I_D R_S$$

$$I_{R1} = I_{R2} = \frac{V_{DD}}{R_1 + R_2}$$

