


# **EE-202 Electronics-I-**

## **Chapter 13:**

# **MOSFET DC Biasing Circuits**
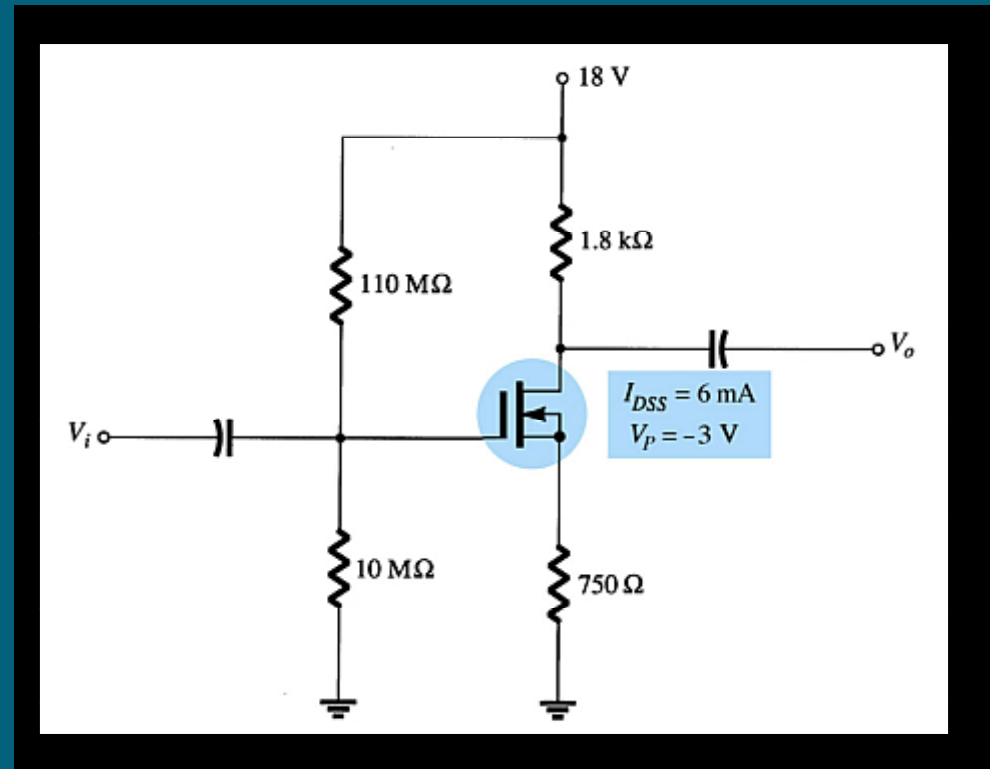
## Depletion-type MOSFET bias circuits

Depletion-type MOSFETs can operate with positive values of  $V_{GS}$  and  $I_D$  values that exceed  $I_{DSS}$ .



# Self-Bias

## Step 1

Plot a line for


- $V_{GS} = V_G, I_D = 0$
- $I_D = V_G/R_S, V_{GS} = 0$

## Step 2

Plot the transfer curve by plotting  $I_{DSS}, V_P$  and calculated values of  $I_D$

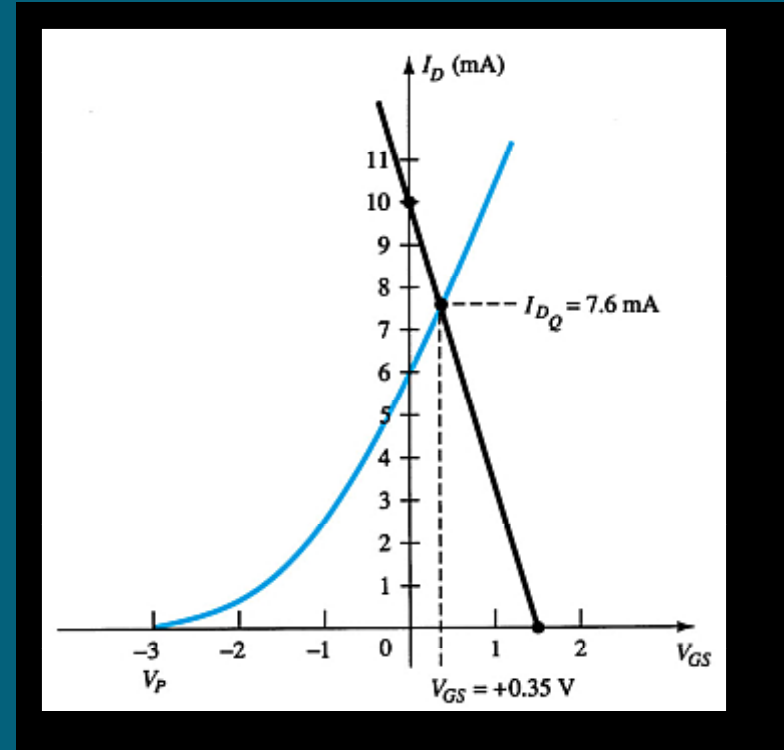
## Step 3

The Q-point is located where the line intersects the transfer curve


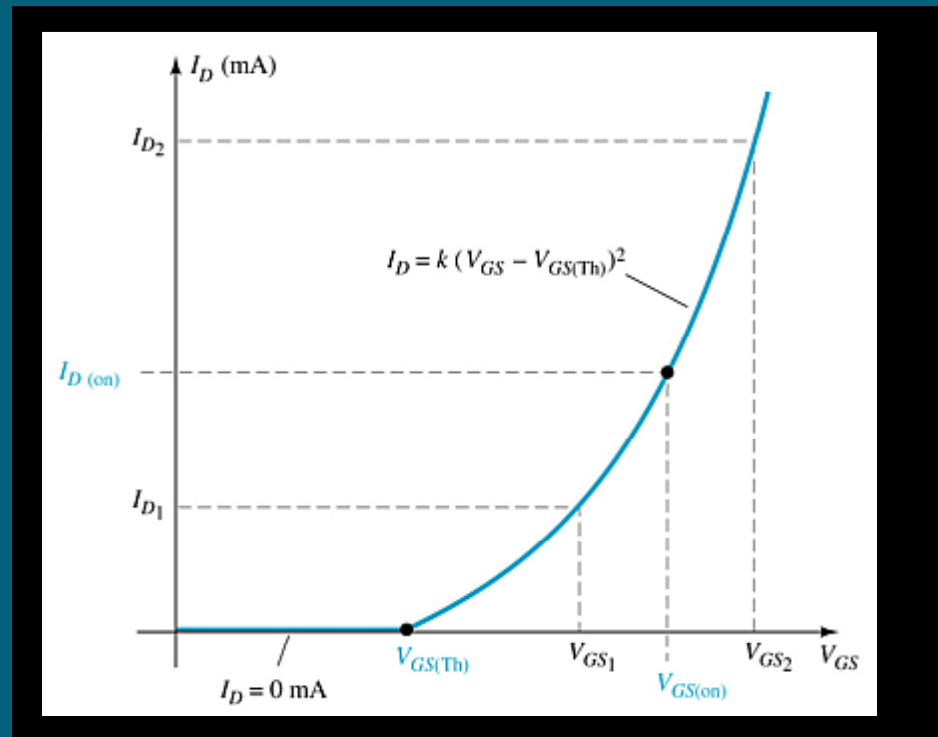
# Enhancement-Type MOSFET

The transfer characteristic for the enhancement-type MOSFET is different from JFET or depletion-type MOSFET.




# Feedback Biasing

$$I_G = 0A, V_{RG} = 0V$$

$$\text{So } V_{DS} = V_{GS}$$
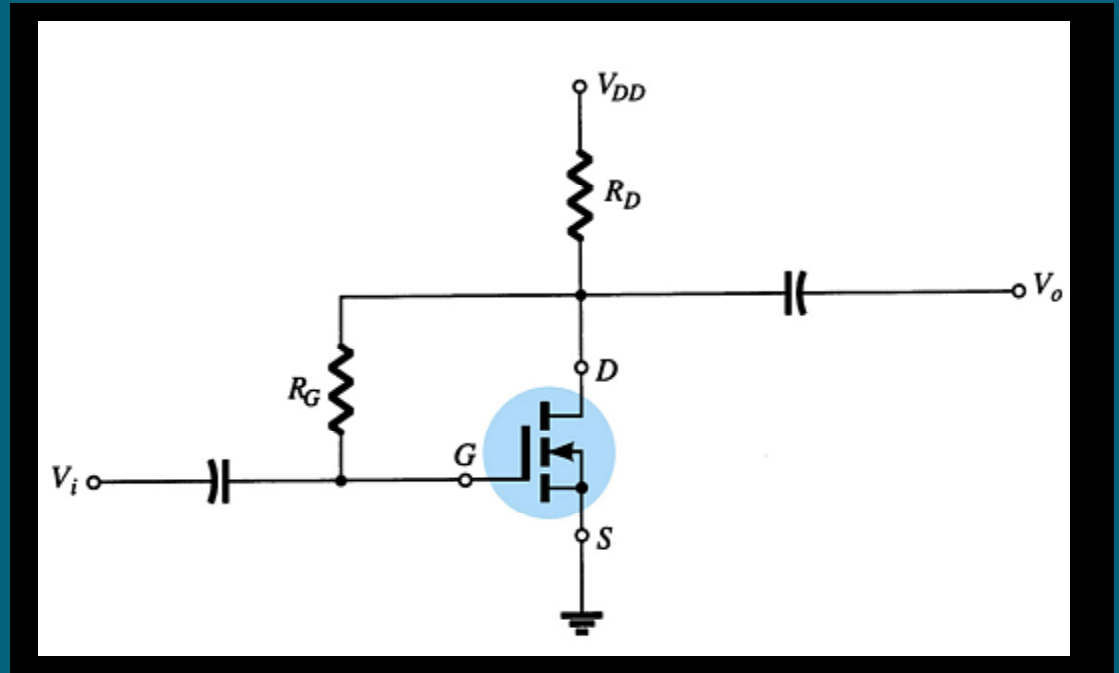
$$\text{And } V_{GS} = V_{DD} - I_D R_D$$




# Voltage-Divider Biasing

Plot the line and the transfer curve to find the Q-point. The equations are:

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

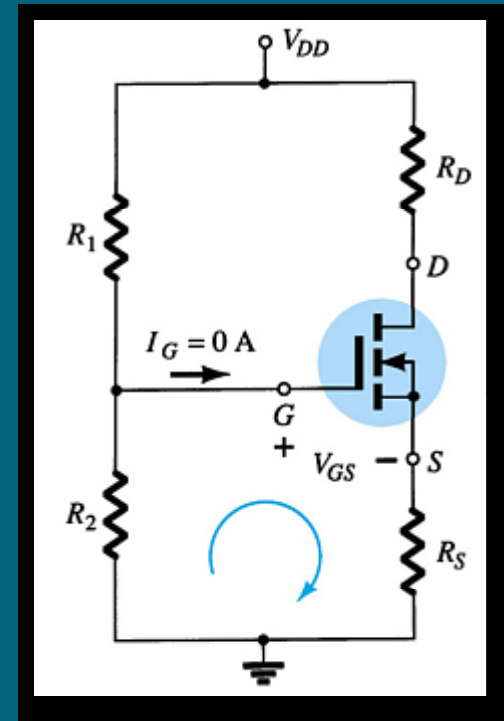

# *p*-Channel FETs

*p*-channel FETs use the same calculations and graphs with *n*-channel, except that the voltage polarities and current directions are the opposite.