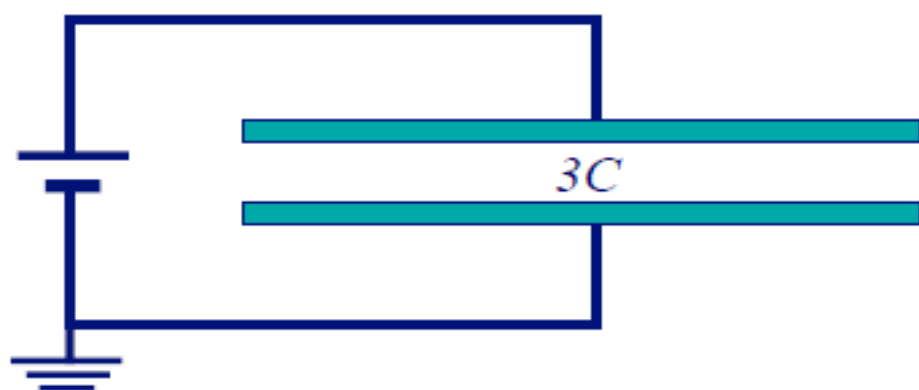


Physics 122: Electricity & Magnetism – Lecture 9 Capacitance (continued)



Prof.Dr. Barış Akaoglu

Capacitors in Parallel


□ No difference between



and

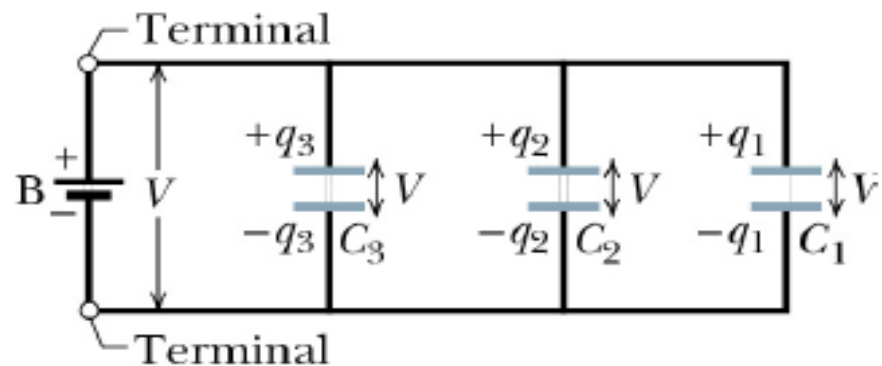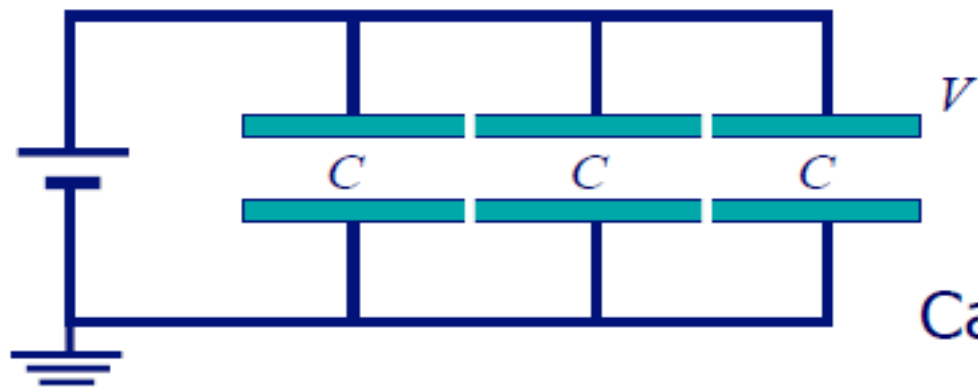

(a)

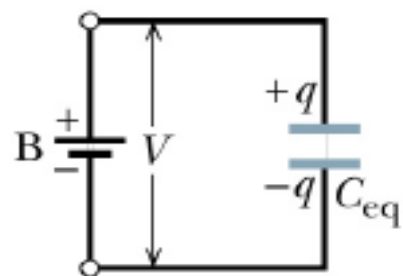


(b)

Capacitors in parallel: $C_{eq} = \sum_{j=1}^n C_j$


Capacitors in Series

- There *is* a difference between

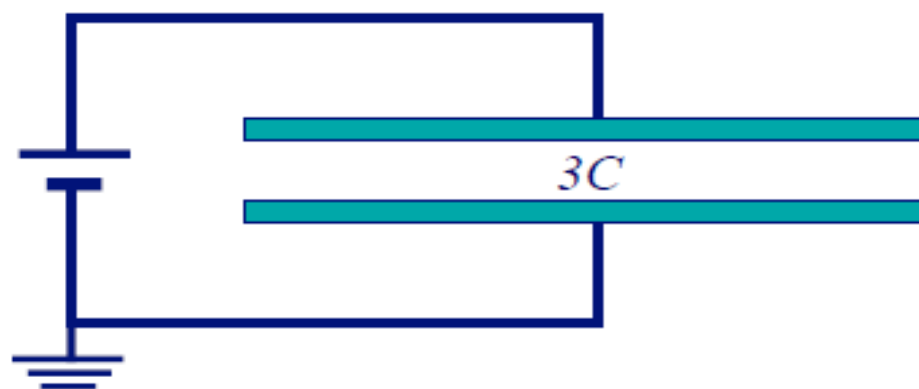

- Charge on lower plate of one and upper plate of next are equal and opposite. (show by gaussian surface around the two plates).
- Total charge is q , but voltage on each is only $V/3$.

and

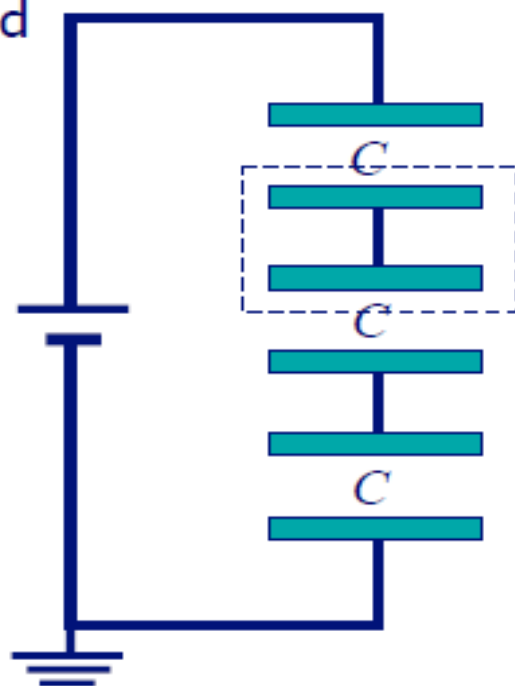

Capacitors in series:

$$\frac{1}{C_{eq}} = \sum_{j=1}^n \frac{1}{C_j}$$

Capacitors in Series

- To see the series formula, consider the individual voltages across each capacitor



$$V_1 = \frac{q}{C_1}, V_2 = \frac{q}{C_2}, V_3 = \frac{q}{C_3}$$

- The sum of these voltages is the total voltage of the battery, V


$$V = V_1 + V_2 + V_3 = \frac{q}{C_1} + \frac{q}{C_2} + \frac{q}{C_3}$$

- Since $V/q = 1/C_{eq}$ we have
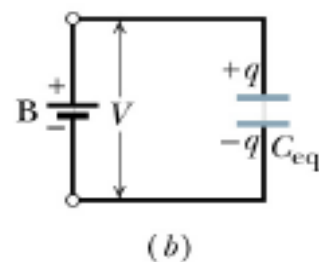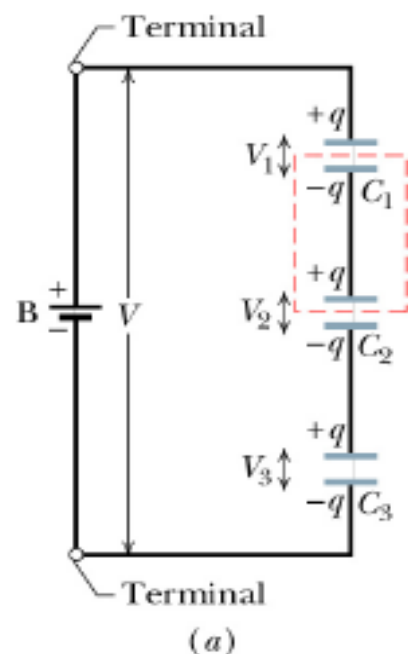
$$\frac{V}{q} = \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$




Example Capacitor Circuit

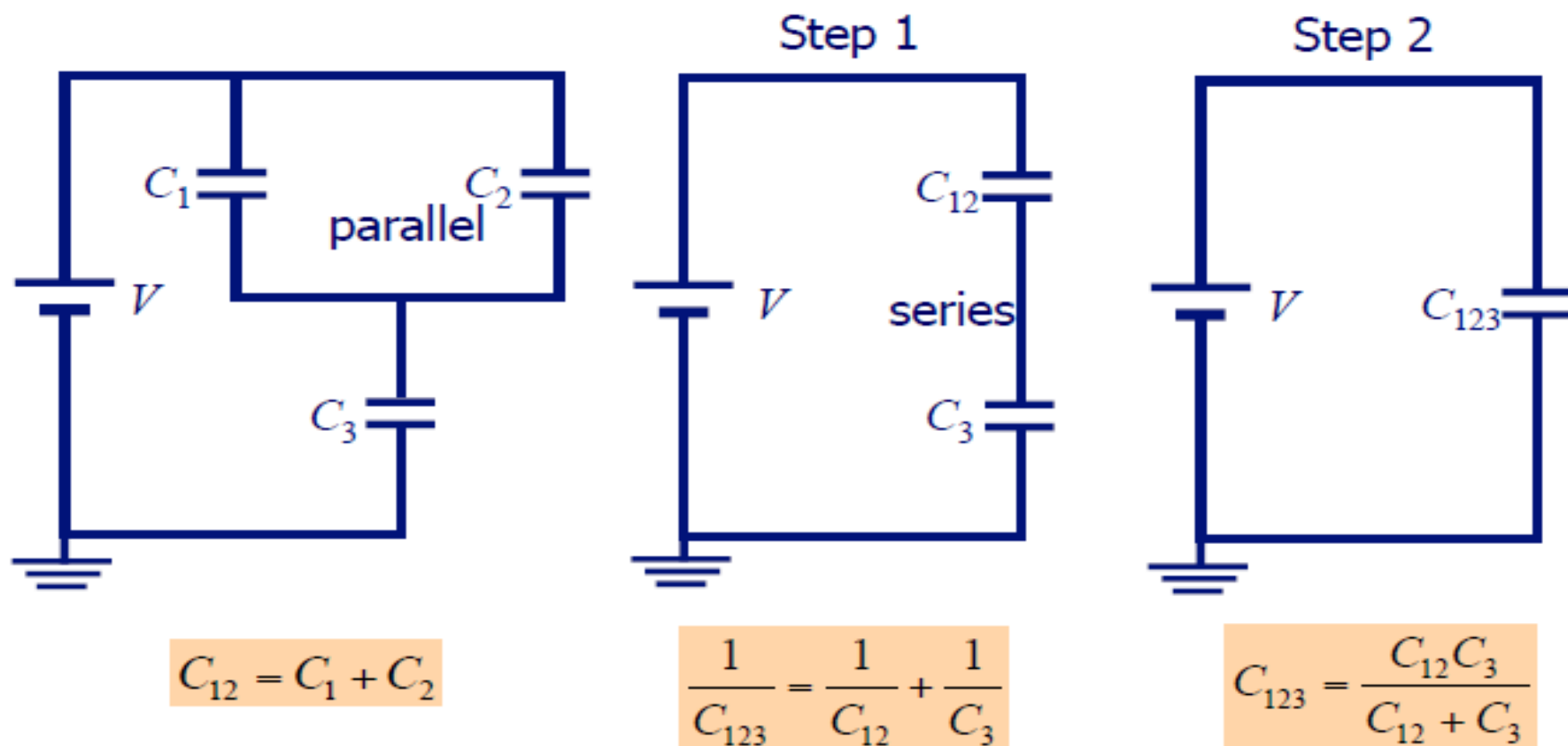


$$C_1 = 12.0 \mu\text{F}, C_2 = 5.3 \mu\text{F}, C_3 = 4.5 \mu\text{F}$$

$$C_{123} = (12 + 5.3)4.5 / (12 + 5.3 + 4.5) \mu\text{F} = 3.57 \mu\text{F}$$

Another Example

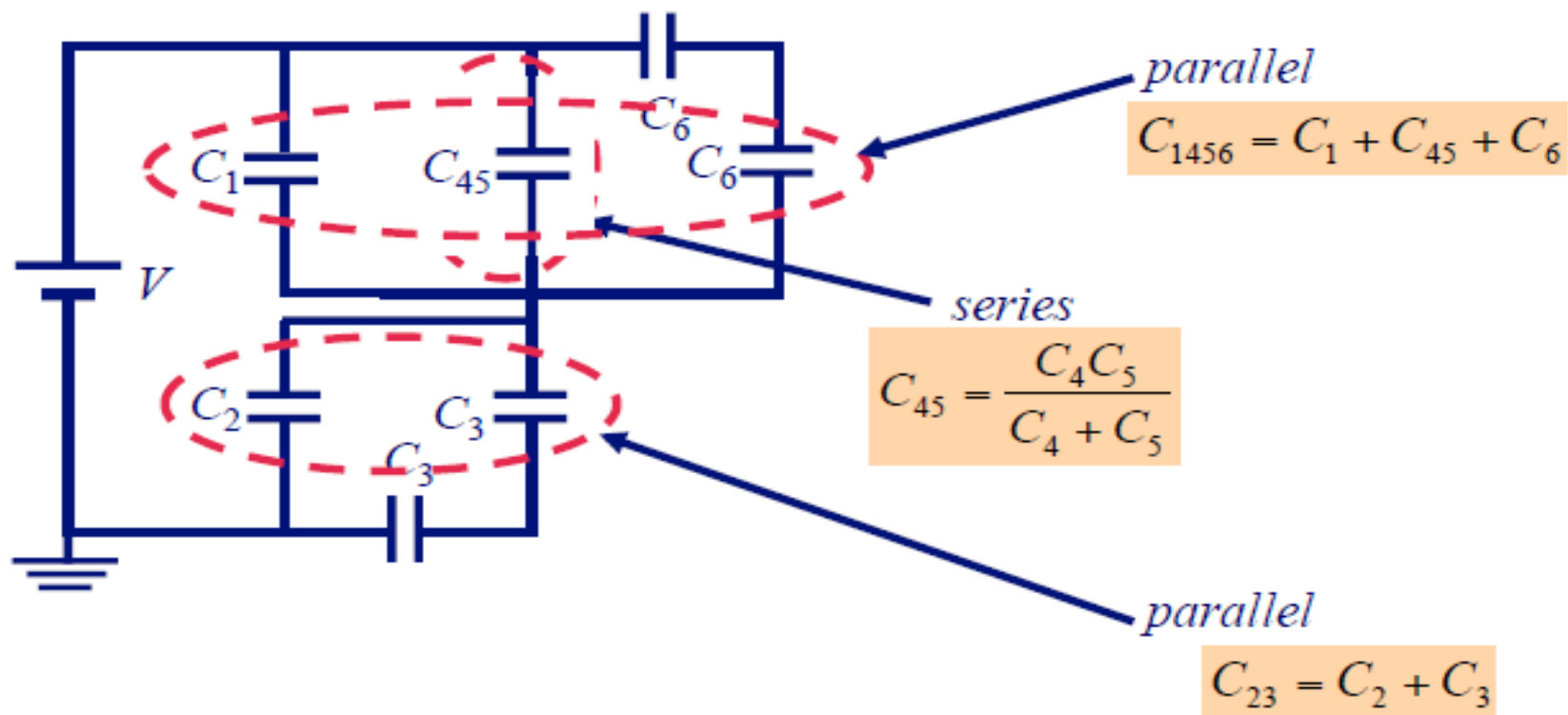

Another Example

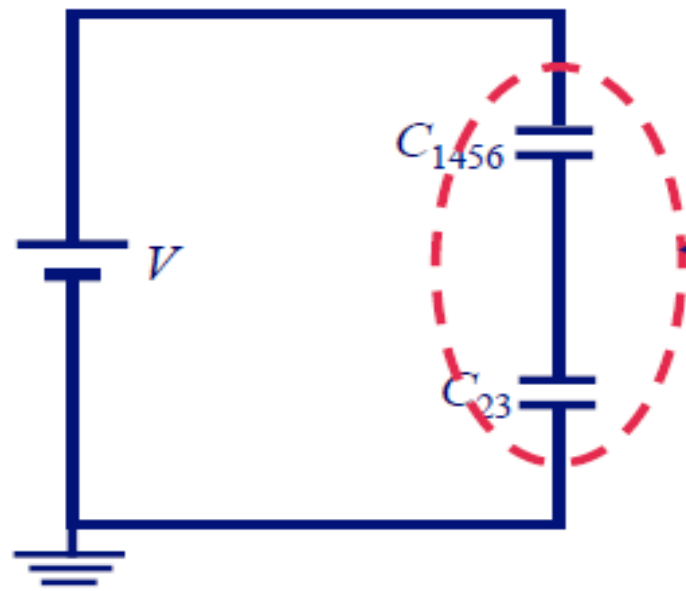

$$C_{45} = \frac{C_4 C_5}{C_4 + C_5}$$

$$C_{1456} = C_1 + C_{45} + C_6$$

$$C_{23} = C_2 + C_3$$

$$C_{123456} = \frac{C_{1456} C_{23}}{C_{1456} + C_{23}}$$

Complete solution

$$C_{123456} = \frac{\left(C_1 + \frac{C_4 C_5}{C_4 + C_5} + C_6 \right) (C_2 + C_3)}{C_1 + \frac{C_4 C_5}{C_4 + C_5} + C_6 + C_2 + C_3}$$


Capacitors Store Energy

- When charges flow from the battery, energy stored in the battery is lost. Where does it go?
- We learned last time that an arrangement of charge is associated with potential energy. One way to look at it is that the charge arrangement stores the energy.
- Recall the definition of electric potential $V = U/q$
- For a distribution of charge on a capacitor, a small element dq will store potential energy $dU = V dq$
- Thus, the energy stored by charging a capacitor from charge 0 to q is

$$U = \frac{1}{C} \int_0^q q' dq' = \frac{q^2}{2C} = \frac{1}{2} CV^2$$

Movie 1

Movie 2

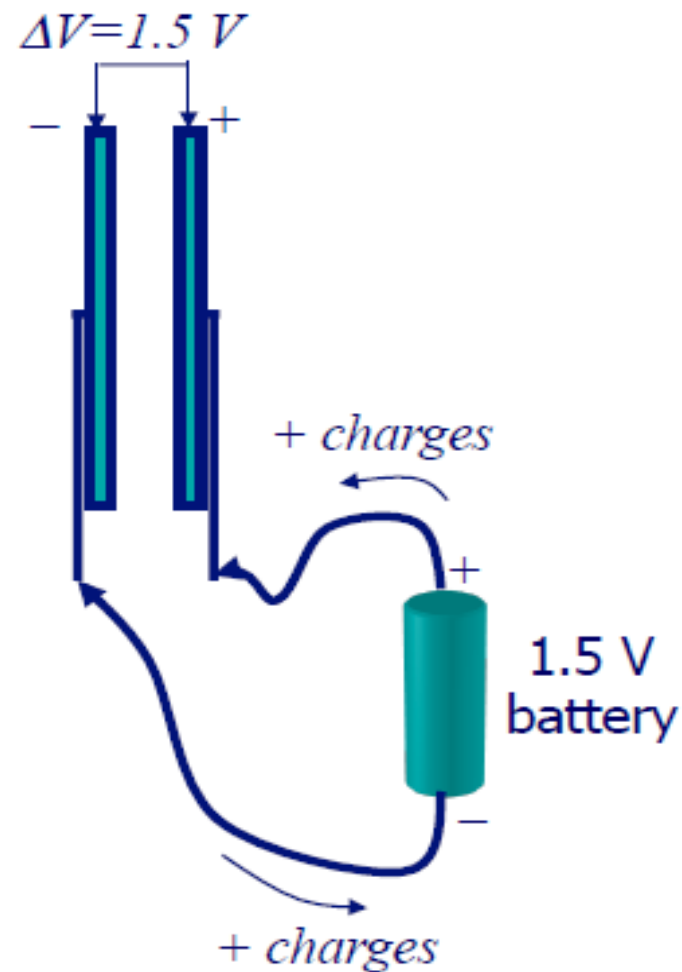

Capacitors Store Energy

- Another way to think about the stored energy is to consider it to be stored in the electric field itself.
- The total energy in a parallel plate capacitor is

$$U = \frac{1}{2} CV^2 = \frac{\epsilon_0 A}{2d} V^2$$

- The volume of space filled by the electric field in the capacitor is $vol = Ad$, so the *energy density* is

$$u = \frac{U}{vol} = \frac{\epsilon_0 A}{2dAd} V^2 = \frac{1}{2} \epsilon_0 \left(\frac{V}{d} \right)^2$$

- But $V = -\int \vec{E} \cdot d\vec{s} = Ed$ for a parallel plate capacitor, so

$$u = \frac{1}{2} \epsilon_0 E^2$$

Energy stored in electric field

Dielectrics


- You may have wondered why we write ϵ_0 (permittivity of free space), with a little zero subscript. It turns out that other materials (water, paper, plastic, even air) have different permittivities $\epsilon = \kappa\epsilon_0$. The κ is called the *dielectric constant*, and is a unitless number. For air, $\kappa = 1.00054$ (so ϵ for air is for our purposes the same as for “free space.”)
- In all of our equations where you see ϵ_0 , you can substitute $\kappa\epsilon_0$ when considering some other materials (called dielectrics).
- The nice thing about this is that we can increase the capacitance of a parallel plate capacitor by filling the space with a dielectric:

$$C' = \frac{\kappa\epsilon_0 A}{d} = \kappa C$$



Material	Dielectric Constant κ	Dielectric Strength (kV/mm)
Air	1.00054	3
Polystyrene	2.6	24
Paper	3.5	16
Transformer Oil	4.5	
Pyrex	4.7	14
Ruby Mica	5.4	
Porcelain	6.5	
Silicon	12	
Germanium	16	
Ethanol	25	
Water (20° C)	80.4	
Water (50° C)	78.5	
Titania Ceramic	130	
Strontium Titanate	310	8

What Happens When You Insert a Dielectric?

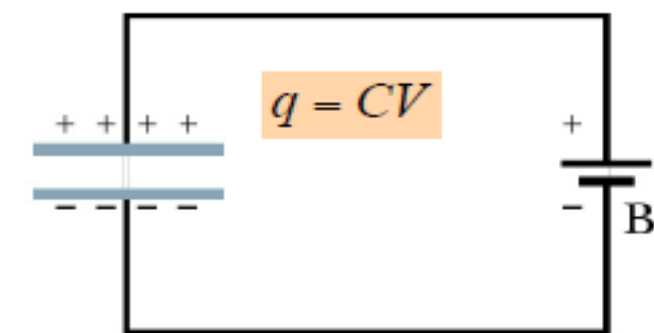
- With battery attached, $V = \text{const}$, so more charge flows to the capacitor



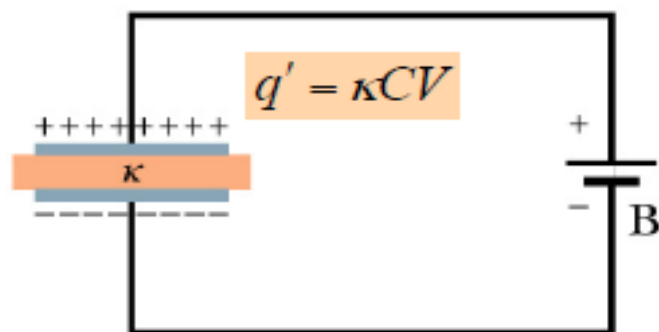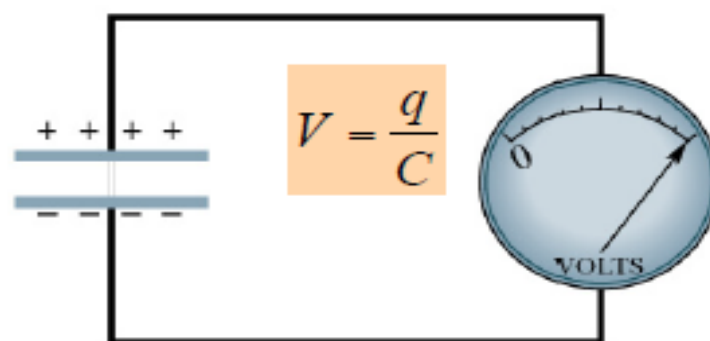- With battery disconnected, $q = \text{const}$, so voltage (for given q) drops.




$V = \text{a constant}$

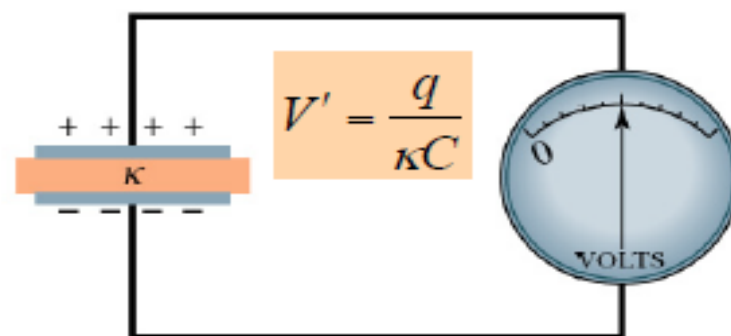


$q = \text{a constant}$

What Does the Dielectric Do?


- A dielectric material is made of molecules.
- Polar dielectrics already have a dipole moment (like the water molecule).
- Non-polar dielectrics are not naturally polar, but actually stretch in an electric field, to become polar.
- The molecules of the dielectric align with the applied electric field in a manner to oppose the electric field.
- This reduces the electric field, so that the net electric field is less than it was for a given charge on the plates.
- This lowers the potential (case b of the previous slide).
- If the plates are attached to a battery (case a of the previous slide), more charge has to flow onto the plates.

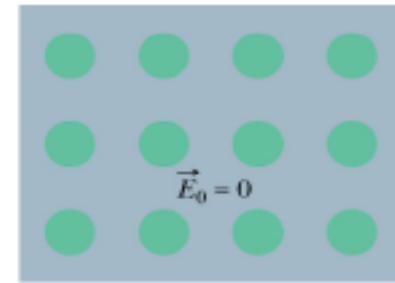

(a)

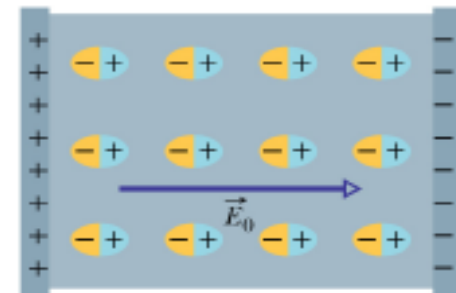


(b)

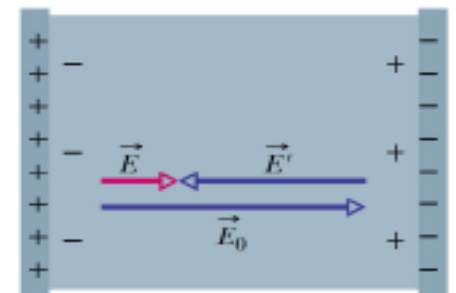

(c)



A Closer Look

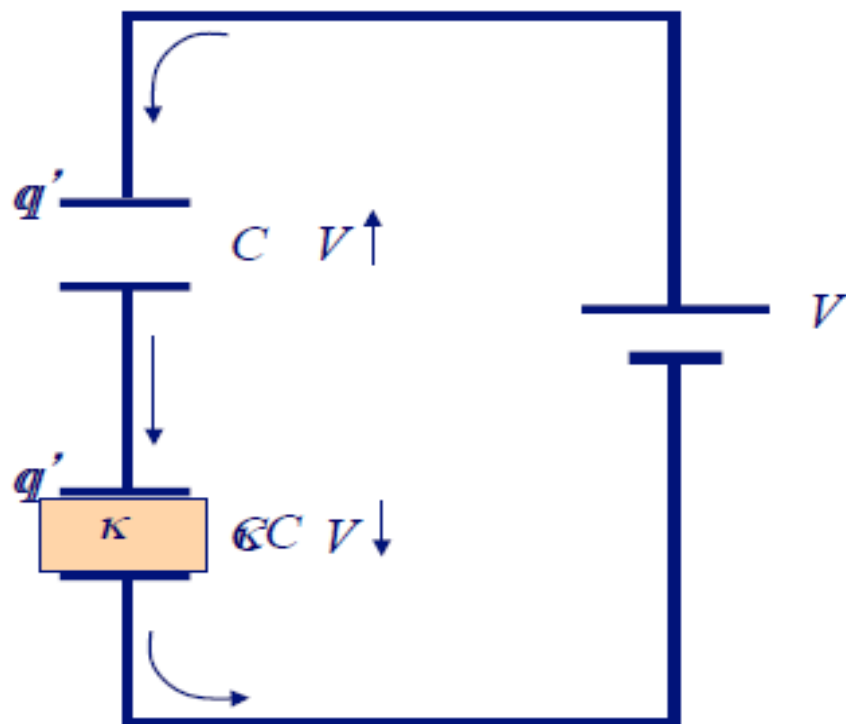- Insert dielectric
- Capacitance goes up by κ
- Charge increases
- Charge on upper plate comes from upper capacitor, so its charge also increases.
- Since $q' = CV_1$ increases on upper capacitor, V_1 must increase on upper capacitor.
- Since total $V = V_1 + V_2 = \text{constant}$, V_2 must decrease.



Dielectrics and Gauss' Law

- Gauss' Law holds without modification, but notice that the charge enclosed by our gaussian surface is less, because it includes the induced charge q' on the dielectric.
- For a given charge q on the plate, the charge enclosed is $q - q'$, which means that the electric field must be smaller. The effect is to weaken the field.
- When attached to a battery, of course, more charge will flow onto the plates until the electric field is again E_0 .

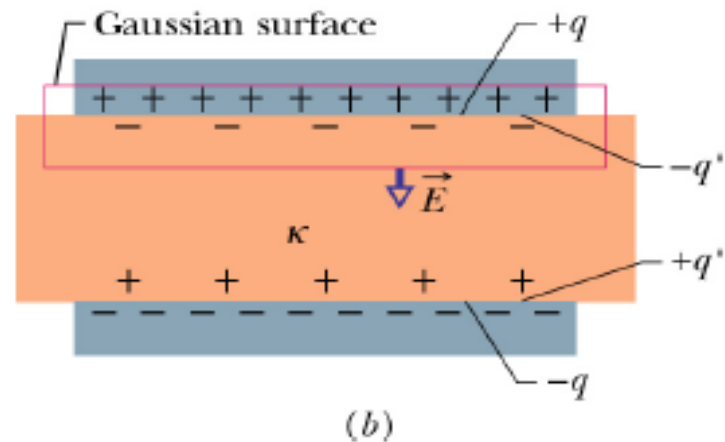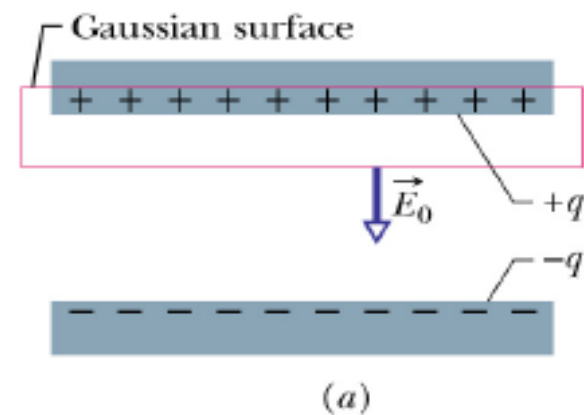

Summary

- Capacitance says how much charge is on an arrangement of conductors for a given potential. $q = CV$

- Capacitance depends only on geometry

- Parallel Plate Capacitor
- Cylindrical Capacitor
- Spherical Capacitor
- Isolated Sphere

$$C = \frac{\epsilon_0 A}{d}$$

$$C = 2\pi\epsilon_0 \frac{L}{\ln(b/a)}$$

$$C = 4\pi\epsilon_0 \frac{ab}{b-a}$$

$$C = 4\pi\epsilon_0 R$$

- Units, F (farad) = C²/Nm or C/V (note $\epsilon_0 = 8.85 \text{ pF/m}$)

- Capacitors in parallel

$$C_{eq} = \sum_{j=1}^n C_j$$

in series

$$\frac{1}{C_{eq}} = \sum_{j=1}^n \frac{1}{C_j}$$

- Energy and energy density stored by capacitor

$$U = \frac{1}{2} CV^2$$

$$u = \frac{1}{2} \epsilon_0 E^2$$

- Dielectric constant increases capacitance due to induced, opposing field. $C' = \kappa C$ κ is a unitless number.