

EEE104

Circuit Analysis I

Ankara University

Faculty of Engineering

Electrical and Electronics Engineering Department

Circuit Elements


EEE104 Circuit Analysis I


Lecture 3

Agenda

- Circuit Model
- Kirchhoff's Laws


- A Circuit Model with a Switch

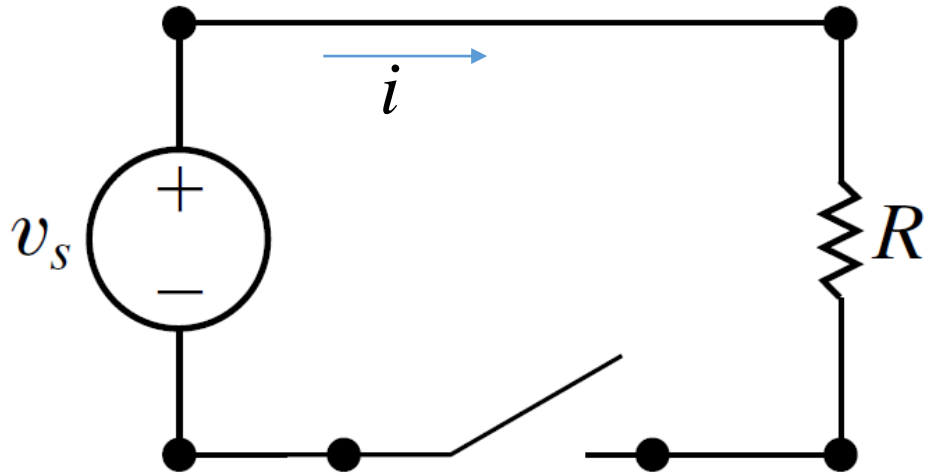

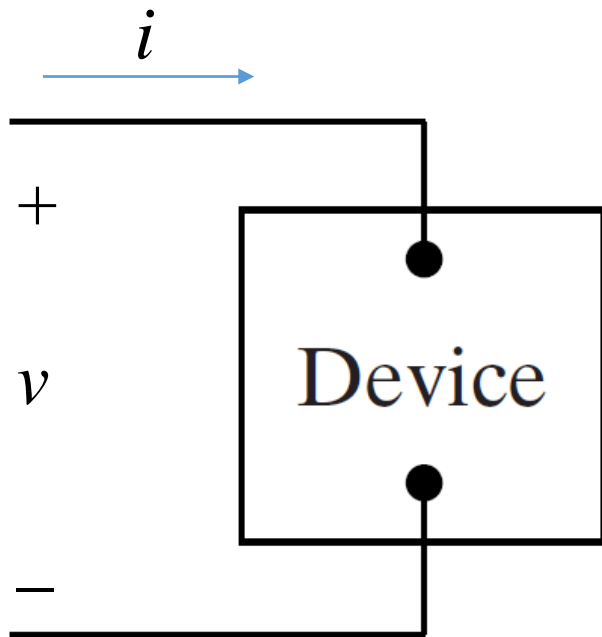


| Measurements | |
|-----------------|-----------------|
| Current (i) | Voltage (v) |
| -5 | -10 |
| 0 | 0 |
| 5 | 10 |
| 10 | 20 |

$$\Rightarrow R = 2 \Omega$$

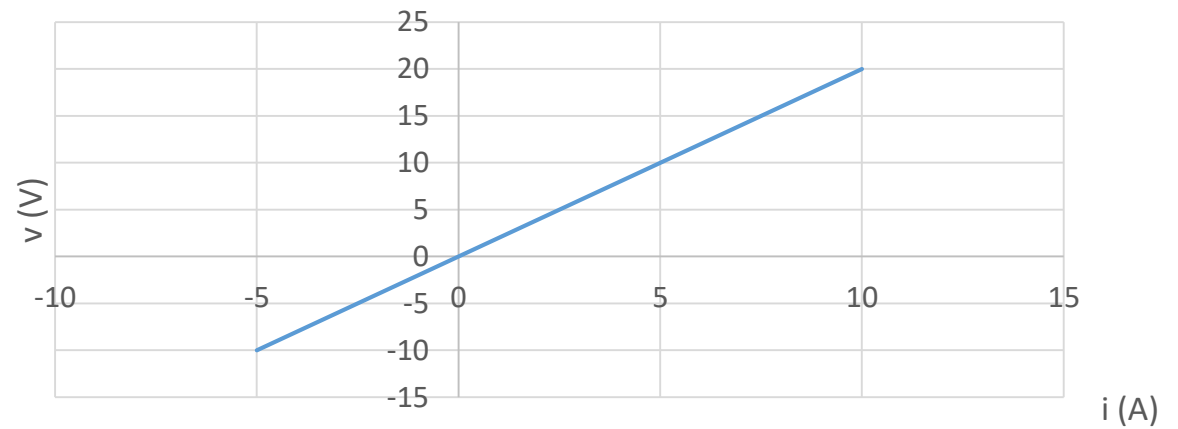

Kirchhoff's Laws

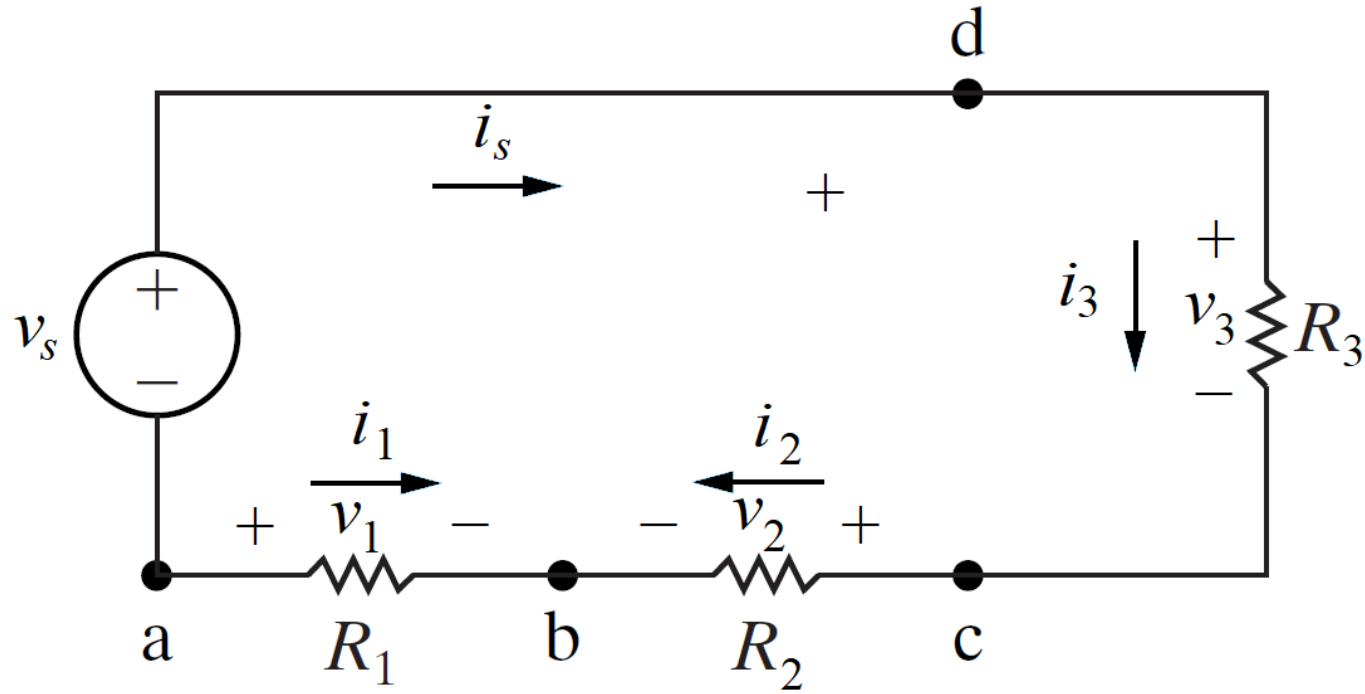

a, b, c, d: Nodes

$$v_1 = i_1 R_1$$

$$v_2 = i_2 R_2$$

$$v_3 = i_3 R_3$$

- Kirchhoff's Current Law

For a node;

(a) Total of incoming currents are zero [Incoming (+), outgoing (-)]

or

(b) Total of outgoing currents are zero [Incoming (-), outgoing (+)]

or

(c) Total of incoming currents equals total of outgoing currents [Incoming (+), outgoing (+)]

- Node a: $-i_1 - i_s = 0$

- Node b: $i_1 + i_2 = 0$

- Node c: $-i_2 + i_3 = 0$

- Node d: $i_s - i_3 = 0$

[Considering (a)]

- Kirchhoff's Voltage Law

Total of voltages in a mesh (closed loop) is zero

$$v_3 + v_2 - v_1 - v_s = 0$$

Reference

- Electric Circuits, Tenth Edition, James W. Nilsson, Susan A. Riedel
Pearson, 2015