

# EEE104

# Circuit Analysis I

Ankara University

Faculty of Engineering

Electrical and Electronics Engineering Department

# Circuit Analysis Techniques


EEE104 Circuit Analysis I

Lecture 6

# Agenda

- Node-Voltage Method
- Mesh-Current Method
- Source Transformations
- Thevenin and Norton Equivalent Circuits
- Maximum Power Transfer
- Superposition

- Node-Voltage Method

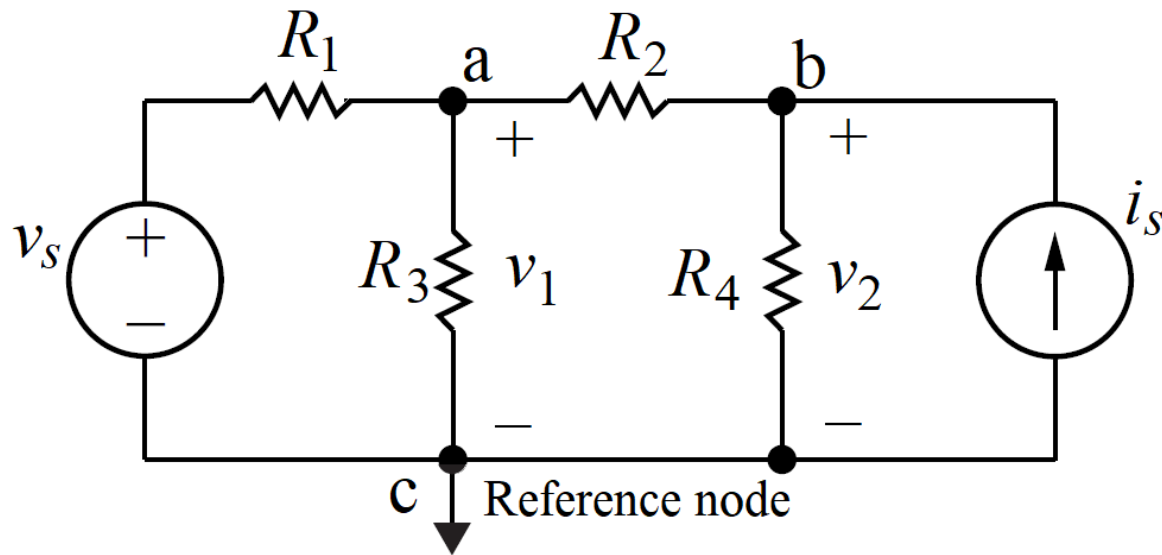

Essential Nodes: a, b, c  
(c is chosen as reference node)


KCL for node a:

$$\frac{v_1 - v_s}{R_1} + \frac{v_1}{R_3} + \frac{v_1 - v_2}{R_2} = 0$$

KCL for node b:

$$\frac{v_2 - v_1}{R_2} + \frac{v_2}{R_4} - i_s = 0$$

- Mesh-Current Method

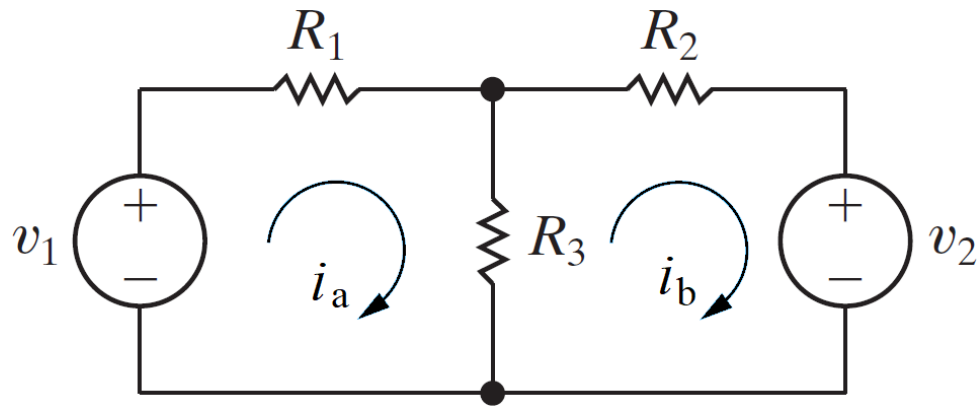


KVL for the mesh @ the left:

$$-v_1 + i_a R_1 + (i_a - i_b) R_3 = 0$$


KVL for the mesh @ the right:

$$v_2 + (i_b - i_a) R_3 + i_b R_2 = 0$$


- Source Transformations

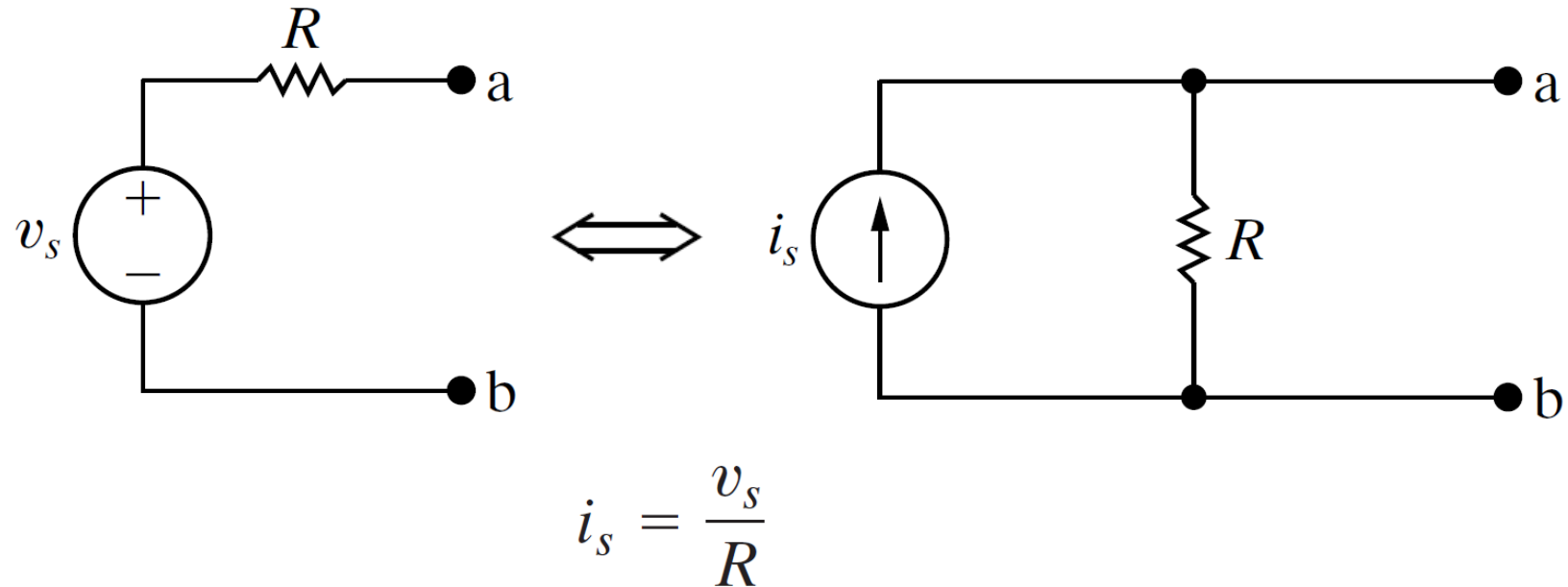

- Thevenin Equivalent Circuit

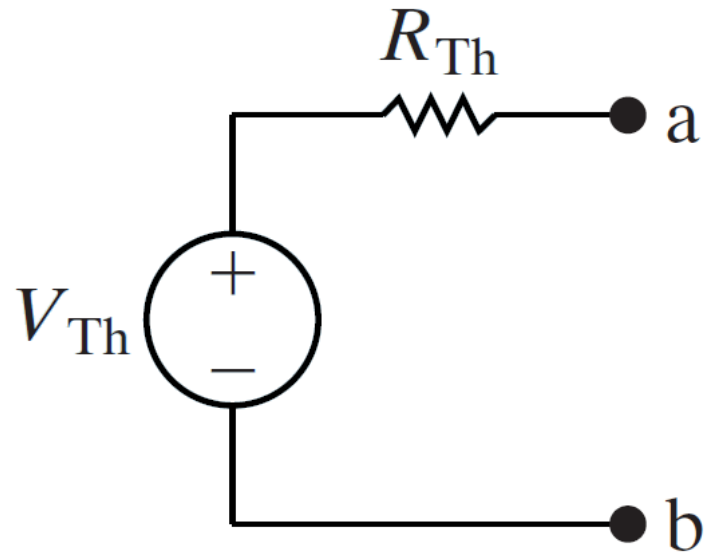


- Norton Equivalent Circuit

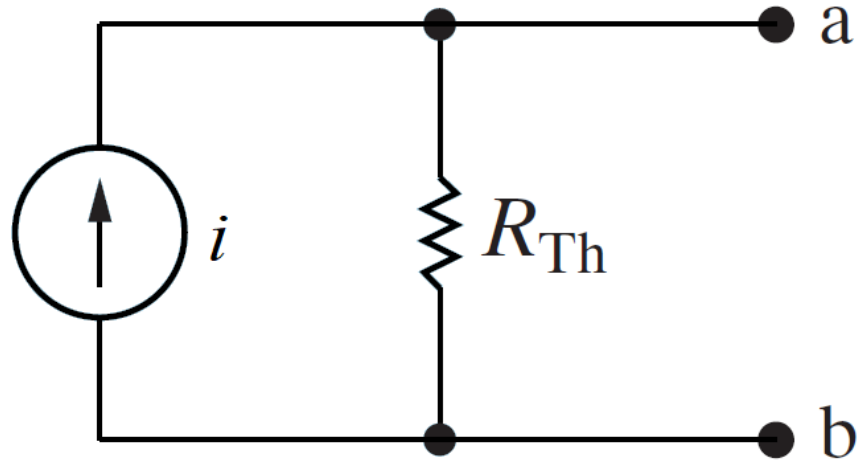



- Maximum Power Transfer

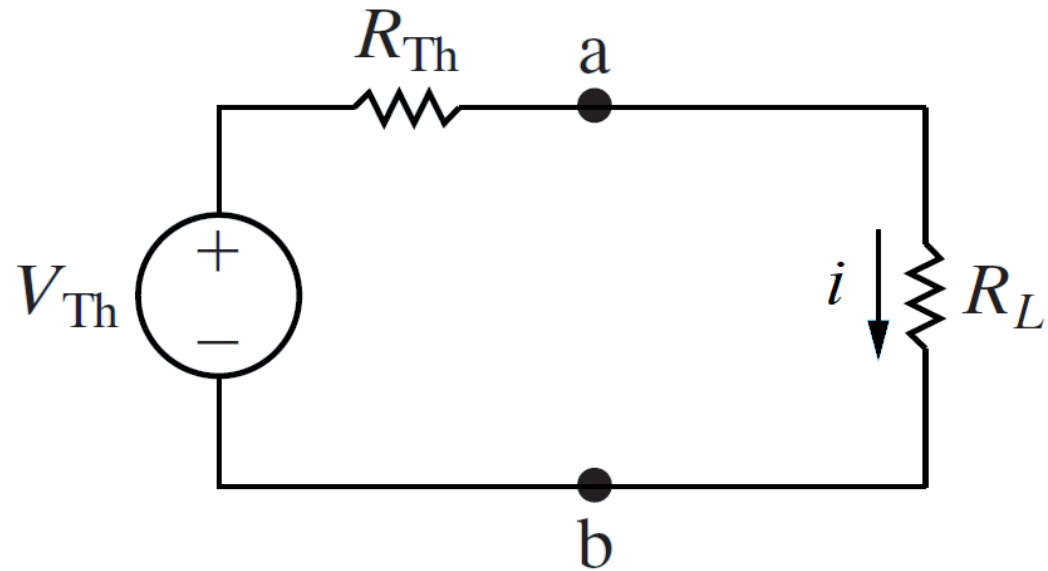

$$R_L = R_{Th}$$
$$p_{\max} = \frac{V_{Th}^2 R_L}{(2R_L)^2} = \frac{V_{Th}^2}{4R_L}$$

- Superposition

- Linear Time Invariant System

- \* Applied for more than one independent sources
    - \* Total response is the sum of individual responses

# Reference

- Electric Circuits, Tenth Edition, James W. Nilsson, Susan A. Riedel  
Pearson, 2015