

# EEE201

# Circuit Analysis II

Ankara University

Faculty of Engineering

Electrical and Electronics Engineering Department

# Sinusoidal Steady-State Analysis

EEE201 Circuit Analysis II

Lecture 1

# Agenda

- Sinusoidal Source
- Sinusoidal Response


# Sinusoidal Source

A sinusoidal voltage:

$$v = V_m \cos(\omega t + \phi)$$


$$f = 1/T \quad (\text{Hz})$$
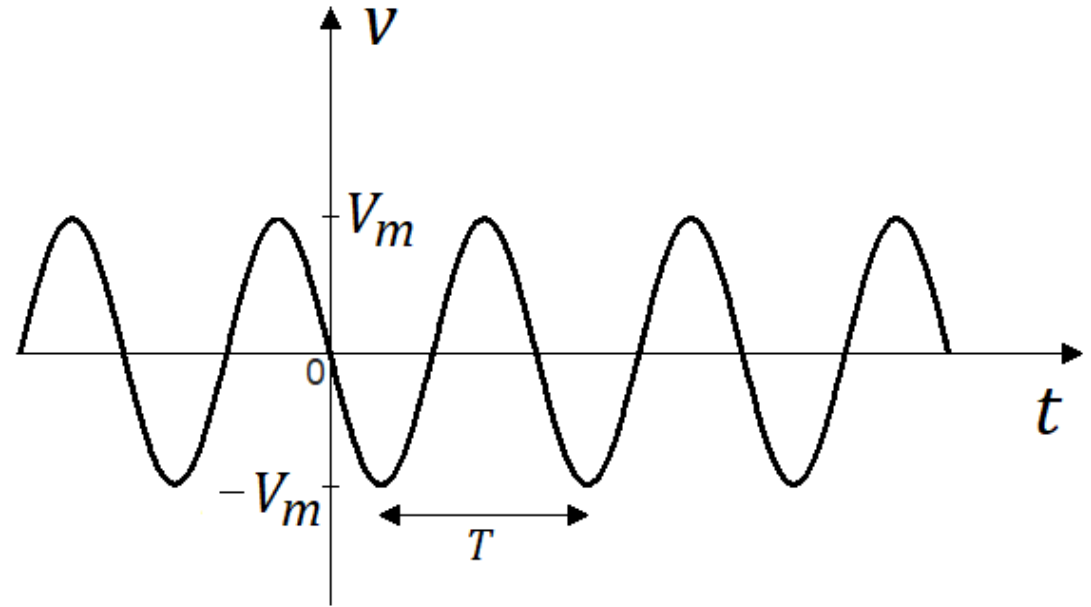
$$\omega = 2\pi f = 2\pi/T \quad (\text{radians/second})$$


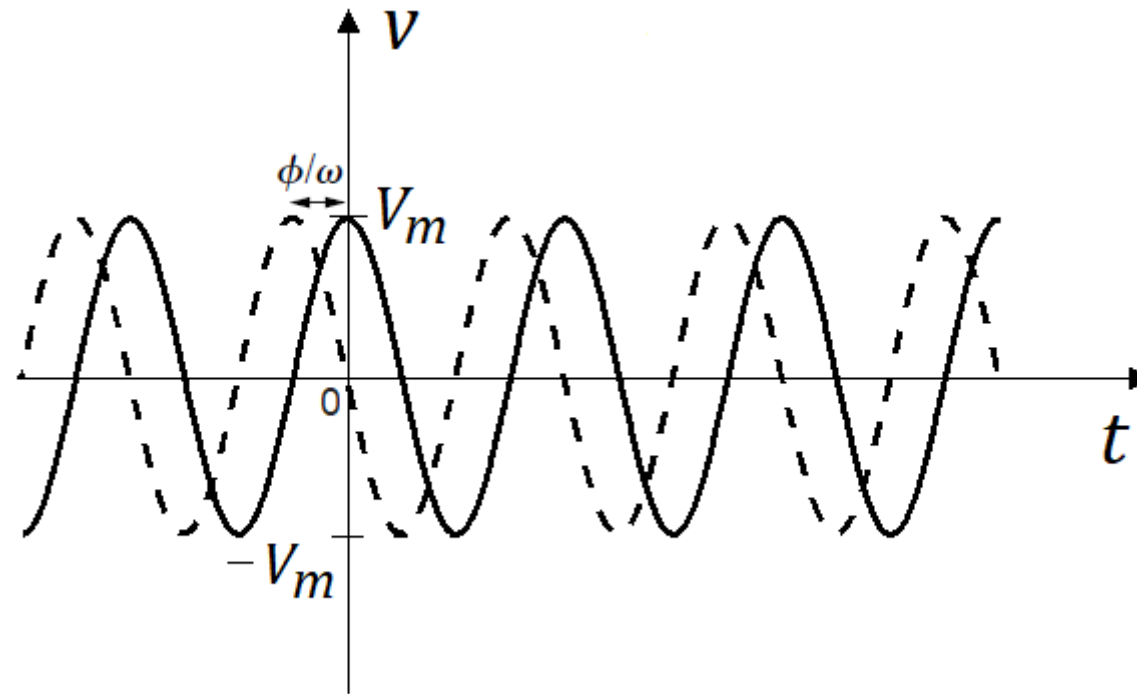
# Sinusoidal Source

Changing the phase angle  $\phi$  shifts the sinusoidal function along the time axis:



# Sinusoidal Source

The rms value of a periodic function is defined as the square root of the mean value of the squared function:

$$V_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt}$$


$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

# Sinusoidal Response

$$v_s = V_m \cos(\omega t + \phi)$$

For  $t \geq 0$ ,
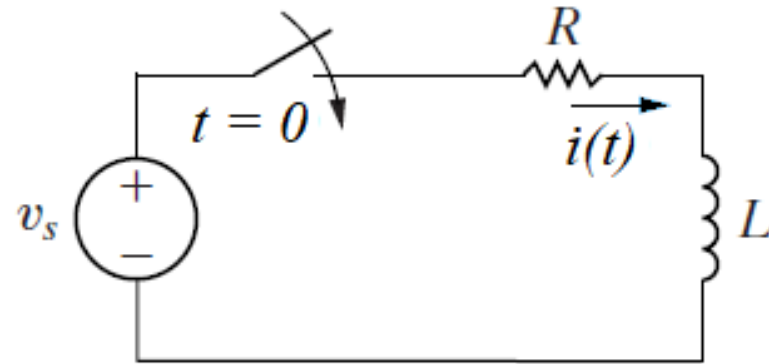
$$L \frac{di}{dt} + Ri = V_m \cos(\omega t + \phi)$$



# Sinusoidal Response

$$i = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-(R/L)t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

The first term  $\rightarrow$  *Transient component*

The second term  $\rightarrow$  *Steady – state component*



# Reference

- Electric Circuits, Tenth Edition, James W. Nilsson, Susan A. Riedel  
Pearson, 2015