

# EEE201

# Circuit Analysis II

Ankara University

Faculty of Engineering

Electrical and Electronics Engineering Department

# Sinusoidal Steady-State Analysis

EEE201 Circuit Analysis II

Lecture 4

# Agenda

- Linear Transformer
- Ideal Transformer

# Linear Transformer


$R_1$ : the resistance of the primary winding

$R_2$ : the resistance of the secondary winding

$L_1$ : the self-inductance of the primary winding

$L_2$ : the self-inductance of the secondary winding

$M$ : the mutual inductance

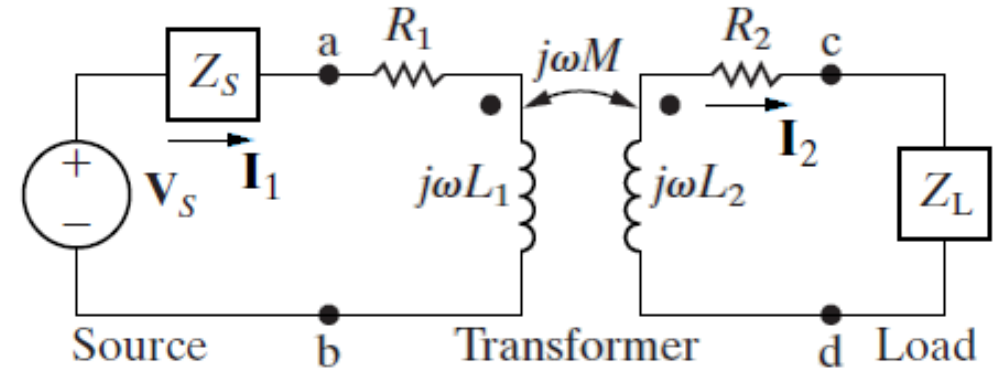


# Linear Transformer

$$Z_{11} = Z_S + R_1 + j\omega L_1$$

$$Z_{22} = R_2 + j\omega L_2 + Z_L$$


$$I_1 = \frac{Z_{22}}{Z_{11}Z_{22} + \omega^2 M^2} V_S$$

$$I_2 = \frac{j\omega M}{Z_{22}} I_1$$

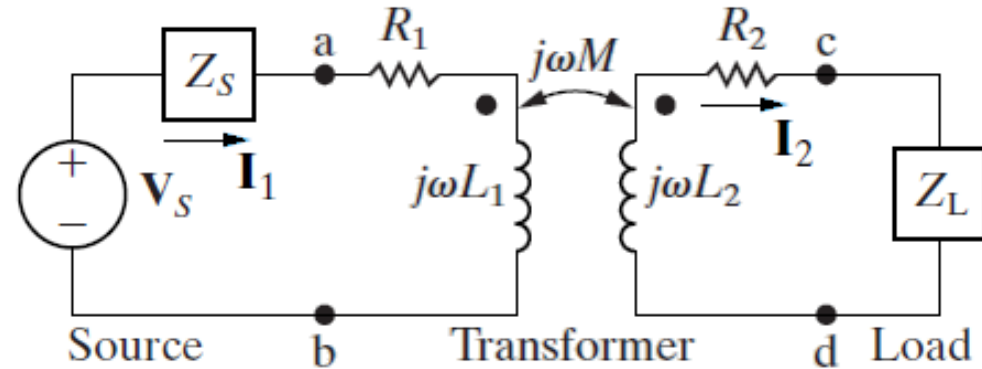

# Linear Transformer

$$Z_{ab} = R_1 + j\omega L_1 + Z_r$$

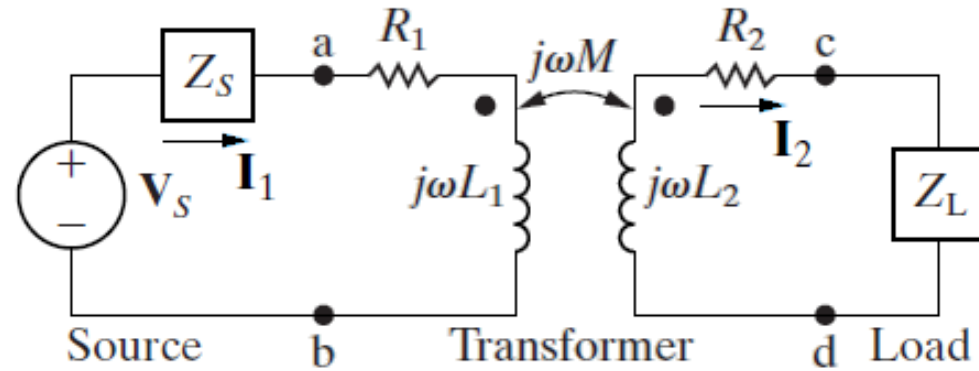


$$Z_r = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} \quad \text{(Reflected impedance)}$$


# Ideal Transformer

$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$I_1 N_1 = I_2 N_2$$

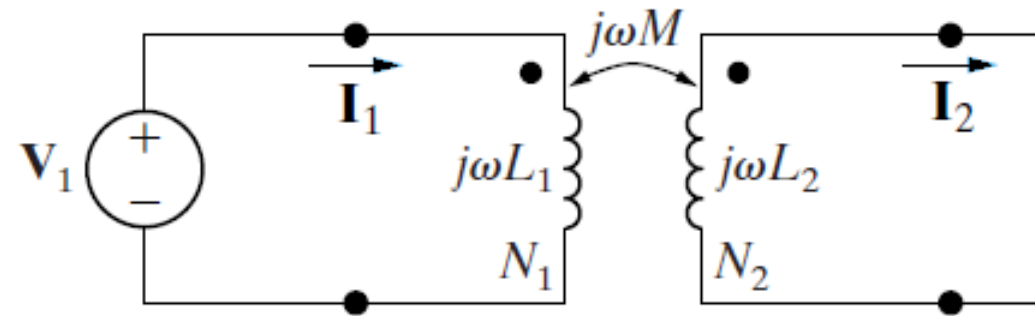

# Ideal Transformer

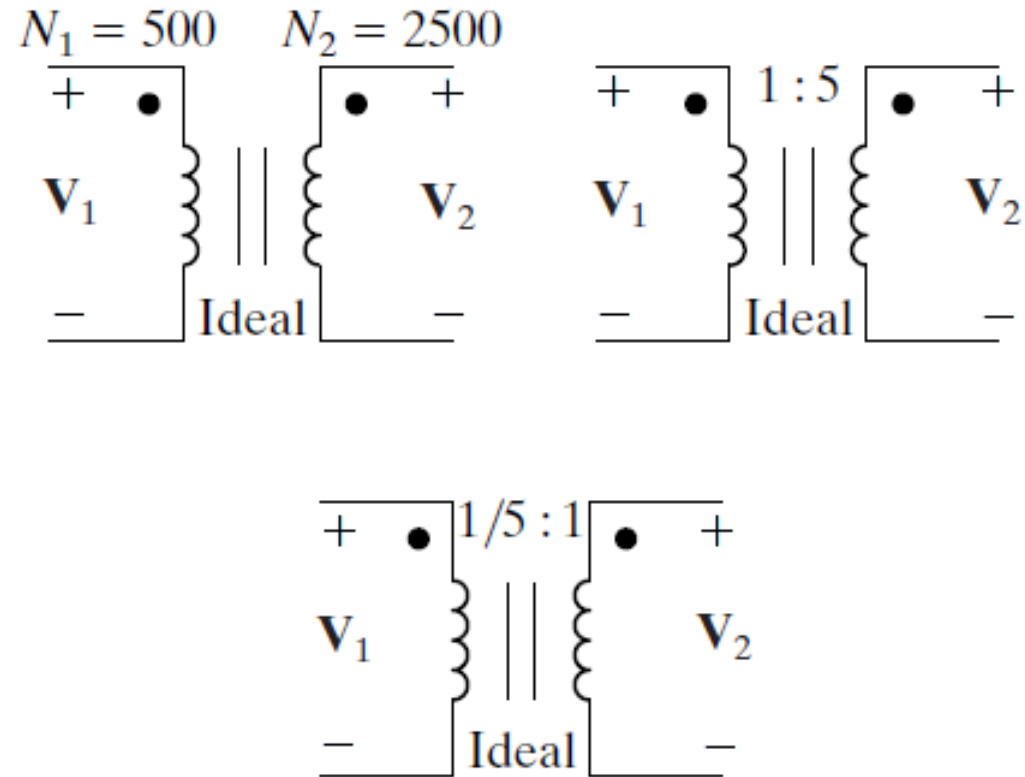



# Reference

- Electric Circuits, Tenth Edition, James W. Nilsson, Susan A. Riedel  
Pearson, 2015