

EEE201

Circuit Analysis II

Ankara University

Faculty of Engineering

Electrical and Electronics Engineering Department

Balanced Three-Phase Circuits

EEE201 Circuit Analysis II


Lecture 7

Agenda

- Balanced Three-Phase Voltages
- Three-Phase Voltage Sources
- Y-Y Circuit

Balanced Three-Phase Voltages

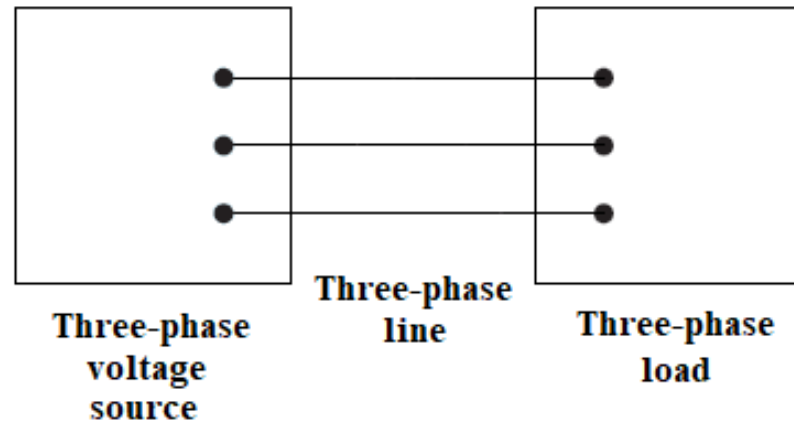a-phase voltage
b-phase voltage
c-phase voltage



Three-phase sources and loads can be either Y-connected or Δ -connected.


Balanced Three-Phase Voltages

abc (or positive) phase sequence:

$$V_a = V_m \angle 0^\circ$$

$$V_b = V_m \angle -120^\circ$$

$$V_c = V_m \angle +120^\circ$$

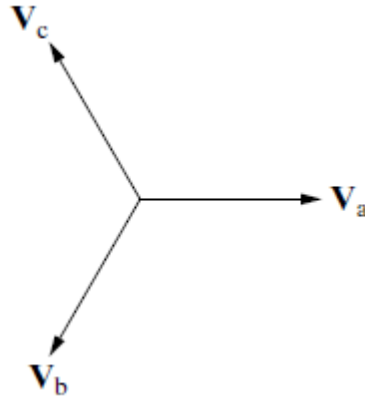


acb (or negative) phase sequence:

$$V_a = V_m \angle 0^\circ$$


$$V_b = V_m \angle +120^\circ$$

$$V_c = V_m \angle -120^\circ$$

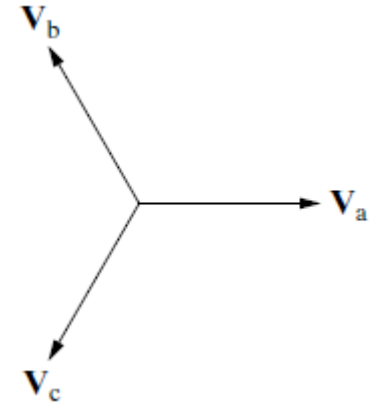


$$V_a + V_b + V_c = 0$$

Three-Phase Voltage Sources

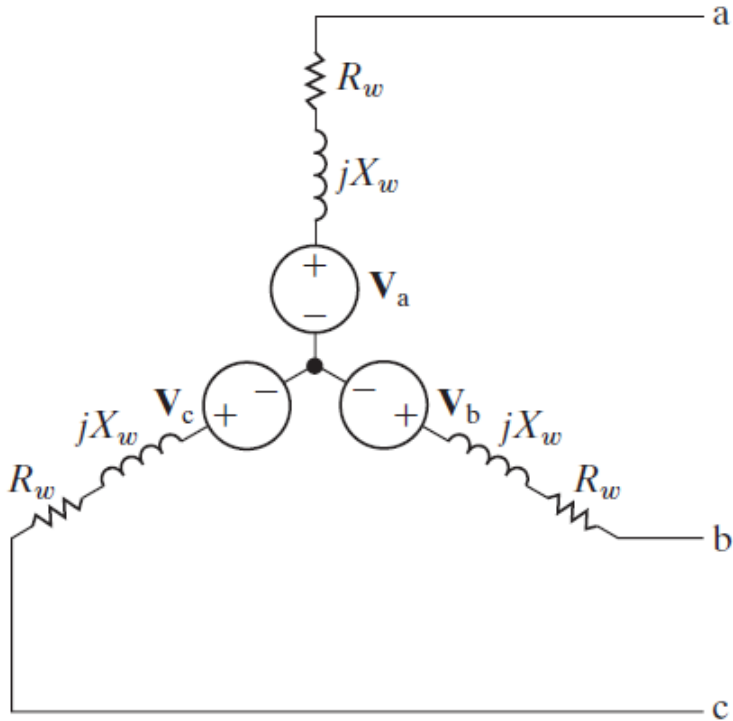

Y-connected source

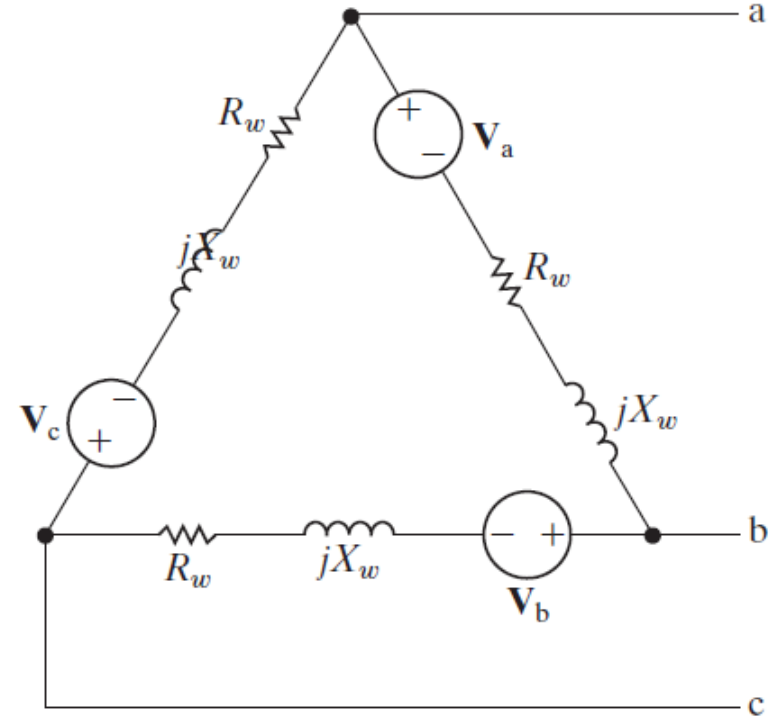


Δ -connected source

Y-Y Circuit

$$I_{aA} = \frac{V_{a'n} - V_N}{Z_A + Z_{1a} + Z_{ga}} = \frac{V_{a'n}}{Z_\phi}$$

$$I_{bB} = \frac{V_{b'n} - V_N}{Z_B + Z_{1b} + Z_{gb}} = \frac{V_{b'n}}{Z_\phi}$$
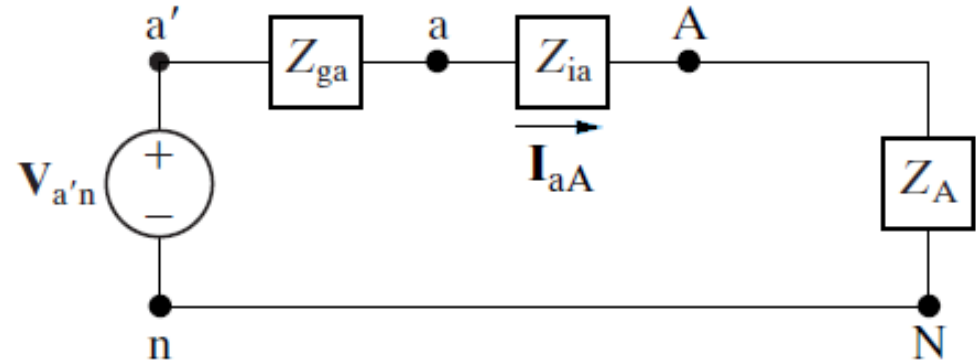
$$I_{cC} = \frac{V_{c'n} - V_N}{Z_C + Z_{1c} + Z_{gc}} = \frac{V_{c'n}}{Z_\phi}$$



Single-phase equivalent circuit

Y-Y Circuit

Line-to-neutral voltages:

$$V_{AN} = V_{\phi} \angle 0^{\circ}$$

$$V_{BN} = V_{\phi} \angle -120^{\circ}$$


$$V_{CN} = V_{\phi} \angle +120^{\circ}$$

Line-to-line voltages:

$$V_{AB} = \sqrt{3}V_{\phi} \angle 30^{\circ}$$

$$V_{BC} = \sqrt{3}V_{\phi} \angle -90^{\circ}$$
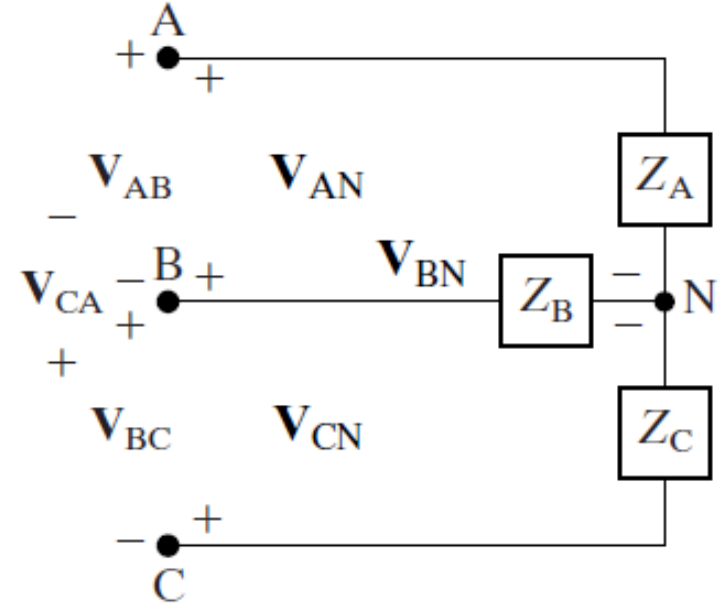
$$V_{CA} = \sqrt{3}V_{\phi} \angle +150^{\circ}$$



Reference

- Electric Circuits, Tenth Edition, James W. Nilsson, Susan A. Riedel
Pearson, 2015