

# EEE201

# Circuit Analysis II

Ankara University

Faculty of Engineering

Electrical and Electronics Engineering Department

# The Laplace Transform in Circuit Analysis

EEE201 Circuit Analysis II

Lecture 11

# Agenda


- Circuit Elements in the  $s$  Domain
- Circuit Analysis in the  $s$  Domain

# Circuit Elements in the s Domain

Resistor:

$$v = Ri$$
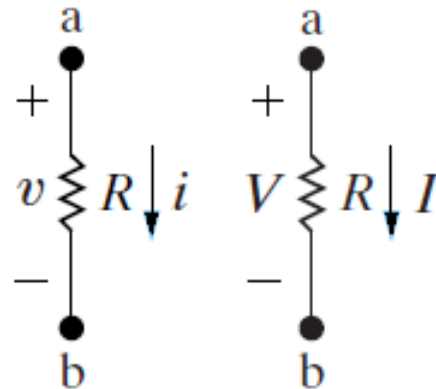
$$\mathcal{L}\{v\} = \mathcal{L}\{Ri\} \implies V = RI$$





# Circuit Elements in the s Domain

Inductor:

$$v = L \frac{di}{dt}$$

$$\mathcal{L}\{v\} = \mathcal{L}\left\{L \frac{di}{dt}\right\} \Rightarrow V = L[sI - i(0^-)]$$



$$V = sLI - LI_0$$

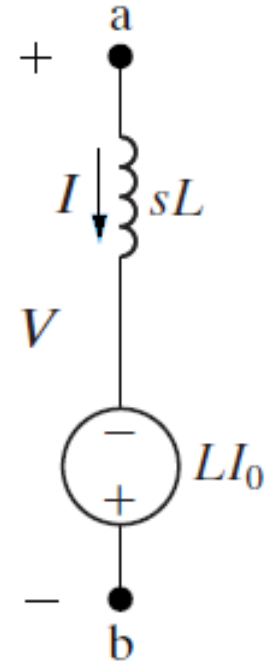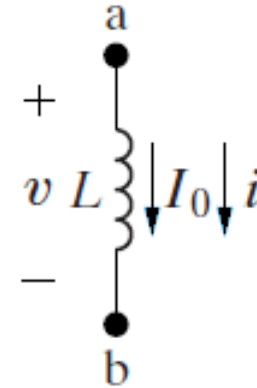
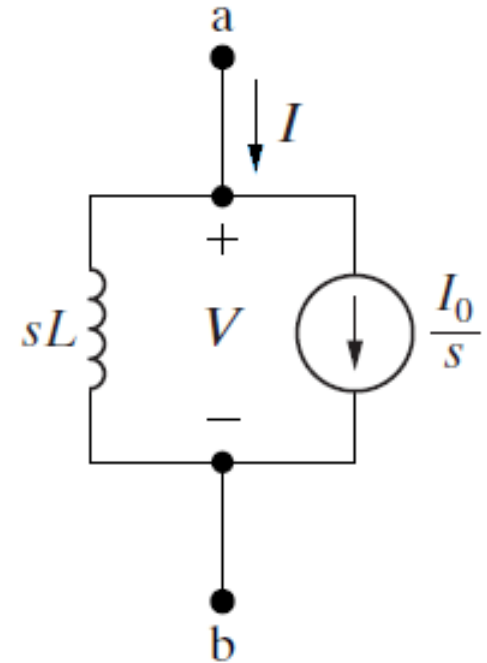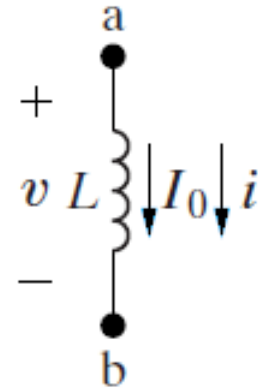
# Circuit Elements in the s Domain

Inductor:

$$V = sLI - LI_0 \Rightarrow I = \frac{V}{sL} + \frac{I_0}{s}$$




# Circuit Elements in the s Domain

Capacitor:

$$i = C \frac{dv}{dt}$$

$$\mathcal{L}\{i\} = \mathcal{L}\left\{C \frac{dv}{dt}\right\} \Rightarrow I = C[sV - v(0^-)]$$



$$I = sCV - CV_0$$

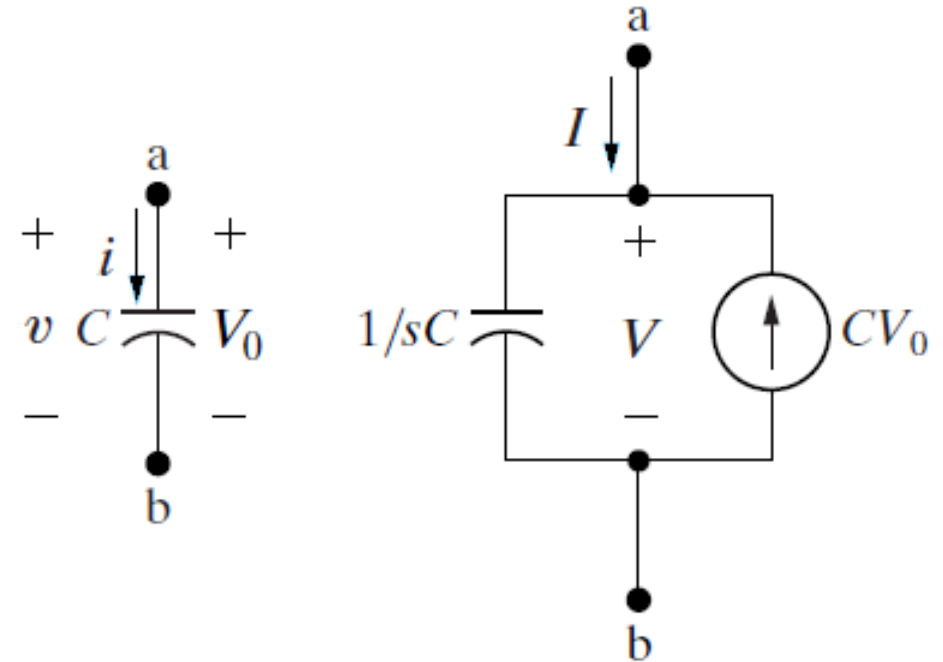
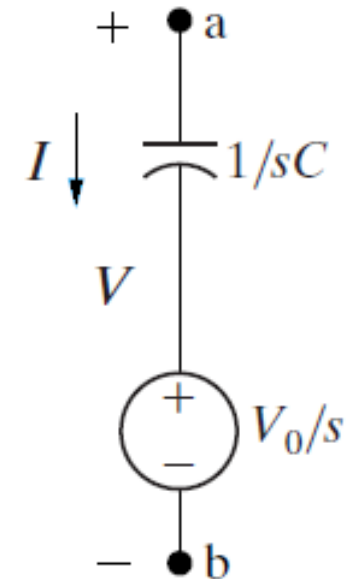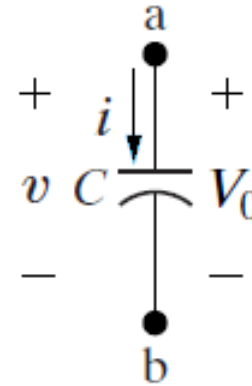
# Circuit Elements in the s Domain

Capacitor:

$$I = sCV - CV_0 \Rightarrow V = \left( \frac{1}{sC} \right) I + \frac{V_0}{s}$$





# Circuit Analysis in the $s$ Domain

Relationship between the terminal voltage and current:

$$V = ZI$$

Kirchhoff's Laws:  $\sum I = 0$  and  $\sum V = 0$

# Reference

- Electric Circuits, Tenth Edition, James W. Nilsson, Susan A. Riedel  
Pearson, 2015