



BME 202 Electronics

Lecture 5 : BJT – DC Biasing – Part 1

Outline



- DC levels for basic BJT configurations
- Saturation and cutoff conditions
- Load-line analysis for basic BJT configurations
- Design process for BJT amplifiers
- Transistor switching networks

Transistor Amplifier Analysis

Biasing: Applying DC voltages to a transistor in order to turn it on so that it can amplify AC signals.

Any increase in AC voltage, current, or power is the result of a transfer of energy from the applied DC supplies

$$V_{BE} \cong 0.7V$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

Biasing and Q-Point

The DC input establishes an operating or *quiescent point* called the ***Q-point***.

Q-point selection?

- Small-signal amplification operation
- Power amplifier

Other Factors

- Temperature stability
- Stability factor

The Three Operating Regions

Active or Linear Region Operation

- Base–Emitter junction is forward biased
- Base–Collector junction is reverse biased

Cutoff Region Operation

- Base–Emitter junction is reverse biased


Saturation Region Operation

- Base–Emitter junction is forward biased
- Base–Collector junction is forward biased

DC Biasing Circuits


- Fixed-bias configuration
- Emitter bias configuration
- Voltage divider bias configuration
- Collector feedback configuration
- Common-base configuration
- Miscellaneous bias configurations

Fixed Bias

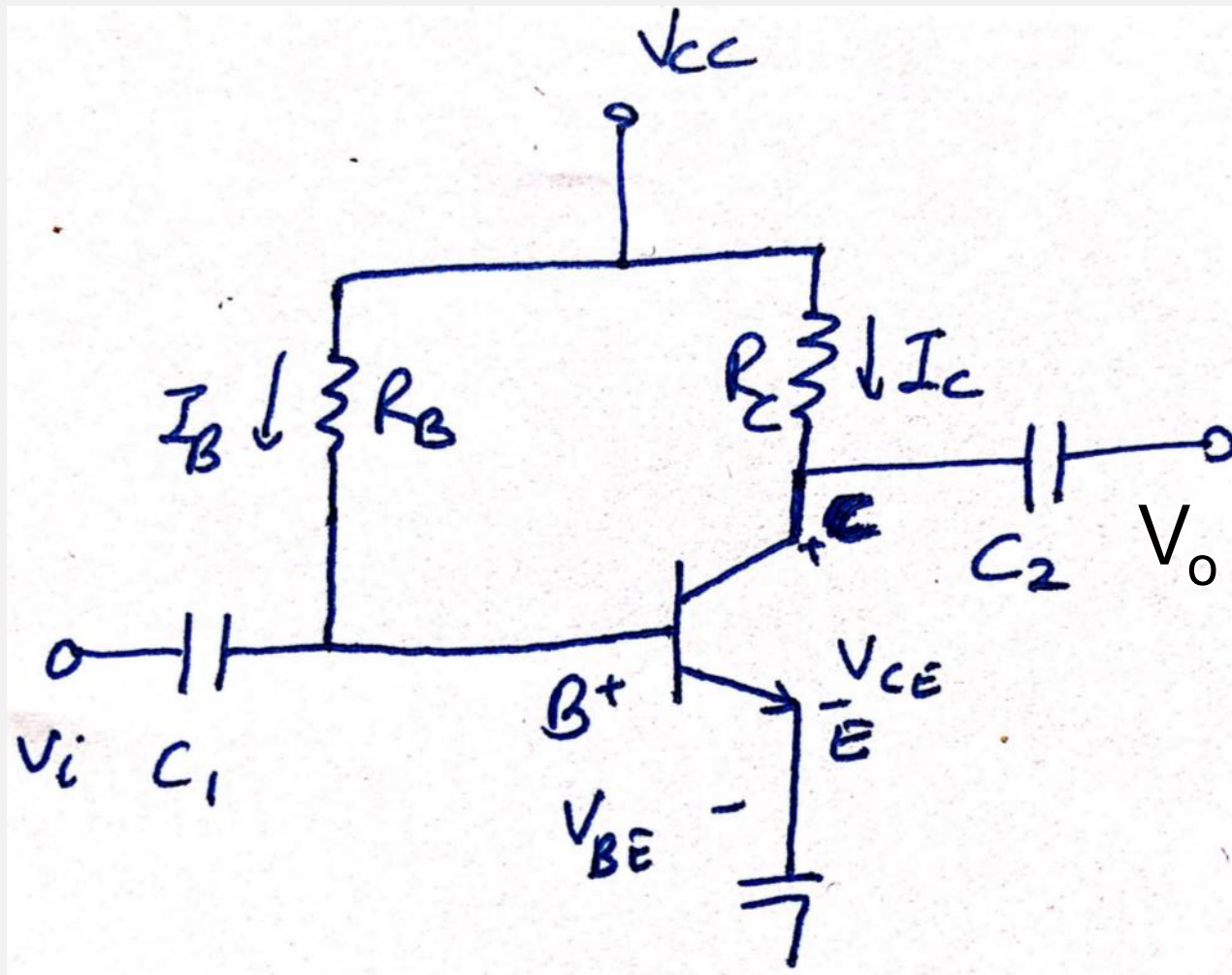

Fixed Bias

The Base-Emitter Loop

 

From KVL:


$$+V_{CC} - I_B R_B - V_{BE} = 0$$

Solving for base current:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

Fixed Bias

The Collector-Emitter Loop

 


Collector current:

$$I_C = \beta I_B$$

From KVL:

$$V_{CE} = V_{CC} - I_C R_C$$

Example

 

Determine I_B , I_{CQ} , V_{CEQ} , V_B , V_C and V_{BC} .

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12V - 0.7V}{240k\Omega} \approx \underline{\underline{47.08 \mu A}}$$

$$I_{CQ} = \beta I_B = 50 \cdot (47.08 \mu A) = \underline{\underline{2.35 mA}}$$

$$V_{CC} - I_C R_C - V_{CEQ} = 0$$

$$V_{CEQ} = V_{CC} - I_C R_C = 12V - (2.35 mA)(2.2k\Omega) = \underline{\underline{6.38V}}$$

$$V_B = V_{CC} - I_C R_C = 12V - (240k\Omega)(47.08 \mu A) = \underline{\underline{0.7V = V_{BE}}}$$


$$V_C = V_{CEQ} = \underline{\underline{6.38V}}, \quad V_{BC} = V_B - V_C = 0.7V - 6.85V = \underline{\underline{-6.15V}}$$

Fixed Bias

Saturation

When the transistor is operating in *saturation*, current through the transistor is at its *maximum* possible value.
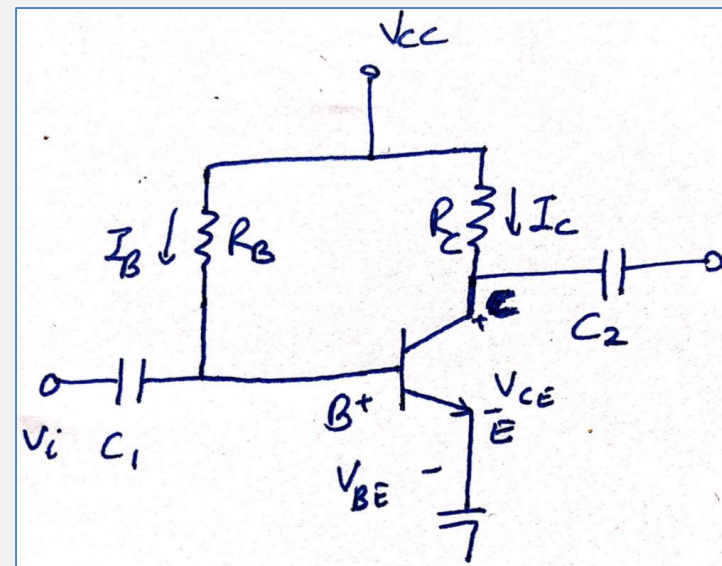
$$I_{Csat} = \frac{V_{CC}}{R_C} \quad V_{CE} \cong 0 \text{ V}$$



Fixed Bias

Load-Line Analysis

The load line end points are:

I_{Csat}


$$I_C = V_{CC} / R_C$$

$$V_{CE} = 0 \text{ V}$$

$V_{CEcutoff}$


$$V_{CE} = V_{CC}$$

$$I_C = 0 \text{ mA}$$

 

The Q-point is the operating point where the value of R_B sets the value of I_B that controls the values of V_{CE} and I_C .


Example

 

Given the load line and the defined Q point, determine:

V_{CC} , R_C and R_B for a fixed-bias config.

Remember Fixed-Bias Config:

 

$$\text{KVL: } V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$\text{When } I_C = 0 \Rightarrow V_{CE} = V_{CC} = 20 \text{ V.}$$

$$\text{When } V_{CE} = 0 \text{ V} \Rightarrow I_C R_C = V_{CC} \Rightarrow R_C = \frac{20 \text{ V}}{10 \text{ mA}} = \underline{\underline{2 \text{ k}\Omega}}$$


From Q Point : $I_B \approx 25 \mu\text{A}$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{20 \text{ V} - 0.7 \text{ V}}{R_B} \Rightarrow R_B = \frac{19.3 \text{ V}}{25 \mu\text{A}} = \underline{\underline{772 \text{ k}\Omega}}$$

Emitter Bias Circuit

Adding a resistor (R_E) to the emitter circuit stabilizes the bias circuit.

 → its response will change less due to undesirable changes in temperature and other parameters.



Emitter Bias Circuit

Base-Emitter Loop

From KVL:


$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

Since $I_E = (\beta + 1)I_B$:

$$V_{CC} - V_{BE} - (\beta + 1)I_B R_E = 0$$

Solving for I_B :
 
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$




Emitter Bias Circuit

Effect of R_E

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$

R_E is reflected back to input base current by a factor $(\beta + 1)$

$$R_i = (\beta + 1)R_E$$

 

Emitter Bias Circuit

Collector-Emitter Loop

From KVL:

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

Since $I_E \cong I_C$:


$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

and:

$$V_E = I_E R_E$$

$$V_C = V_{CE} + V_E = V_{CC} - I_C R_C$$

 
$$V_B = V_{CC} - I_R R_B = V_{BE} + V_E$$



Example

For the following circuit, determine $I_B, I_C, V_{CE},$

V_C, V_E, V_B, V_{BC}

 

$$I) 20V - (430k\Omega)I_B - V_{BE} - (\beta+1)R_E I_B = 0$$

$$I_B (430k\Omega + (51)(1k\Omega)) = 20V - 0.7V$$

$$I_B = \frac{19.3V}{481k\Omega} = 40.1\mu A \Rightarrow I_C = \beta I_B = 50 \cdot (40.1\mu A) = \underline{\underline{2.01mA}}$$

$$II) \overset{I_E \approx I_C}{20V} - (2k\Omega)I_C - V_{CE} - (1k\Omega)I_C = 0$$

$$V_{CE} = 20V - \overset{2.01mA}{I_C} (3k\Omega) = \underline{\underline{13.97V}}$$

$$V_C = 20V - (2k\Omega)I_C = 20V - 4.02V = \underline{\underline{15.98V}}$$

$$V_E = 1k\Omega I_C = (2.01mA)(1k\Omega) = \underline{\underline{2.01V}}$$

$$V_B = V_E + V_{BE} = 2.01V + 0.7V = \underline{\underline{2.71V}}$$

$$V_{BC} = V_B - V_C = 2.71V - 15.98V = \underline{\underline{-13.27V}}$$

Emitter Bias Circuit

Improved Biased Stability

Stability refers to a condition in which the currents and voltages remain fairly constant over a wide range of temperatures and transistor Beta (β) values.

Adding R_E to the emitter improves the stability of a transistor.

Example: change β from 50 to 100 and compare with fixed bias.


Fixed-Bias

β	I_B (μA)	I_C (mA)	V_{CE} (V)
50	47.08	2.35	6.83
100	47.08	4.71	1.64

Emitter-Bias

β	I_B (μA)	I_C (mA)	V_{CE} (V)
50	40.1	2.01	13.97
100	36.3	3.63	9.11

Voltage Divider Bias

 


The currents and voltages are nearly independent of any variations in β .

A very stable bias circuit.


- Exact Analysis
- Approximate Analysis

Voltage Divider Bias *Exact Analysis*

 

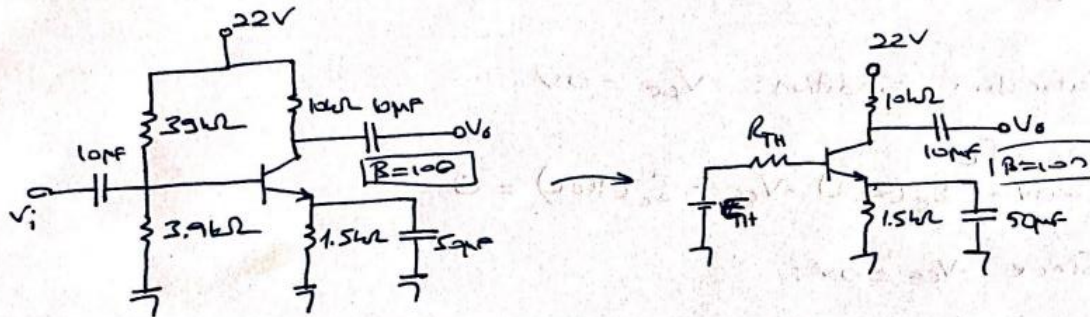Example

Determine V_{CE} and I_C for the following circuit:



$$R_{TH} = R_1 \parallel R_2 = (39k\Omega) \parallel (3.9k\Omega) = 3.55k\Omega$$

$$E_{TH} = \frac{R_2 V_{CC}}{R_1 + R_2} = \frac{(3.9k\Omega)(22V)}{(39k\Omega + 3.9k\Omega)} = 2V$$


$$I_B = \frac{E_{TH} - V_{BE}}{R_{TH} + (\beta + 1)R_E} = \frac{2V - 0.7V}{(3.55k\Omega) + (101)(1.5k\Omega)} = \frac{1.3V}{(3.55k\Omega) + (151.5k\Omega)} = \underline{\underline{8.38 \mu A}}$$

$$I_C = \beta I_B = 100 \cdot (8.38 \mu A) = \underline{\underline{0.84 mA}}$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E) = 22V - 0.84 mA(10k\Omega + 1.5k\Omega) = \underline{\underline{12.34V}}$$

Voltage Divider Bias *Approximate*

Analysis

 

$$I_B \ll I_1 \text{ and } I_1 \cong I_2$$

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$\beta R_E > 10R_2:$$

$$I_E = \frac{V_E}{R_E}$$

$$V_E = V_B - V_{BE}$$

using Kirchhoff's voltage law:


$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$I_E \cong I_C$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

 Example

Determine $I_{C\text{sat}}$ of the following circuit:



Saturation condition: $V_{CE} = 0V$.

$$\text{II) } I_C \approx I_E$$
$$20V - I_C(2k\Omega) - V_{CE} - I_C(1k\Omega) = 0$$


Since $V_{CE} = 0V$:

$$20V = I_C(3k\Omega)$$

$$I_{CE} = I_{C\text{sat}} = \frac{20V}{3k\Omega} = \underline{\underline{6.67\text{mA}}}$$

Voltage Divider Bias

Transistor Saturation Level

 

$$I_{C\text{sat}} = I_{C\text{max}} = \frac{V_{CC}}{R_C + R_E}$$

Load Line Analysis

Cutoff

$$V_{CE} = V_{CC}$$

$$I_C = 0 \text{ mA}$$

Saturation

$$I_C = \frac{V_{CC}}{R_C + R_E}$$

$$V_{CE} = 0 \text{ V}$$

Summary



DC Biasing Configurations

- Fixed-bias configuration
- Emitter bias configuration
- Voltage divider bias configuration
- Collector feedback configuration
- Common-base configuration
- Miscellaneous bias configurations

Part 1

Part 2