



# BME 202 Electronics

## Lecture 6: BJT – DC Biasing – Part 2

# Outline

---



- DC levels for basic BJT configurations
- Saturation and cutoff conditions
- Load-line analysis for basic BJT configurations
- Design process for BJT amplifiers
- Transistor switching networks

# DC Biasing Circuits


---

- Fixed-bias configuration
  - Emitter bias configuration
  - Voltage divider bias configuration
  - Collector feedback configuration
  - Common-base configuration
  - Miscellaneous bias configurations
- Part 1
- Part 2
 
# Collector Feedback Configuration

Another way to **improve the stability** of a bias circuit is to add a feedback path from collector to base.

In this bias circuit the Q-point is slightly dependent on the transistor beta,  $\beta$ .



# Collector Feedback Configuration

## Base-Emitter Loop

From KVL


$$V_{CC} - I'_C R_C - I_B R_F - V_{BE} - I_E R_E = 0$$

$$I_B \ll I_C \quad I'_C = I_C + I_B \cong I_C$$

Having  $I_C = \beta I_B$  and  $I_E \cong I_C$ , the loop equation becomes:

$$V_{CC} - \beta I_B R_C - I_B R_F - V_{BE} - \beta I_B R_E = 0$$

 Solving for  $I_B$ : 
$$I_B = \frac{V_{CC} - V_{BE}}{R_F + \beta(R_C + R_E)}$$



# Collector Feedback Configuration

## Collector-Emitter Loop

Applying KVL:


$$I_E + V_{CE} + I'_C R_C - V_{CC} = 0$$

Since  $I'_C \cong I_C$  and  $I_C = \beta I_B$ :

$$I_C(R_C + R_E) + V_{CE} - V_{CC} = 0$$


Solving for  $V_{CE}$ :

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

 

Exactly the same as voltage divider bias

# Examples

 

Determine the quiescent levels of  $I_{CQ}$  and  $V_{CEQ}$  for the network given on the left.

I. KVL

$$I_{C'} = I_E \approx I_C = \beta I_B$$

$$10V - \beta(4.7k\Omega)I_B - (250\Omega)I_B - V_{BE} - \beta(1.2k\Omega)I_B = 0$$

$$I_B = \frac{10V - 0.7V}{(250\Omega) + \beta(4.7k\Omega + 1.2k\Omega)} = \frac{9.3V}{(250\Omega + 531k\Omega)} = \frac{9.3V}{781k\Omega}$$

$$I_B = 11.91 \mu A$$

$$I_{CQ} = \beta I_B = 90 (11.91 \mu A) = 1.07 mA$$

II. KVL


$$I_C \approx I_E$$

$$10V - (4.7k\Omega)I_C - V_{CEQ} - (1.2k\Omega)I_C = 0$$

$$V_{CEQ} = 10V - (1.07mA)(4.7k\Omega + 1.2k\Omega) \\ = 10V - 6.31V$$


$$V_{CEQ} = 3.69V$$

# Emitter-Follower

 




# Common-Base Configuration

 
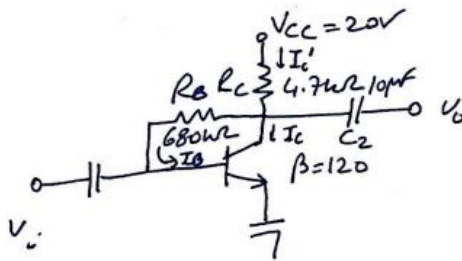
# Miscellaneous Bias Configurations

For the network given below:

- Determine  $I_{CQ}$  and  $V_{CEQ}$
- Find  $V_B$ ,  $V_C$ ,  $V_E$  and  $V_{BC}$



I KVL :  $I_{C'} \approx I_C = \beta I_B$

$$20V - (4.7k\Omega)\beta I_B - (680k\Omega)I_B - V_{BE} = 0$$

$$I_B = \frac{20V - 0.7V}{(\beta(4.7k\Omega) + 680k\Omega)} = \frac{19.3V}{1.244M\Omega} = \boxed{15.51\mu A}$$

$$I_{CQ} = \beta I_B = \boxed{1.86mA}$$

II KVL :  $I_{C'} \approx I_C$

$$20V - (4.7k\Omega)I_C - V_{CEQ} = 0$$

$$V_{CEQ} = 20V - (1.86mA)(4.7k\Omega) = \boxed{11.26V}$$

$$V_B = V_{BE} = \boxed{0.7V}$$

$$V_C = V_{CE} = \boxed{11.26V}$$


$$V_E = \boxed{0}$$

$$V_{BE} = V_B - V_C = 0.7V - 11.26V = \boxed{-10.56V}$$
 
# Miscellaneous Bias Configurations



Determine  $V_C$  and  $V_B$  for the network given below:



I. KVL

$$(-100\text{k}\Omega) I_B - V_{BE} + 9\text{V} = 0$$

$$I_B = \frac{9\text{V} - 0.7\text{V}}{100\text{k}\Omega} = \underline{\underline{83\text{ }\mu\text{A}}}$$

$$I_C = \beta I_B = \underline{\underline{3.735\text{ mA}}}$$

$$0 - (1.2\text{k}\Omega) I_C - V_{CEQ} + 9\text{V} = 0$$

$$V_{CEQ} = 9\text{V} - (1.2\text{k}\Omega) (3.735\text{ mA}) = 4.52\text{V}$$



$$V_C = -I_C R_C = \underline{\underline{-4.48\text{V}}}$$

$$V_B = -I_B R_B = \underline{\underline{-8.3\text{V}}}$$

# Design Examples

Given the device characteristics given below and the fixed bias configuration, determine

$V_{CC}$ ,  $R_B$ , and  $R_C$ :

  

From the load line :  $V_{CC} = 20V$

$$I_C = \frac{V_{CC}}{R_C} \quad | \quad V_{CE} = 0V$$

$$R_C = \frac{V_{CC}}{I_C} = \frac{20V}{8mA} = \underline{\underline{2.5k\Omega}}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \Rightarrow R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

$$R_B = \frac{20V - 0.7V}{40\mu A} = \frac{19.3V}{40\mu A} = \underline{\underline{482.5k\Omega}}$$


# Multiple BJT Networks

---

## Cascaded Systems

- The output of one amplifier is the input to the next amplifier
- The overall voltage gain is determined by the product of gains of the individual stages
- The DC bias circuits are isolated from each other by the coupling capacitors
- The DC calculations are independent of the cascading
- The AC calculations for gain and impedance are interdependent

# Darlington Connection

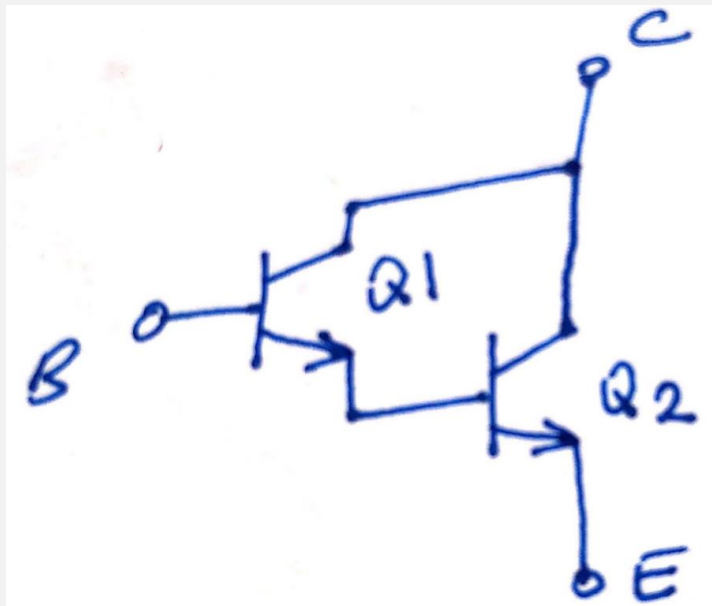


The Darlington circuit provides very **high current gain**, equal to the product of the individual current gains:

$$\beta_D = \beta_1 \beta_2$$

The practical significance is that the circuit provides a **very high input impedance**.

# DC Bias of Darlington Circuits

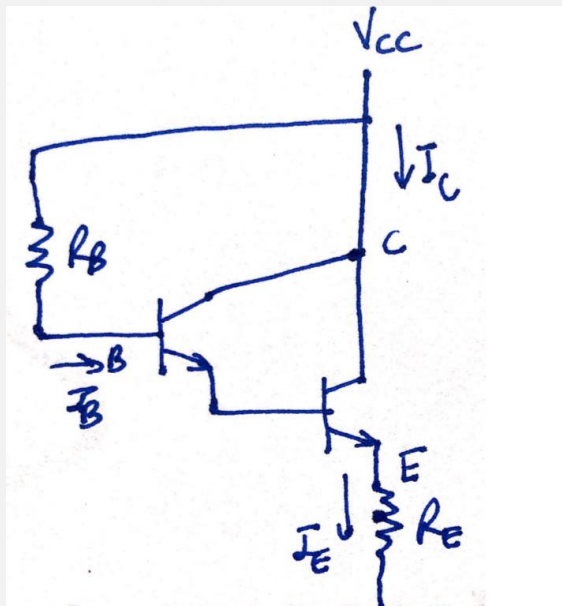

Base current:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta_D R_E}$$

Emitter current:

$$I_E = (\beta_D + 1)I_B \cong \beta_D I_B$$

Emitter voltage:


$$V_E = I_E R_E$$

Base voltage:

$$V_B = V_E + V_{BE}$$
 
# Feedback Pair

This is a two-transistor circuit that operates like a Darlington pair, *but it is not a Darlington pair.*




It has similar characteristics:

- High current gain
- Voltage gain near unity
- Low output impedance
- High input impedance

The difference is that a Darlington uses a pair of like transistors, whereas the feedback-pair configuration uses **complementary transistors**.




# Current Mirrors

 


Current mirror circuits provide **constant current** in integrated circuits.
 
# Current Source Circuits

Constant-current sources can be built using FETs, BJTs, and combinations of these devices.


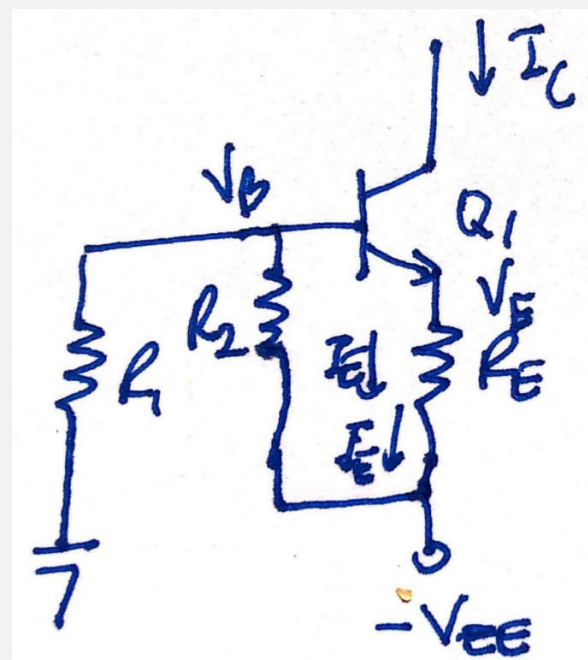
$$I \cong I_E = \frac{V_Z - V_{BE}}{R_E}$$



$$I_E \cong I_C$$

# PNP Transistors

---

The analysis for *pnp* transistor biasing circuits is the same as that for *npn* transistor circuits. The only difference is that the currents are flowing in the opposite direction.