



BME 212 Electronics Laboratory

Experiment #2 Diode Applications





Objective



- In this experiment, most common diode applications such as rectifiers, clippers and clampers will be studied and basic operation of a zener diode will be examined.

Preliminary Work

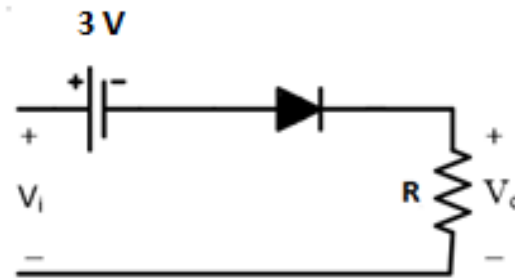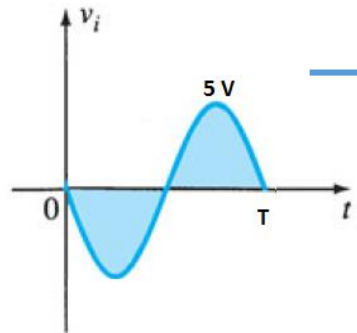1- Plot the output voltage, V_o , for the given inputs ($R = 220 \Omega$, $F = 1\text{KHz}$).




Output ??

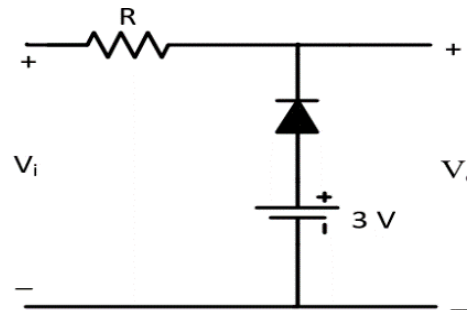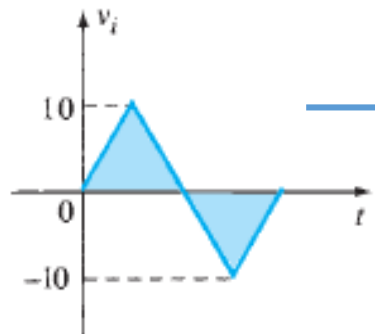

Output ??

Preliminary Work (Cont.)

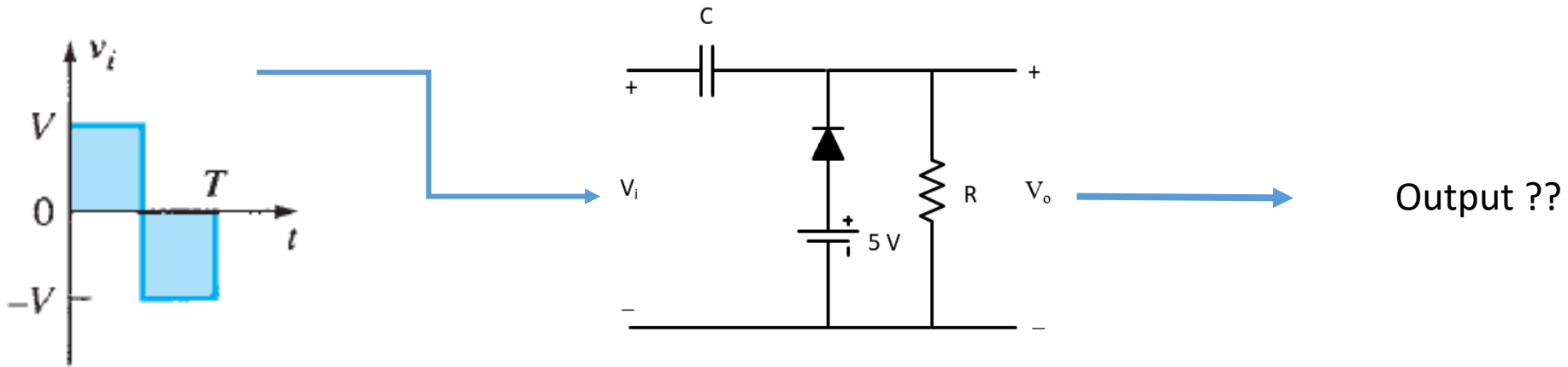2- Plot the output voltage, V_o , for the given input ($R = 100 \text{ k}\Omega$, $C = 1 \text{ }\mu\text{F}$, $V = 10 \text{ Vpp}$, $T = 1 \text{ ms}$).






Preliminary Work (Cont.)

3- Calculate the V_L , I_L , I_Z and I_R values for the given circuit if the input is given as: $V_i = 5\text{ V}$ and $V_i = 12\text{ V}$.





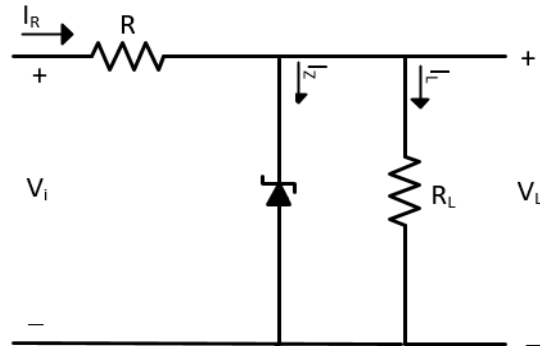
$$(R = 220\ \Omega, R_L = 2.2\ \text{k}\Omega, V_Z = 6.2\ \text{V})$$



Procedure


CHECK ALL THE DIODES USING MULTIMETER BEFORE START.

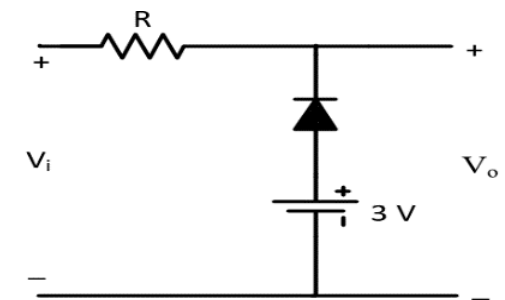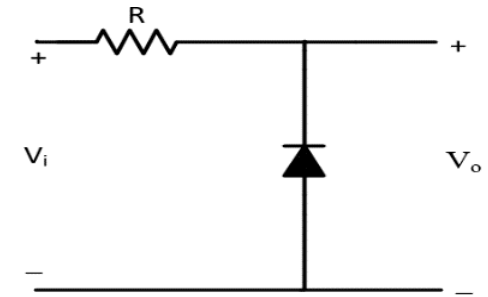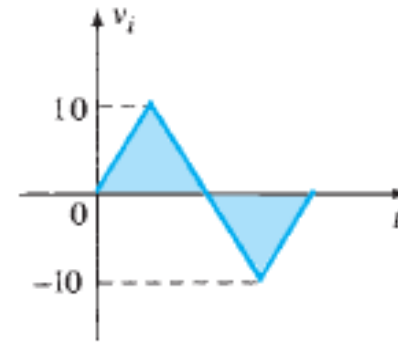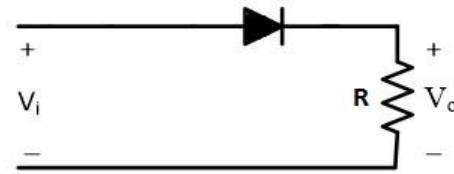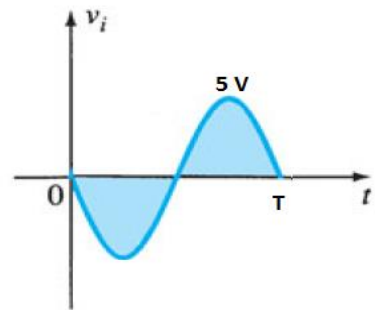1) Set up the circuits given below, plot the graph of V_o output voltages and compare the results. ($R = 220 \Omega$, $F = 1\text{KHz}$).



Procedure (Cont.)

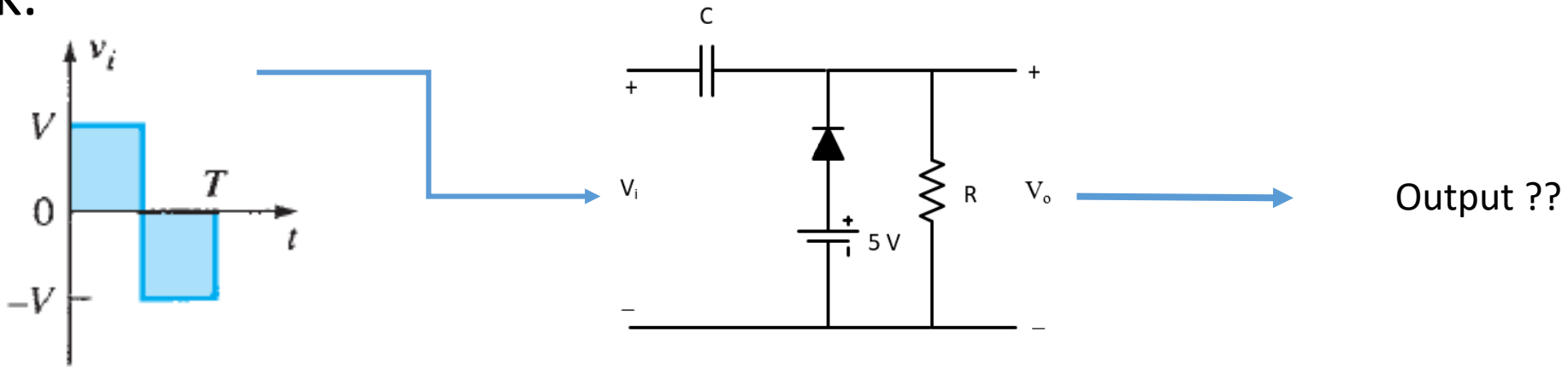2) For given circuit in Preliminary Work 2, adjust the $T = 1 \text{ ms}$, plot the graph of V_o output voltage and compare the results with Preliminary Work.






Procedure (Cont.)

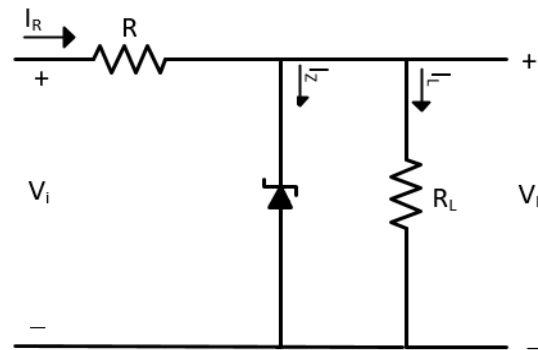3) For given circuit in Preliminary Work 3, measure and tabulate the V_L , I_L , I_Z and I_R values for the the input given as: $V_i = 5\text{ V}$ and $V_i = 12\text{ V}$. Compare the results with Preliminary Work.

$$(R = 220\ \Omega, R_L = 2.2\ \text{k}\Omega, V_Z = 6.2\ \text{V})$$








BME212 Report#2 Results



- 1) Plot graph of V_0 output voltage

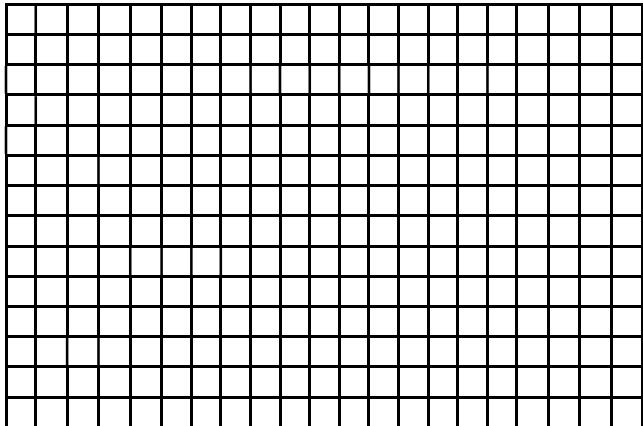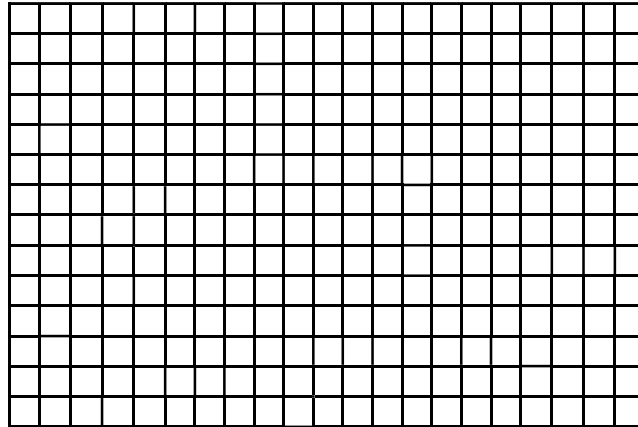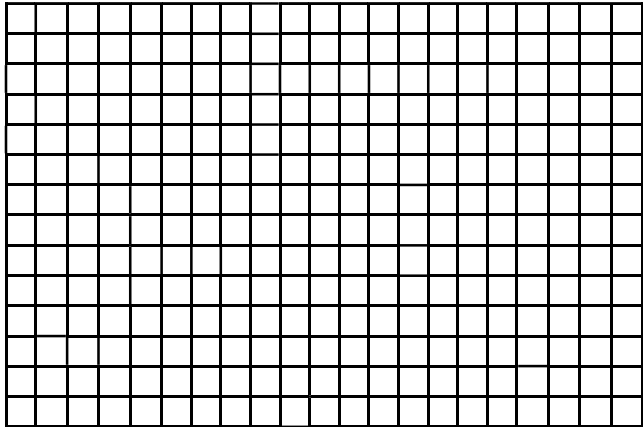


Comment:



BME212 Report#2 Results (Cont.)

2) Plot graph of V_0 output voltage

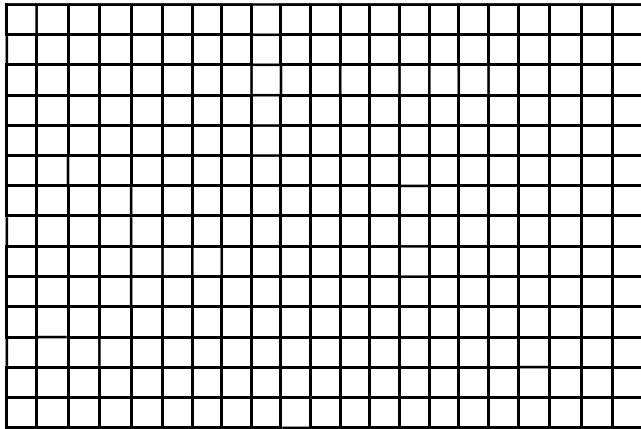

Comment:



BME212 Report#2 Results (Cont.)



3) Obtaining measurements

| V_i | V_L | I_L | I_Z | I_R |
|-------|-------|-------|-------|-------|
| 5 V | | | | |
| | | | | |
| 12 V | | | | |
| | | | | |

Comment: