
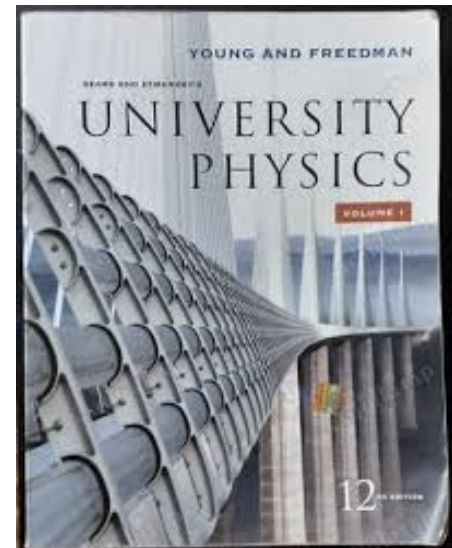


# PHYSICS II

Assoc.Prof. Yeşim MOĞULKOÇ

## References for this lecture:

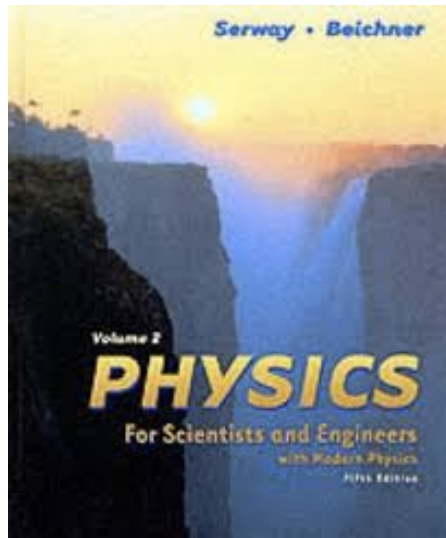

### Example 28.1 Terminal Voltage of a Battery

A battery has an emf of 12.0 V and an internal resistance of  $0.05 \Omega$ . Its terminals are connected to a load resistance of  $3.00 \Omega$ .

(A) Find the current in the circuit and the terminal voltage of the battery.

**Solution** Equation 28.3 gives us the current:

$$I = \frac{\mathcal{E}}{R + r} = \frac{12.0 \text{ V}}{3.05 \Omega} = 3.93 \text{ A}$$

and from Equation 28.1, we find the terminal voltage:

$$\Delta V = \mathcal{E} - Ir = 12.0 \text{ V} - (3.93 \text{ A})(0.05 \Omega) = 11.8 \text{ V}$$

To check this result, we can calculate the voltage across the load resistance  $R$ :

$$\Delta V = IR = (3.93 \text{ A})(3.00 \Omega) = 11.8 \text{ V}$$

(B) Calculate the power delivered to the load resistor, the power delivered to the internal resistance of the battery, and the power delivered by the battery.

**Solution** The power delivered to the load resistor is

$$\mathcal{P}_R = I^2 R = (3.93 \text{ A})^2 (3.00 \Omega) = 46.3 \text{ W}$$

The power delivered to the internal resistance is

$$\mathcal{P}_r = I^2 r = (3.93 \text{ A})^2 (0.05 \Omega) = 0.772 \text{ W}$$

Hence, the power delivered by the battery is the sum of these quantities, or 47.1 W. You should check this result, using the expression  $\mathcal{P} = I\mathcal{E}$ .

### Example 28.5 Finding $R_{eq}$ by Symmetry Arguments


Consider five resistors connected as shown in Figure 28.10a. Find the equivalent resistance between points  $a$  and  $b$ .

**Solution** If we inspect this system of resistors, we realize that we cannot reduce it by using our rules for series and parallel

connections. We can, however, assume a current entering junction  $a$  and then apply symmetry arguments. Because of the symmetry in the circuit (all  $1\text{-}\Omega$  resistors in the outside loop), the currents in branches  $ac$  and  $ad$  must be equal; hence, the electric potentials at points  $c$  and  $d$  must be equal.


This means that  $\Delta V_{cd} = 0$  and there is no current between points  $c$  and  $d$ . As a result, points  $c$  and  $d$  may be connected together without affecting the circuit, as in Figure 28.10b. Thus, the  $5\text{-}\Omega$  resistor may be removed from the circuit and

the remaining circuit then reduced as in Figures 28.10c and d. From this reduction we see that the equivalent resistance of the combination is  $1\text{ }\Omega$ . Note that the result is  $1\text{ }\Omega$  regardless of the value of the resistor connected between  $c$  and  $d$ .

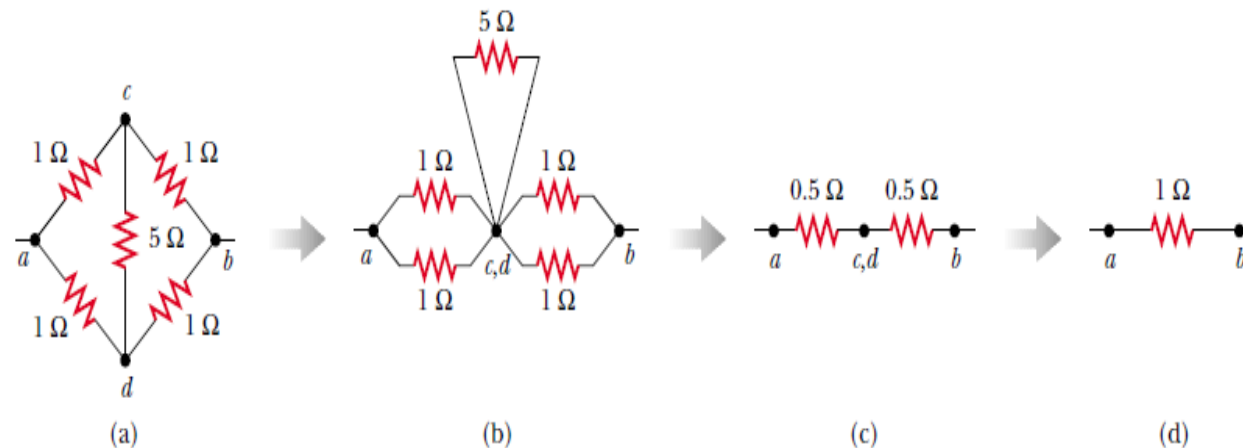

**Figure 28.10** (Example 28.5) Because of the symmetry in this circuit, the  $5\text{-}\Omega$  resistor does not contribute to the resistance between points  $a$  and  $b$  and therefore can be disregarded when we calculate the equivalent resistance.

6. (a) Find the equivalent resistance between points  $a$  and  $b$  in Figure P28.6. (b) A potential difference of  $34.0\text{ V}$  is applied between points  $a$  and  $b$ . Calculate the current in each resistor.

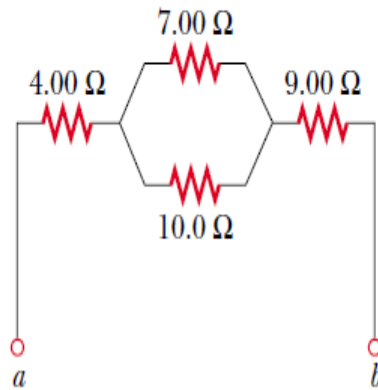

**Figure P28.6**

P28.6 (a) 
$$R_p = \frac{1}{(1/7.00 \Omega) + (1/10.0 \Omega)} = 4.12 \Omega$$

$$R_s = R_1 + R_2 + R_3 = 4.00 + 4.12 + 9.00 = \boxed{17.1 \Omega}$$

(b)  $\Delta V = IR$

$34.0 \text{ V} = I(17.1 \Omega)$

$I = \boxed{1.99 \text{ A}}$  for 4.00  $\Omega$ , 9.00  $\Omega$  resistors.

Applying  $\Delta V = IR$ ,  $(1.99 \text{ A})(4.12 \Omega) = 8.18 \text{ V}$

$8.18 \text{ V} = I(7.00 \Omega)$

so  $I = \boxed{1.17 \text{ A}}$  for 7.00  $\Omega$  resistor

$8.18 \text{ V} = I(10.0 \Omega)$

so  $I = \boxed{0.818 \text{ A}}$  for 10.0  $\Omega$  resistor.

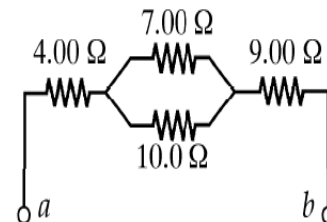

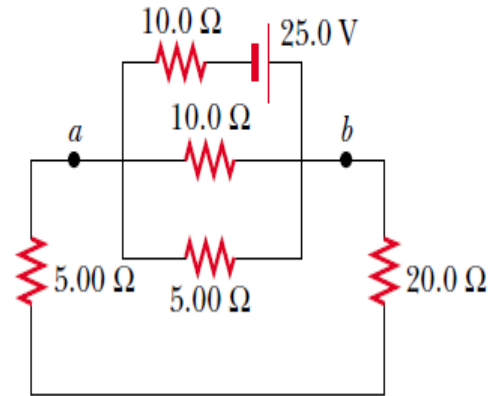


FIG. P28.6

9.  Consider the circuit shown in Figure P28.9. Find (a) the current in the  $20.0\text{-}\Omega$  resistor and (b) the potential difference between points  $a$  and  $b$ .



**Figure P28.9**

**P28.9** If we turn the given diagram on its side, we find that it is the same as figure (a). The  $20.0\ \Omega$  and  $5.00\ \Omega$  resistors are in series, so the first reduction is shown in (b). In addition, since the  $10.0\ \Omega$ ,  $5.00\ \Omega$ , and  $25.0\ \Omega$  resistors are then in parallel, we can solve for their equivalent resistance as:

$$R_{\text{eq}} = \frac{1}{\left(\frac{1}{10.0\ \Omega} + \frac{1}{5.00\ \Omega} + \frac{1}{25.0\ \Omega}\right)} = 2.94\ \Omega.$$

This is shown in figure (c), which in turn reduces to the circuit shown in figure (d).

Next, we work backwards through the diagrams applying  $I = \frac{\Delta V}{R}$  and  $\Delta V = IR$  alternately to every resistor, real and equivalent. The  $12.94\ \Omega$  resistor is connected across  $25.0\ \text{V}$ , so the current through the battery in every diagram is

$$I = \frac{\Delta V}{R} = \frac{25.0\ \text{V}}{12.94\ \Omega} = 1.93\ \text{A}.$$

In figure (c), this  $1.93\ \text{A}$  goes through the  $2.94\ \Omega$  equivalent resistor to give a potential difference of:


$$\Delta V = IR = (1.93\ \text{A})(2.94\ \Omega) = 5.68\ \text{V}.$$

From figure (b), we see that this potential difference is the same across  $\Delta V_{ab}$ , the  $10\ \Omega$  resistor, and the  $5.00\ \Omega$  resistor.

(b) Therefore,  $\Delta V_{ab} = \boxed{5.68\ \text{V}}$ .

(a) Since the current through the  $20.0\ \Omega$  resistor is also the current through the  $25.0\ \Omega$  line  $ab$ ,


$$I = \frac{\Delta V_{ab}}{R_{ab}} = \frac{5.68\ \text{V}}{25.0\ \Omega} = 0.227\ \text{A} = \boxed{227\ \text{mA}}.$$

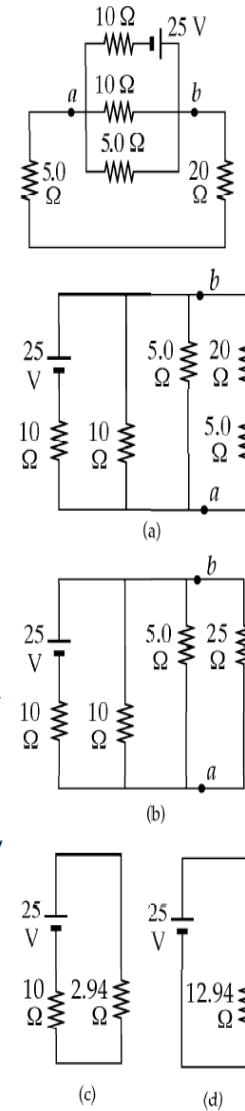

**FIG. P28.9**






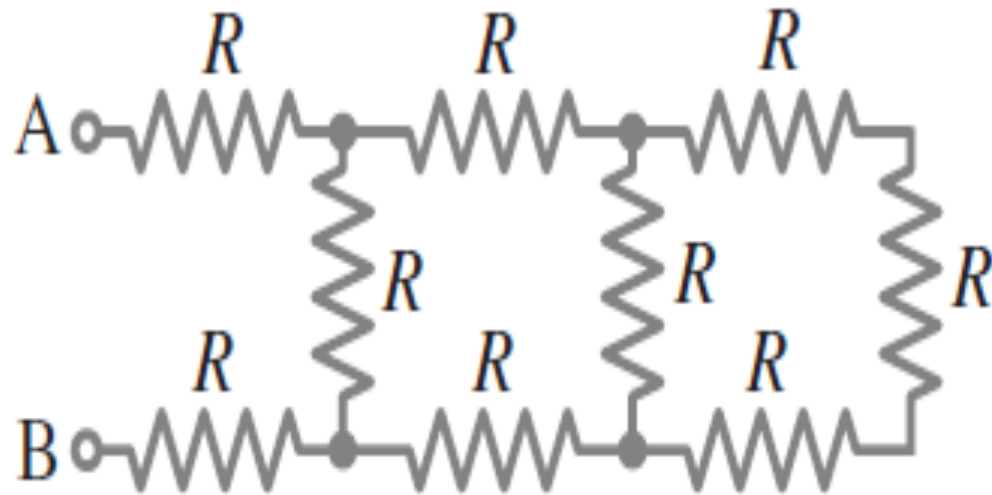
Find the equivalent resistance between A and B points




$$R_{\text{eq1}} = \left( \frac{1}{R} + \frac{1}{3R} \right)^{-1} = \frac{3}{4}R$$

$$R_{\text{eq2}} = \left( \frac{1}{R} + \frac{4}{11R} \right)^{-1} = \frac{11}{15}R$$
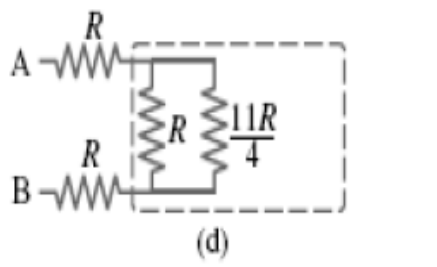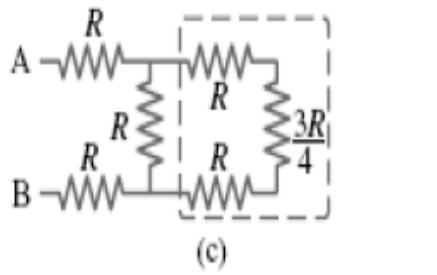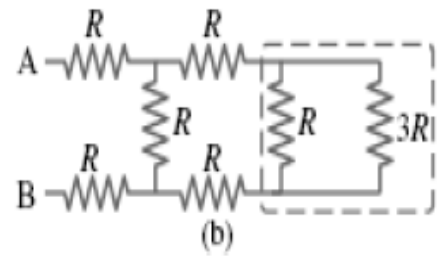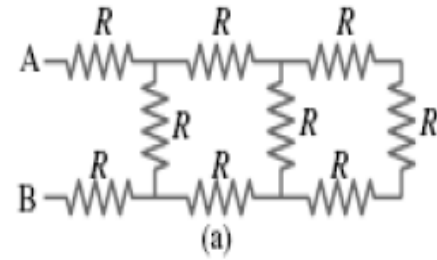
$$R_{\text{eq}} = 2R + \frac{11}{15}R = \frac{41}{15}R$$




19. (II) What is the net resistance of the circuit connected to the battery in Fig. 19–50?

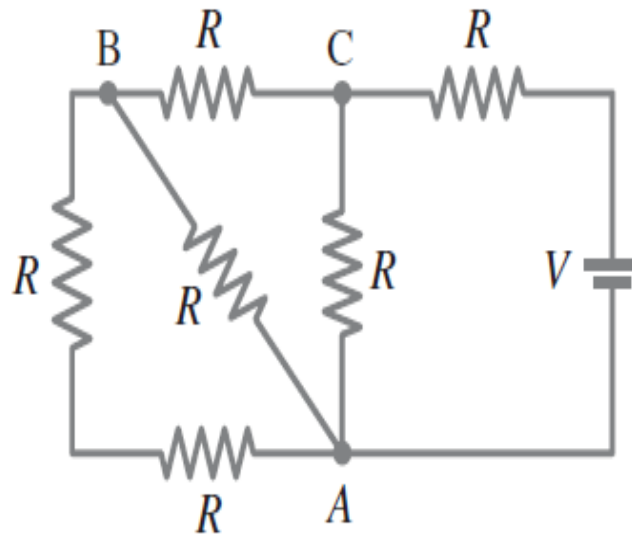

**FIGURE 19–50**  
Problems 19 and 20.

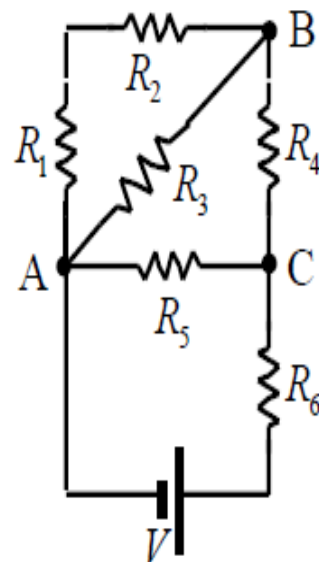19. The resistors have been numbered in the accompanying diagram to help in the analysis.  $R_1$  and  $R_2$  are in series with an equivalent resistance of  $R_{12} = R + R = 2R$ . This combination is in parallel with  $R_3$ , with an equivalent resistance of  $R_{123} = \left(\frac{1}{R} + \frac{1}{2R}\right)^{-1} = \frac{2}{3}R$ . This combination is in series with  $R_4$ , with an equivalent resistance of  $R_{1234} = \frac{2}{3}R + R = \frac{5}{3}R$ . This combination is in parallel with  $R_5$ , with an equivalent resistance of  $R_{12345} = \left(\frac{1}{R} + \frac{3}{5R}\right)^{-1} = \frac{5}{8}R$ .



Finally, this combination is in series with  $R_6$ , and we calculate the final equivalent resistance.


$$R_{\text{eq}} = \frac{5}{8}R + R = \boxed{\frac{13}{8}R}$$

### Example 28.8 A Single-Loop Circuit

A single-loop circuit contains two resistors and two batteries, as shown in Figure 28.16. (Neglect the internal resistances of the batteries.)

(A) Find the current in the circuit.

**Solution** We do not need Kirchhoff's rules to analyze this simple circuit, but let us use them anyway just to see how they are applied. There are no junctions in this single-loop circuit; thus, the current is the same in all elements. Let us assume that the current is clockwise, as shown in Figure 28.16. Traversing the circuit in the clockwise direction, starting at  $a$ , we see that  $a \rightarrow b$  represents a potential difference of  $+\mathcal{E}_1$ ,  $b \rightarrow c$  represents a potential difference of  $-IR_1$ ,  $c \rightarrow d$  represents a potential difference of  $-\mathcal{E}_2$ , and

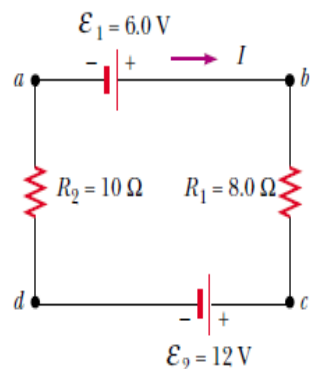

**Figure 28.16** (Example 28.8) A series circuit containing two batteries and two resistors, where the polarities of the batteries are in opposition.

$d \rightarrow a$  represents a potential difference of  $-IR_2$ . Applying Kirchhoff's loop rule gives

$$\sum \Delta V = 0$$

$$\mathcal{E}_1 - IR_1 - \mathcal{E}_2 - IR_2 = 0$$

Solving for  $I$  and using the values given in Figure 28.16, we obtain

$$(1) \quad I = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2} = \frac{6.0 \text{ V} - 12 \text{ V}}{8.0 \Omega + 10 \Omega} = -0.33 \text{ A}$$

The negative sign for  $I$  indicates that the direction of the current is opposite the assumed direction. Notice that the emfs in the numerator subtract because the batteries have opposite polarities in Figure 28.16. In the denominator, the resistances add because the two resistors are in series.

(B) What power is delivered to each resistor? What power is delivered by the 12-V battery?

**Solution** Using Equation 27.23,

$$\mathcal{P}_1 = I^2 R_1 = (0.33 \text{ A})^2 (8.0 \Omega) = 0.87 \text{ W}$$

$$\mathcal{P}_2 = I^2 R_2 = (0.33 \text{ A})^2 (10 \Omega) = 1.1 \text{ W}$$

Hence, the total power delivered to the resistors is  $\mathcal{P}_1 + \mathcal{P}_2 = 2.0 \text{ W}$ .

The 12-V battery delivers power  $I\mathcal{E}_2 = 4.0 \text{ W}$ . Half of this power is delivered to the two resistors, as we just calculated. The other half is delivered to the 6-V battery, which is being charged by the 12-V battery. If we had included the internal resistances of the batteries in our analysis, some of the power would appear as internal energy in the batteries; as a result, we would have found that less power was being delivered to the 6-V battery.

Find the currents  $I_1$ ,  $I_2$ , and  $I_3$  in the circuit shown in Figure 28.17.


**Solution** Conceptualize by noting that we cannot simplify the circuit by the rules of adding resistances in series and in parallel. (If the 10.0-V battery were taken away, we could reduce the remaining circuit with series and parallel combinations.) Thus, we categorize this problem as one in which we must use Kirchhoff's rules. To analyze the circuit, we arbitrarily choose the directions of the currents as labeled in Figure 28.17. Applying Kirchhoff's junction rule to junction  $c$  gives

$$(1) \quad I_1 + I_2 = I_3$$

We now have one equation with three unknowns— $I_1$ ,  $I_2$ , and  $I_3$ . There are three loops in the circuit— $abcd$ ,  $befcb$ , and  $afda$ . We therefore need only two loop equations to determine the unknown currents. (The third loop equation would give no new information.) Applying Kirchhoff's loop rule to loops  $abcd$  and  $befcb$  and traversing these loops clockwise, we obtain the expressions

$$(2) \quad abcd \quad 10.0 \text{ V} - (6.0 \, \Omega)I_1 - (2.0 \, \Omega)I_3 = 0$$

$$(3) \quad befcb \quad -14.0 \text{ V} + (6.0 \, \Omega)I_1 - 10.0 \text{ V} - (4.0 \, \Omega)I_2 = 0$$

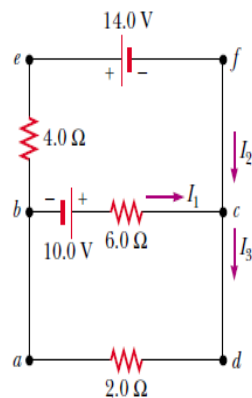

**Figure 28.17** (Example 28.9) A circuit containing different branches.

Note that in loop  $befcb$  we obtain a positive value when traversing the 6.0- $\Omega$  resistor because our direction of travel is opposite the assumed direction of  $I_1$ . Expressions (1), (2), and (3) represent three independent equations with three unknowns. Substituting Equation (1) into Equation (2) gives

$$10.0 \text{ V} - (6.0 \, \Omega)I_1 - (2.0 \, \Omega)(I_1 + I_2) = 0$$

$$(4) \quad 10.0 \text{ V} = (8.0 \, \Omega)I_1 + (2.0 \, \Omega)I_2$$

Dividing each term in Equation (3) by 2 and rearranging gives

$$(5) \quad -12.0 \text{ V} = -(3.0 \, \Omega)I_1 + (2.0 \, \Omega)I_2$$

Subtracting Equation (5) from Equation (4) eliminates  $I_2$ , giving

$$22.0 \text{ V} = (11.0 \, \Omega)I_1$$

$$I_1 = 2.0 \text{ A}$$

Using this value of  $I_1$  in Equation (5) gives a value for  $I_2$ :

$$(2.0 \, \Omega)I_2 = (3.0 \, \Omega)I_1 - 12.0 \text{ V} \\ = (3.0 \, \Omega)(2.0 \text{ A}) - 12.0 \text{ V} = -6.0 \text{ V}$$

$$I_2 = -3.0 \text{ A}$$

Finally,

$$I_3 = I_1 + I_2 = -1.0 \text{ A}$$

To finalize the problem, note that  $I_2$  and  $I_3$  are both negative. This indicates only that the currents are opposite the direction we chose for them. However, the numerical values are correct. What would have happened had we left the current directions as labeled in Figure 28.17 but traversed the loops in the opposite direction?