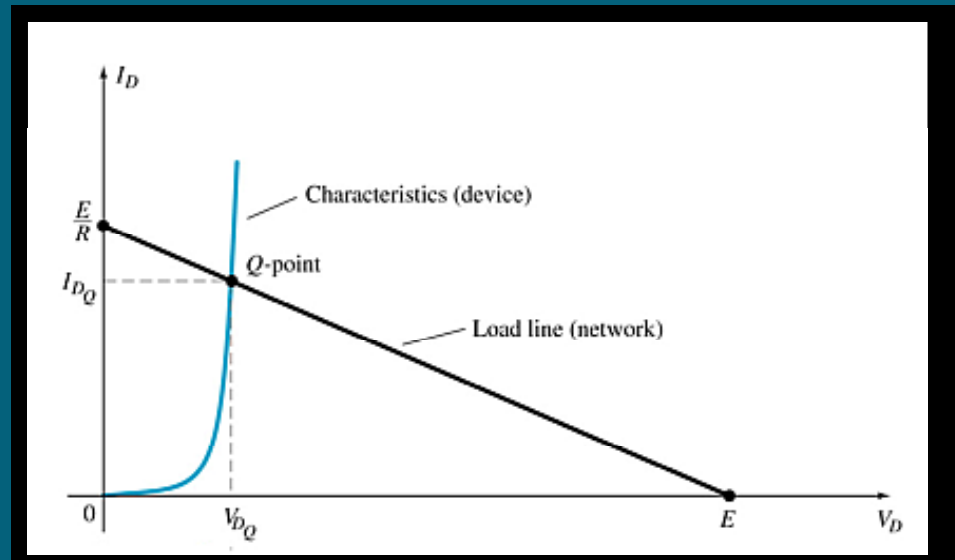


EE-202 Electronics
Chapter 4:
Diode Applications
Half and Full-Wave rectifiers
Zeners

Load-Line



The load line shows all possible current via voltage conditions.

Load line and the characteristic curve intersects in the Q-point,



Half-Wave Rectification


The diode conducts when forward biased.

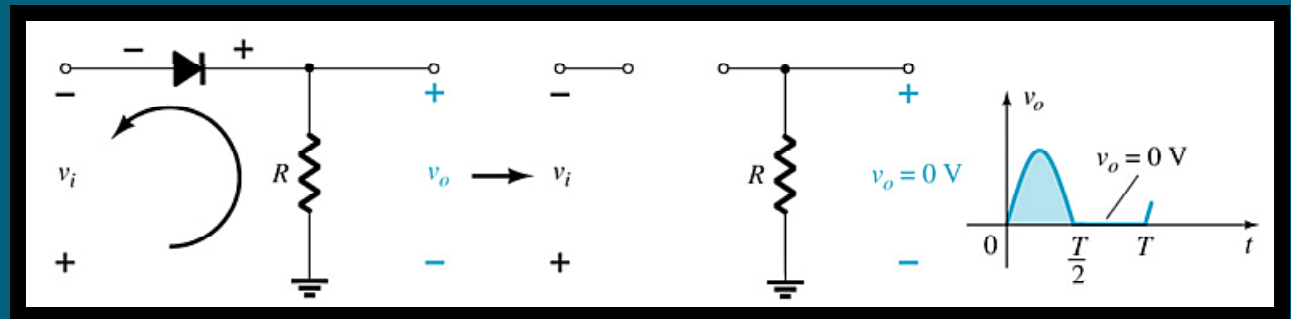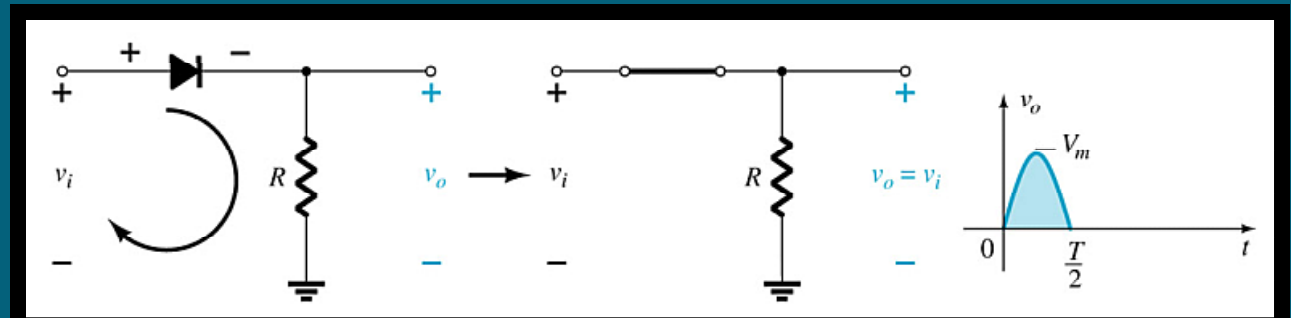


Full-Wave Rectification

Full-wave rectification produces a greater DC output:

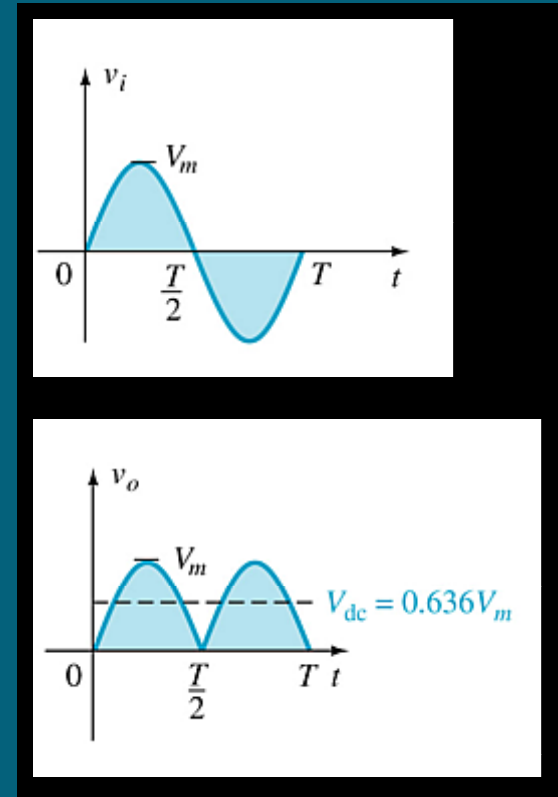- Half-wave: $V_{dc} = 0.318V_m$
- Full-wave: $V_{dc} = 0.636V_m$




Full-Wave Rectification

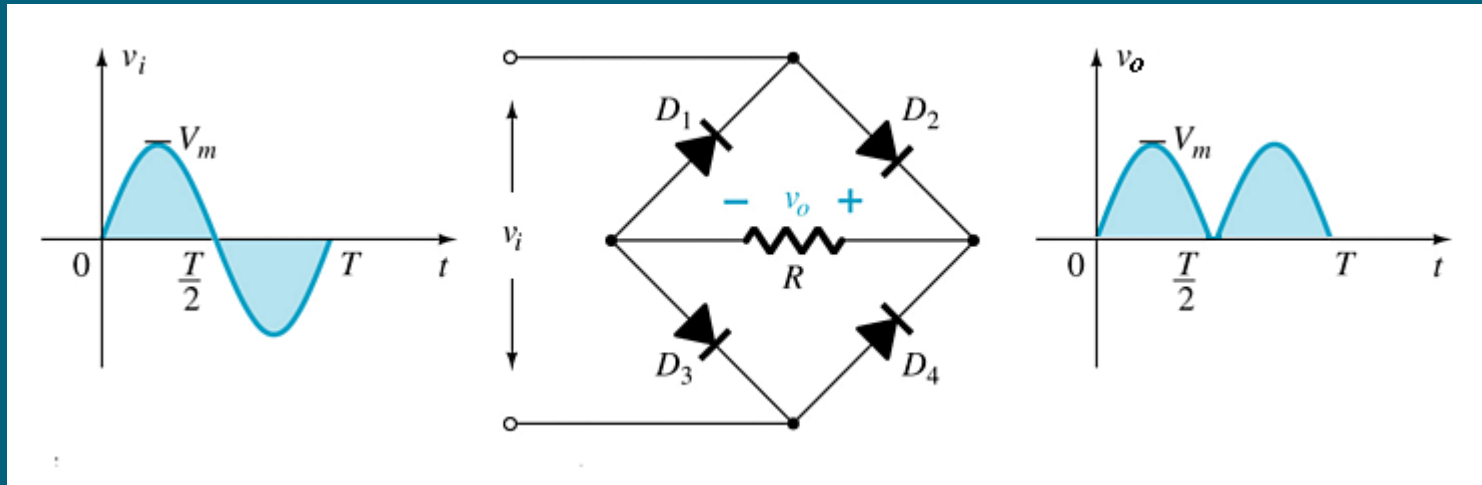

Bridge Rectifier

- Four diodes are required
- $V_{DC} = 0.636 V_m$

Full-Wave Rectification

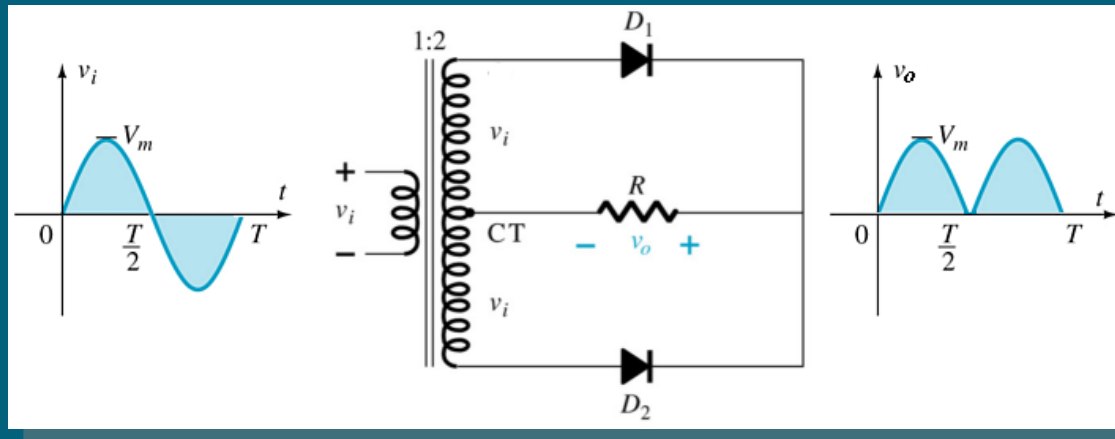

Center-Tapped Transformer Rectifier


Requires

- Two diodes
- Center-tapped transformer


$$V_{DC} = 0.636(V_m)$$

Zener Diodes

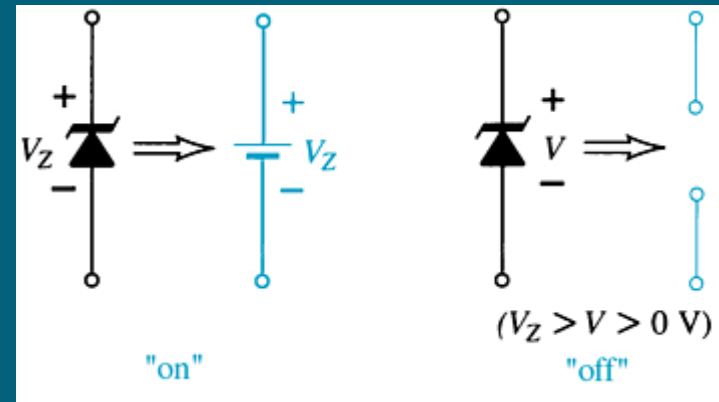The Zener is a diode operated in reverse bias at the Zener Voltage (V_Z).



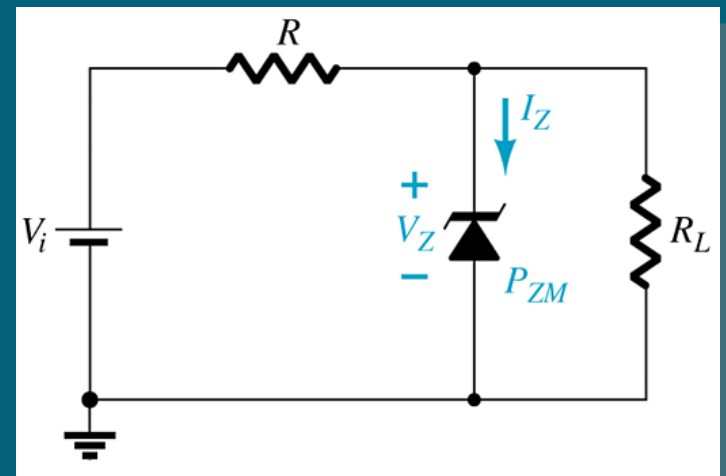- When $V_i \geq V_Z$
 - The Zener is on
 - Voltage across the Zener is V_Z
 - Zener current: $I_Z = I_R - I_{RL}$
 - The Zener Power: $P_Z = V_Z I_Z$
- When $V_i < V_Z$
 - The Zener is off
 - The Zener acts as an open circuit



Zener Resistor Values

If R is too large, the Zener diode cannot conduct.

The minimum current is given by:

$$I_{Lmin} = I_R - I_{ZK}$$

The *maximum* value of resistance is:


$$R_{Lmax} = \frac{V_Z}{I_{Lmin}}$$

If R is too small, maximum current for the circuit :

$$I_{Lmax} = \frac{V_L}{R_L} = \frac{V_Z}{R_{Lmin}}$$

The *minimum* value of resistance is:


$$R_{Lmin} = \frac{RV_Z}{V_i - V_Z}$$

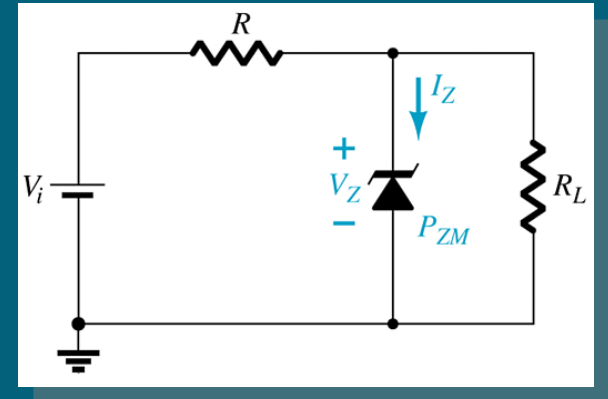

Voltage-Multiplier Circuits

- **Voltage Doubler**
- **Voltage Tripler**
- **Voltage Quadrupler**

Voltage Doubler

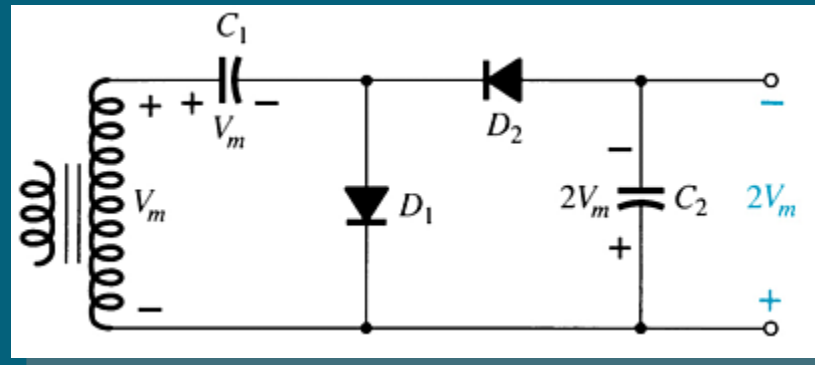

Output of the half-wave voltage doubler's:

$$V_{\text{out}} = V_{C_2} = 2V_m$$

V_m = peak secondary voltage of the transformer