

**EE-202 Electronics**  
**Chapter 5:**  
**Bipolar Junction Transistors**  
**Common Base Configuration**

# Transistor Construction


Two types of transistors:

- *pnp*
- *npn*


The terminals are:

- **E** - Emitter
- **B** - Base
- **C** - Collector

*pnp*

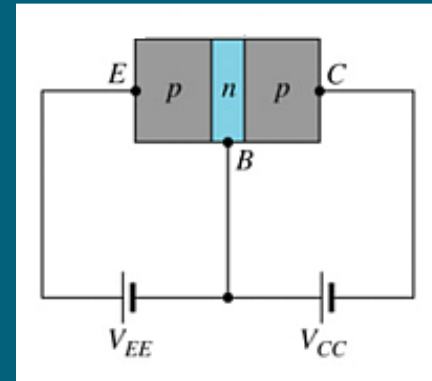

*npn*

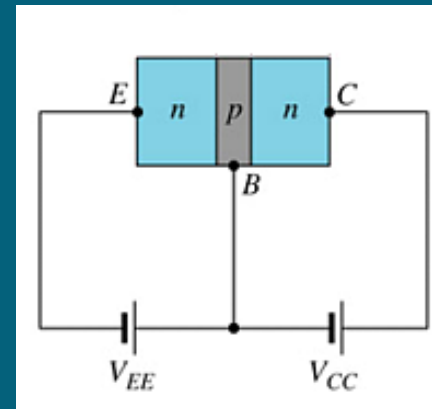


# Transistor Operation

For pnp transistor,

External sources,  $V_{EE}$  and  $V_{CC}$ , are connected as:

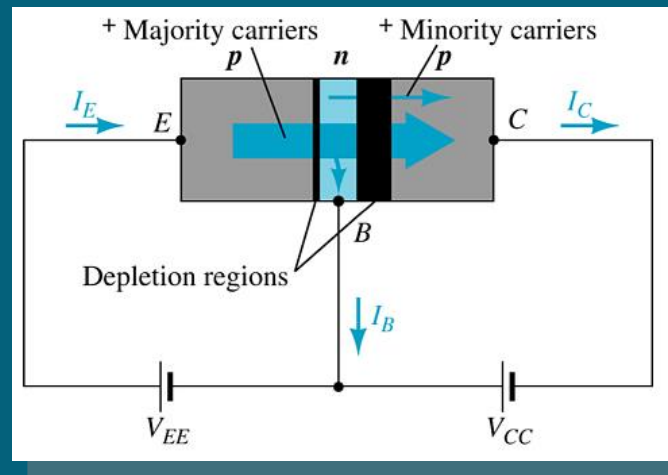- The E-B junction is forward biased
- The B-C junction is reverse biased




# Currents in a Transistor

For npn transistor,  
Emitter current is :


$$I_E = I_C + I_B$$

The collector current is :
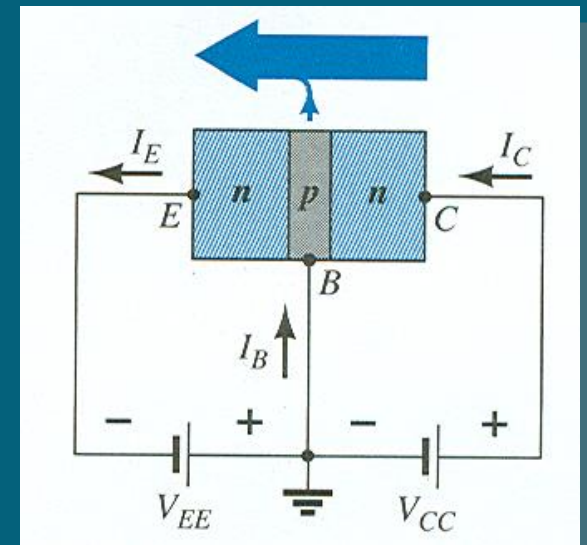
$$I_C = I_{C\text{majority}} + I_{C0\text{minority}}$$



# Common-Base Configuration

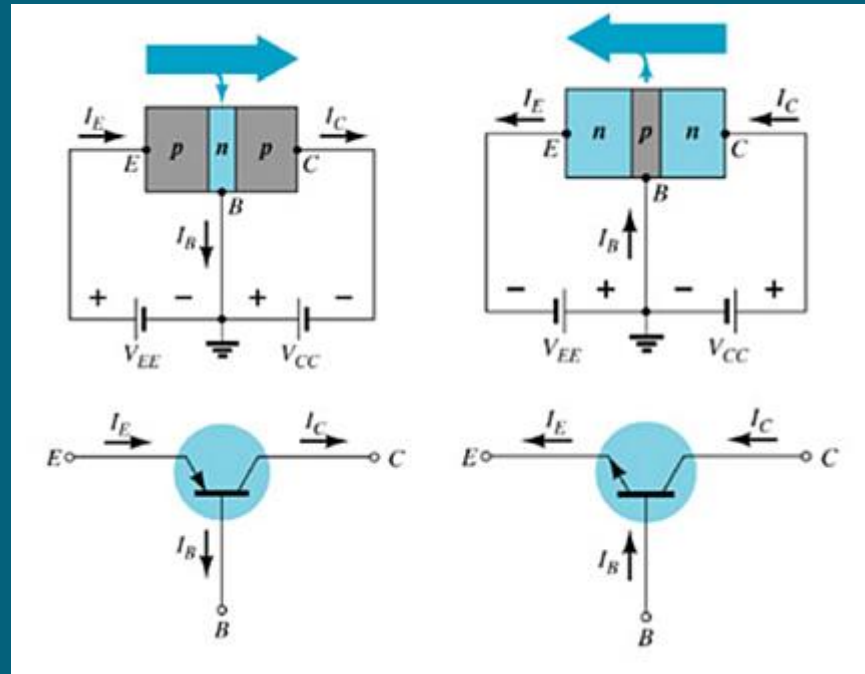


The base is common for input (E–B) and output (C–B) .

# Common-Base Amplifier
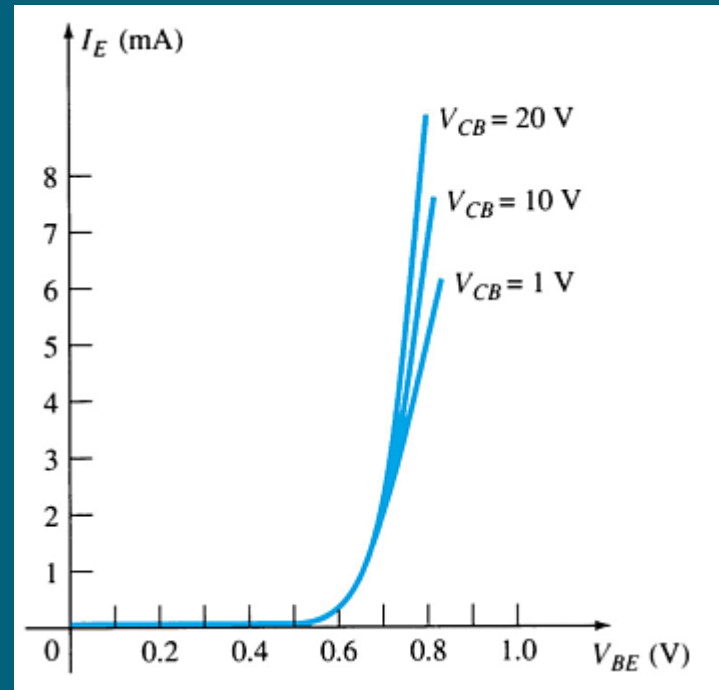
## Input Characteristics

This curve shows the relationship between the input current ( $I_E$ ) and input voltage ( $V_{BE}$ ) for different levels of output voltage ( $V_{CB}$ ).



# Common-Base Amplifier

## Output Characteristics

The relationship between output current ( $I_C$ ) and output voltage ( $V_{CB}$ ) for various levels of input current ( $I_E$ ).


## Operating Regions

**Active**—Operating range of the amplifier.

**Cutoff**—Transistor off. There is voltage, but little current.

**Saturation**—Transistor fully on.

There is current, but little voltage.

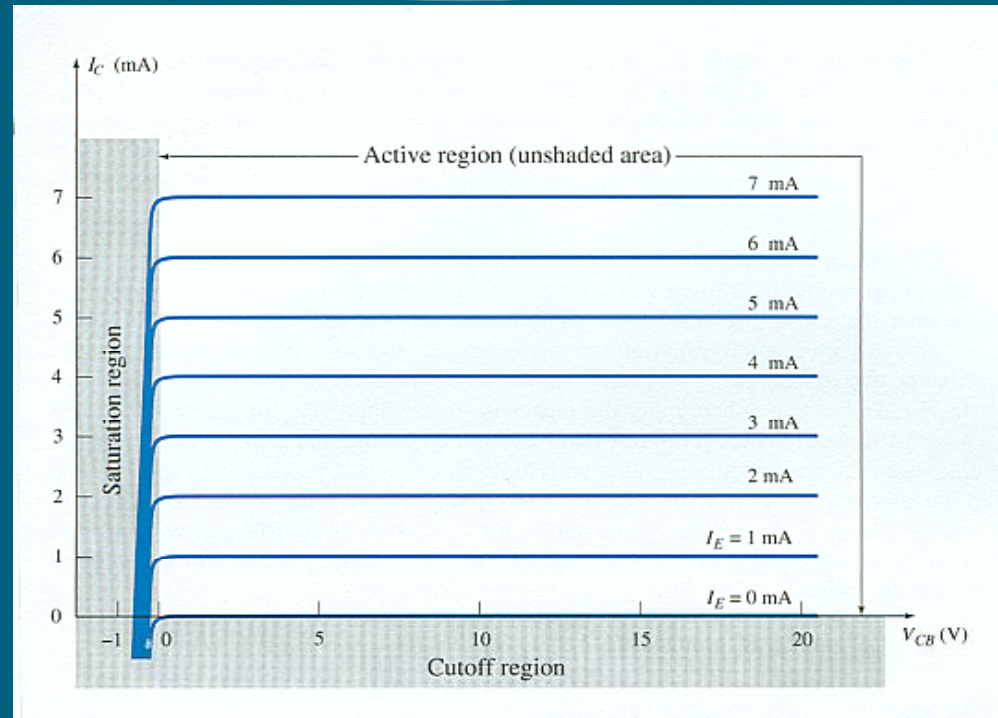

## Approximations

Emitter and collector currents:

$$I_C \cong I_E$$

Base-emitter voltage:

$$V_{BE} = 0.7$$