



# **EE-202 Electronics-I-**

## **Chapter 6:**


# **Bipolar Junction Transistors Common Emitter-Common Base Configurations**
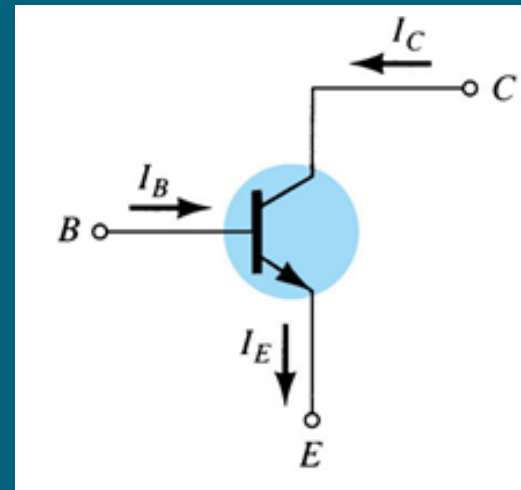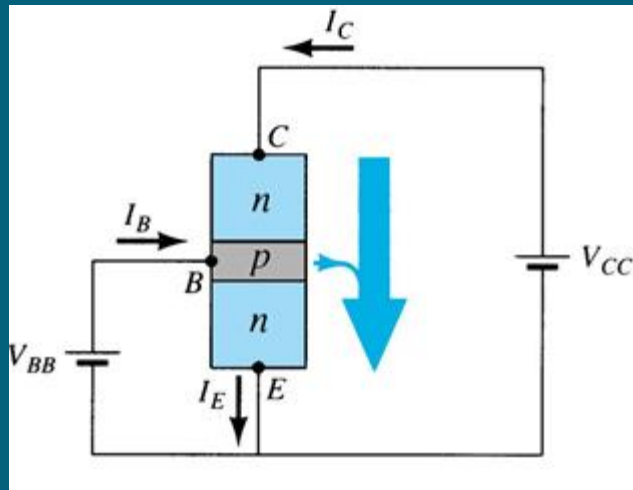
# Common-Emitter Configuration


The emitter is common to both input (base-emitter) and output (collector-emitter).



# Common-Emitter Characteristics

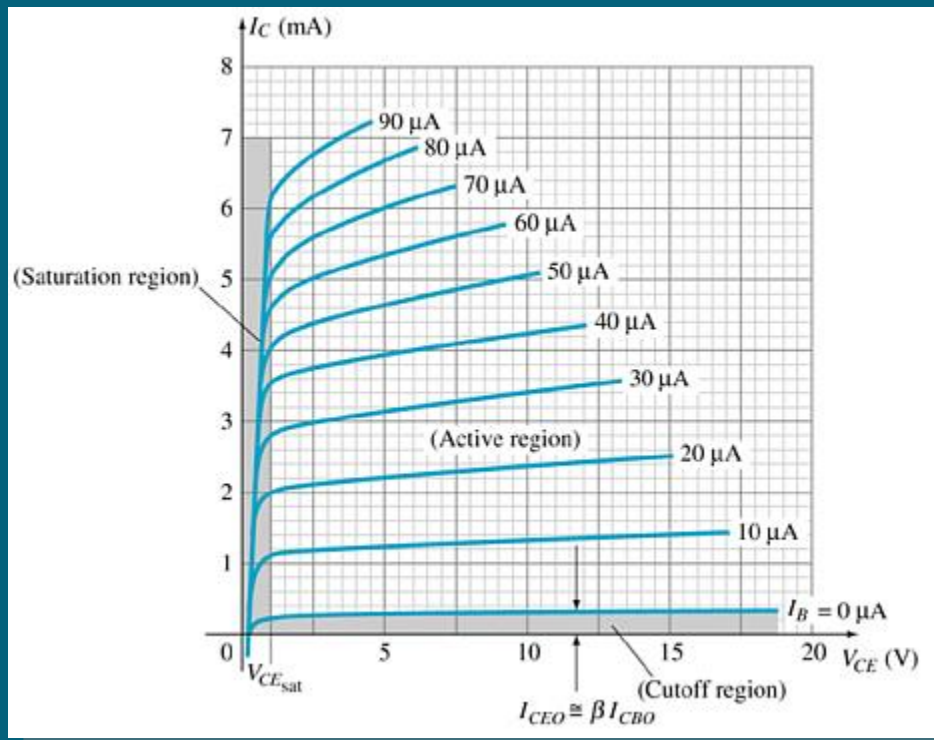

Collector Characteristics

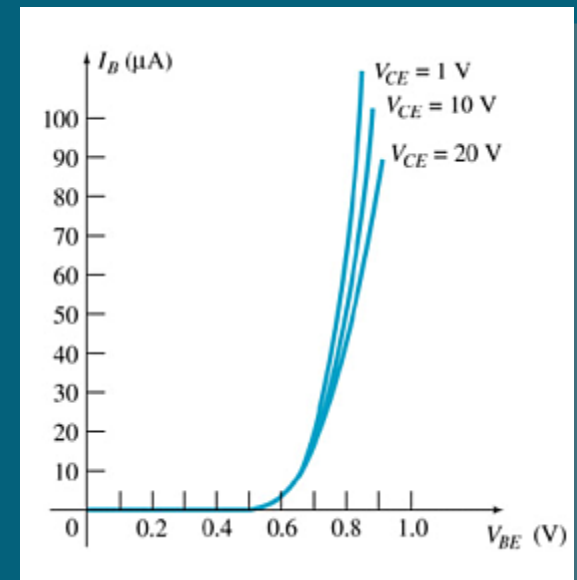

Base Characteristics

# Common-Emitter Amplifier Currents

## Ideal

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E$$

## Actual

where  $I_{CBO}$  = minority collector current

$$I_C = \alpha I_E + I_{CBO}$$

When  $I_B = 0 \mu\text{A}$  the transistor is in cutoff, but there is some minority current called  $I_{CEO}$ .

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \Big|_{I_B = 0 \mu\text{A}}$$

# Beta ( $\beta$ )

$\beta$  : amplification factor.

**DC mode:**

$$\beta_{dc} = \frac{I_C}{I_B}$$

**AC mode:**

$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$

# Beta ( $\beta$ )

Relationship between amplification factors  $\beta$  and  $\alpha$


$$\alpha = \frac{\beta}{\beta + 1} \qquad \beta = \frac{\alpha}{\alpha - 1}$$

Relationship Between Currents

$$I_C = \beta I_B \qquad I_E = (\beta + 1) I_B$$
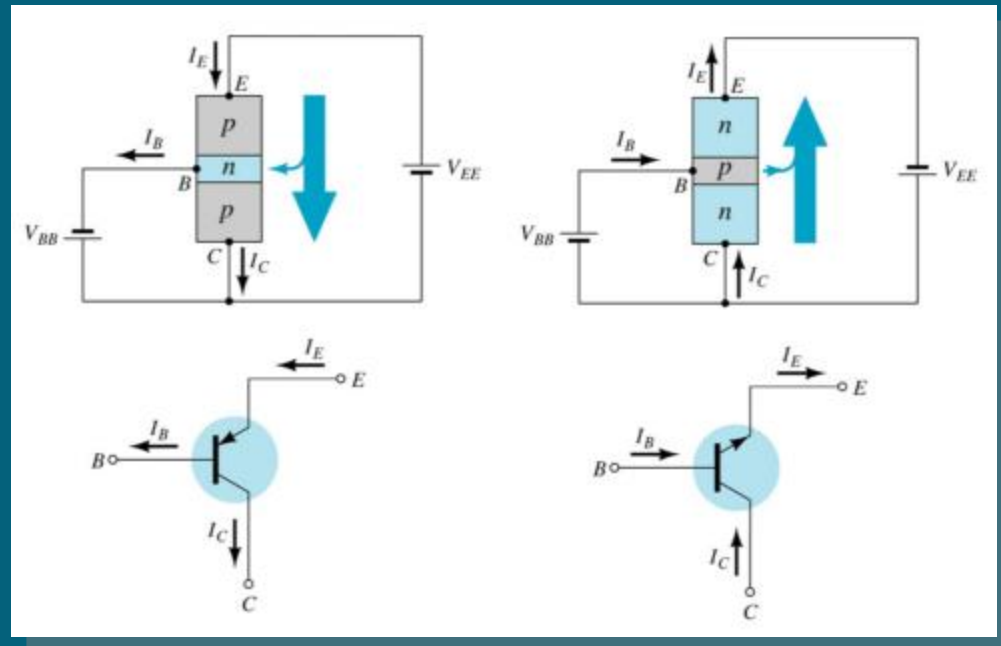
# Common-Collector Configuration

The input is on the base and the output is on the emitter.



# Common-Collector Characteristics

The characteristics are similar to those of the common-emitter configuration, except the vertical axis is  $I_E$ .

